
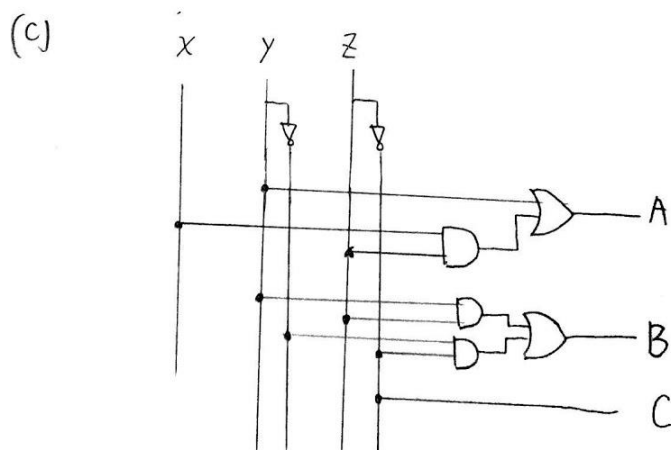


HW4-1 solution

1. (20%) Design a combinational circuit with three inputs, x (MSB), y , and z (LSB), and three outputs, A (MSB), B , and C (LSB). When the binary input is 0, 2 or 3, the binary output is three greater than the input ($xyz=000$ (0) \Rightarrow $ABC=011$ (3), $xyz=010$ (2) \Rightarrow $ABC=101$ (5).). When the binary input is 1, 4, 5, 6, or 7, the binary is one less than the input ($xyz=110$ (6) \Rightarrow $ABC=101$ (5), $xyz=100$ (4) \Rightarrow $ABC=011$ (1)).
- (a) Derive the truth table. (5%)
- (b) Derive the simplified Boolean expressions for A , B , and C using maps. (10%)
- (c) Draw the related logic diagram. (5%)

(a)





x	y	z	A	B	C
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

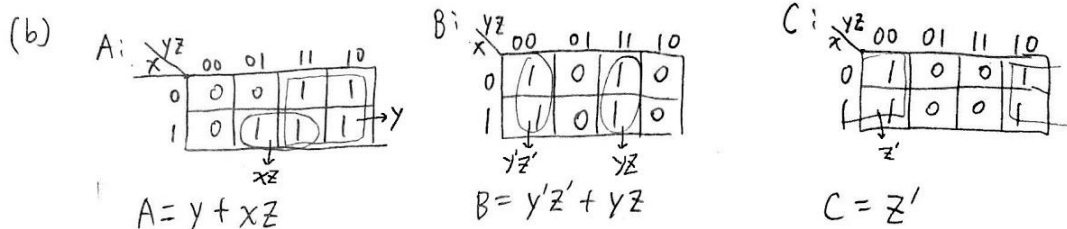

2. (10%) Design an excess-3-to-binary decoder using the unused combinations of the code as don't-care conditions.


2. Excess-3 to binary decoder
(wxyz) (b3b2b1b0)

Excess-3				binary			
w	x	y	z	b3	b2	b1	b0
0	0	0	0	x	x	x	x
0	0	0	1	x	x	x	x
0	0	1	0	x	x	x	x
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

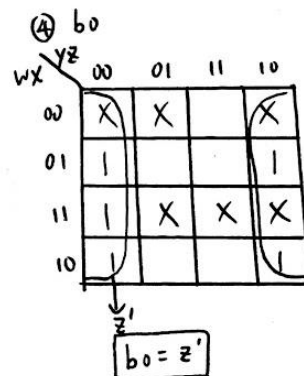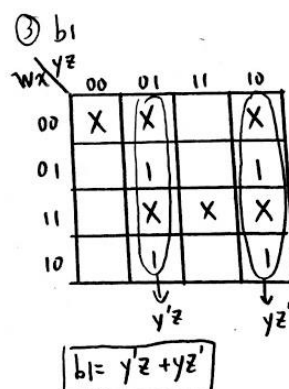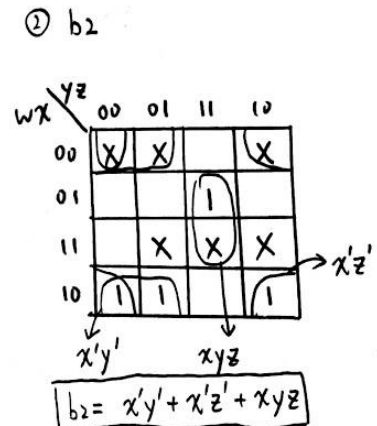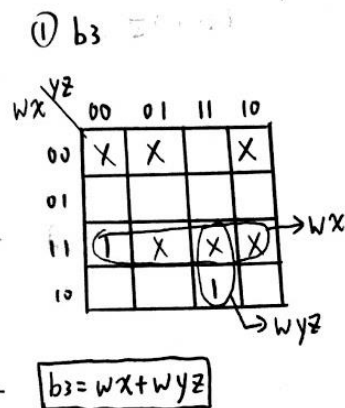

$$\begin{cases} b_3 = wx + wyz \\ b_2 = x'y' + x'z' + xyz \\ b_1 = y'z + yz' \\ b_0 = z' \end{cases}$$

題目未要求電路圖
做到 Boolean 即可算對

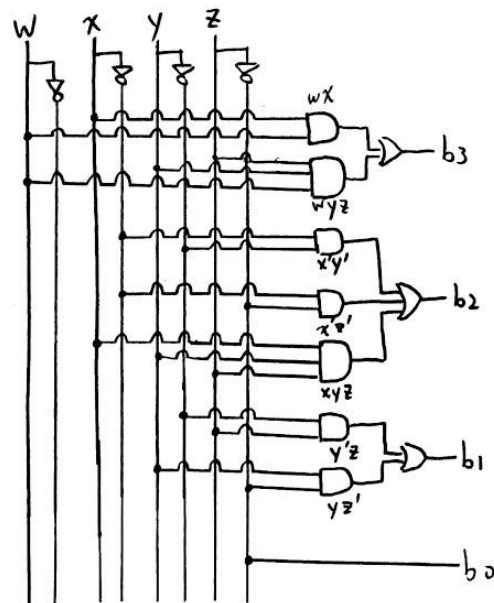

3. (10%) Design a 3-bit absolute value calculator. ($Z=|z|$).

b_2	b_1	b_0	y_2	y_1	y_0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	0	X	X
1	0	1	0	1	1
1	1	0	0	1	0
1	1	1	0	0	1

① for y_2
 $y_2 = 0$

② for y_1

b_2
0
1

	$b_2 b_0$	00	01	11	10
0				1	1
1		1	1	1	1

$b_2' b_1$
 $b_2 b_1'$
 $b_1 b_0'$

$y_1 = b_2 b_1' + b_2' b_1 + b_1 b_0'$


③ for y_0

b_2
0
1

	$b_2 b_0$	00	01	11	10
0			1	1	
1		1	1	1	1

b_0
 $y_0 = b_0$

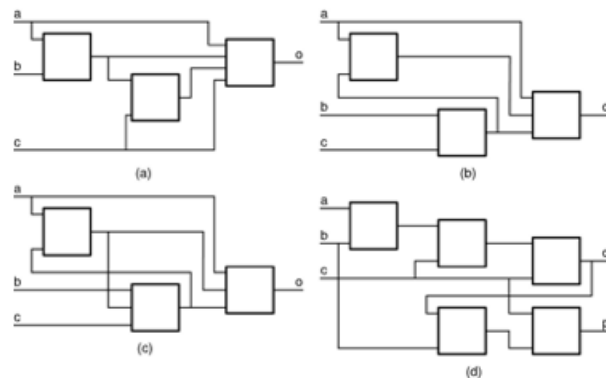4. (10%) Which of the following circuits are combinational? Each box in the figure is itself a combinational circuit.



Ans:

c 的 feedback 會出現 loop，故只有 c 不為 Combinational circuits

