

Combinational Logic

Hsi-Pin Ma 馬席彬

<https://elearn.nthu.edu.tw/course/view.php?id=8548>

Department of Electrical Engineering
National Tsing Hua University

Outline

- Combinational Circuits
- Analysis of Combinational Circuits
- Design Procedure
- Binary Adder-Subtractor
- Decimal Adder
- Binary Multiplier
- Magnitude Comparator
- Decoder
- Encoders
- Arbiters
- Multiplexers
- Shifters

Combinational Circuits


Logic Circuits for the Digital System

- **Combinational circuits** 輸出只與輸入有關，不會因時間而改變


- Logic circuits whose outputs at any time are determined *directly and only* from the present *input combination*.

- **Sequential circuits** 輸出與輸入、狀態（時間）有關

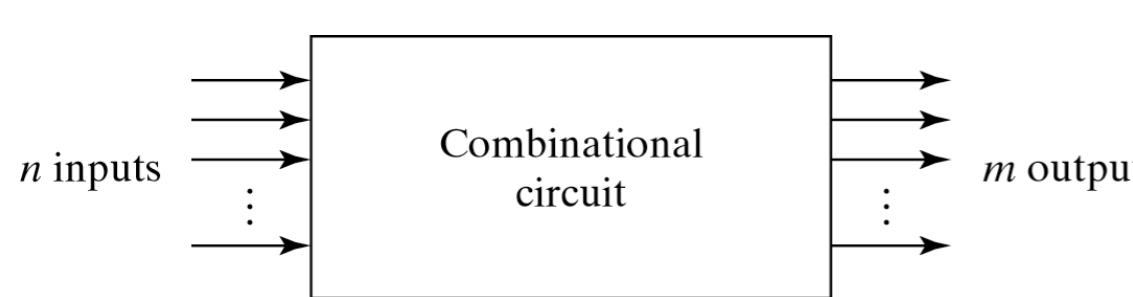- Circuits that employ memory elements + (combinational) logic gates 記憶元件
- Outputs are determined from the present input combination as well as the state of the memory cells.



Hsi-Pin Ma feedforward 只會往前

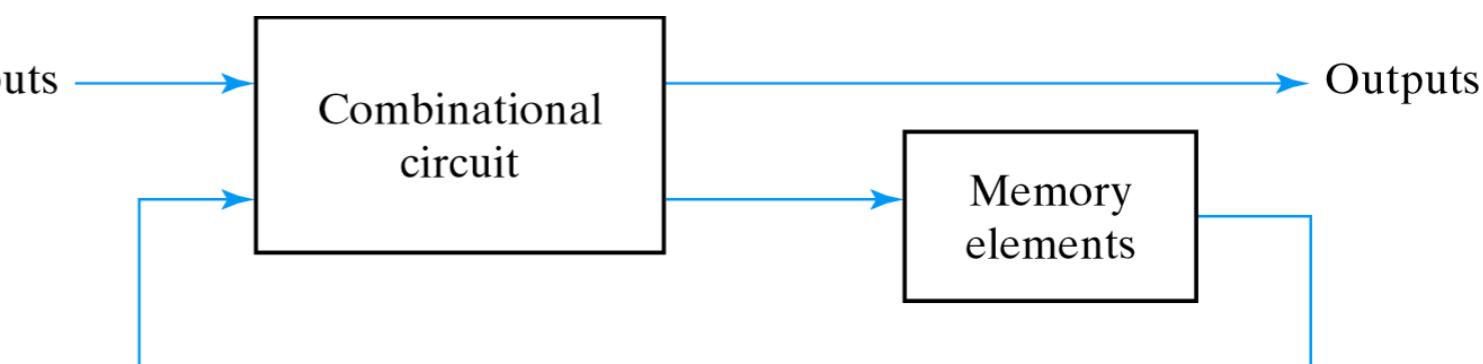


由後往前的箭頭 feedback

Combinational Logic Circuits


- Memoryless: $o=f(i)$

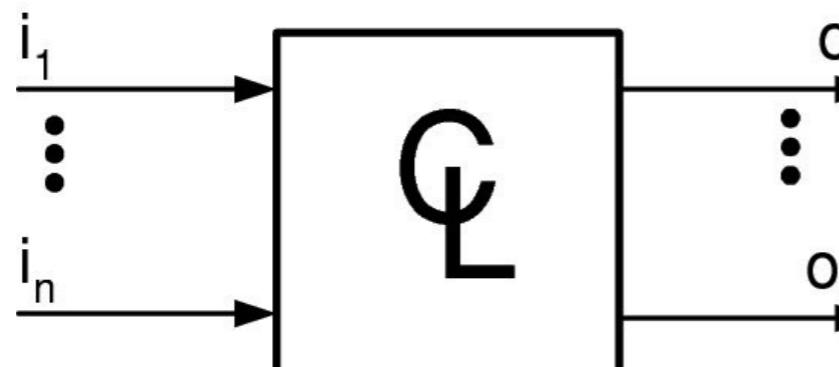- Used for control, arithmetic, and data steering.



(a)

CL = combinational logic

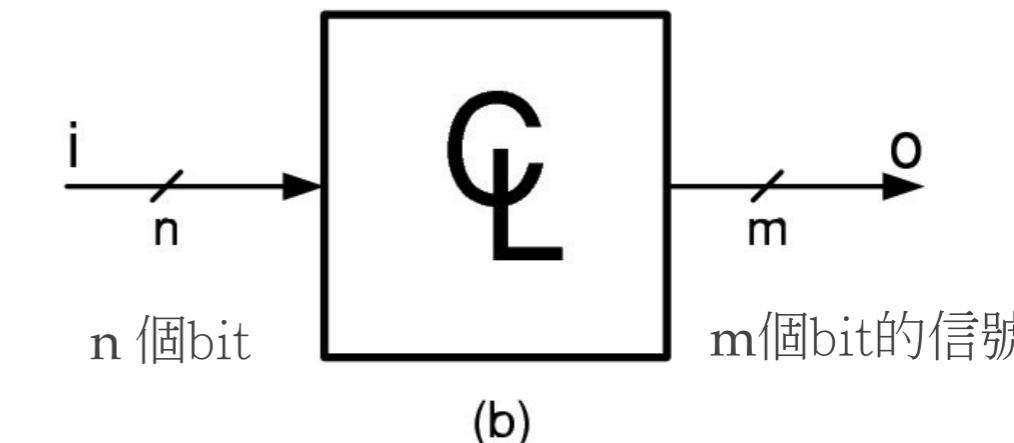

(b)

a 的簡化



Closure

- Combinational logic circuits are closed under ***acyclic*** composition

// acyclic: not displaying a form of a cycle

- Cyclic composition of two combinational logic circuits

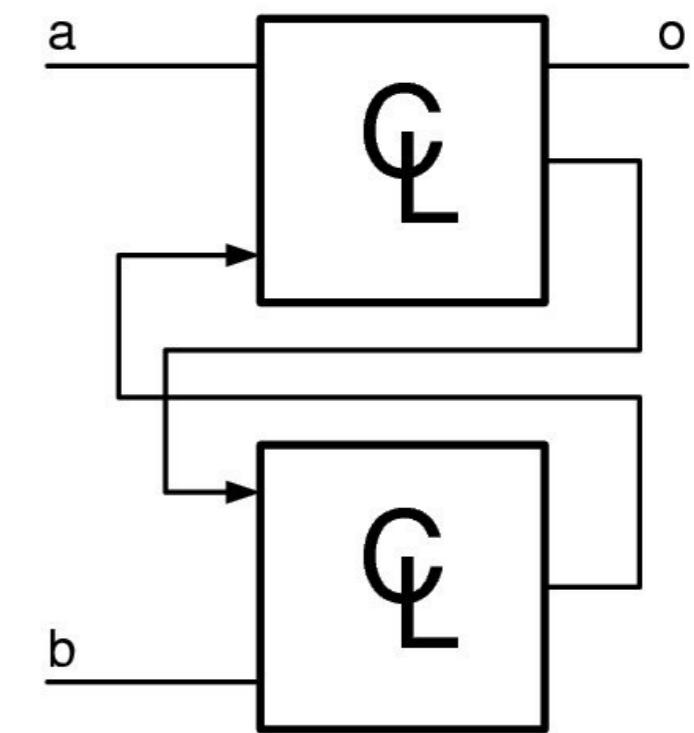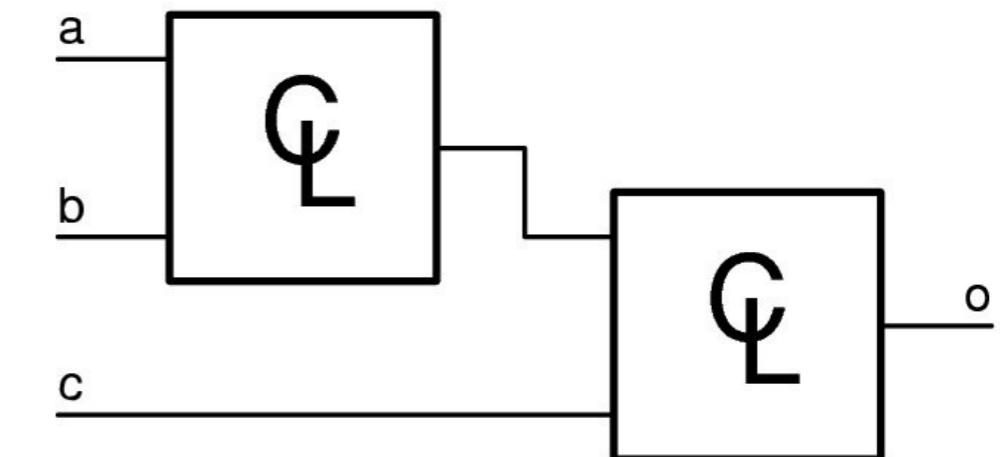- The ***feedback*** variable can remember the ***history*** of the circuits
- Sequential logic circuit



Analysis of Combinational Circuits

Analysis Procedure

- Analysis for an available logic diagram
 - Make sure the given circuit is combinational
 - No *feedback path* or *memory element*
 - Derive the corresponding *Boolean functions*
 - Derive the corresponding *truth table*
 - Verify and analyze the design
 - Logic simulation (waveforms)
 - Explain the function


Derivation of Boolean Functions (1/2)

- Label all gate outputs that are functions of the input variables only. Determine the functions.
- Label all gate outputs that are functions of the input variables and previously labeled gate outputs, and find the functions.
- Repeat previous step until all the primary outputs are obtained.

Derivation of Boolean Functions (2/2)

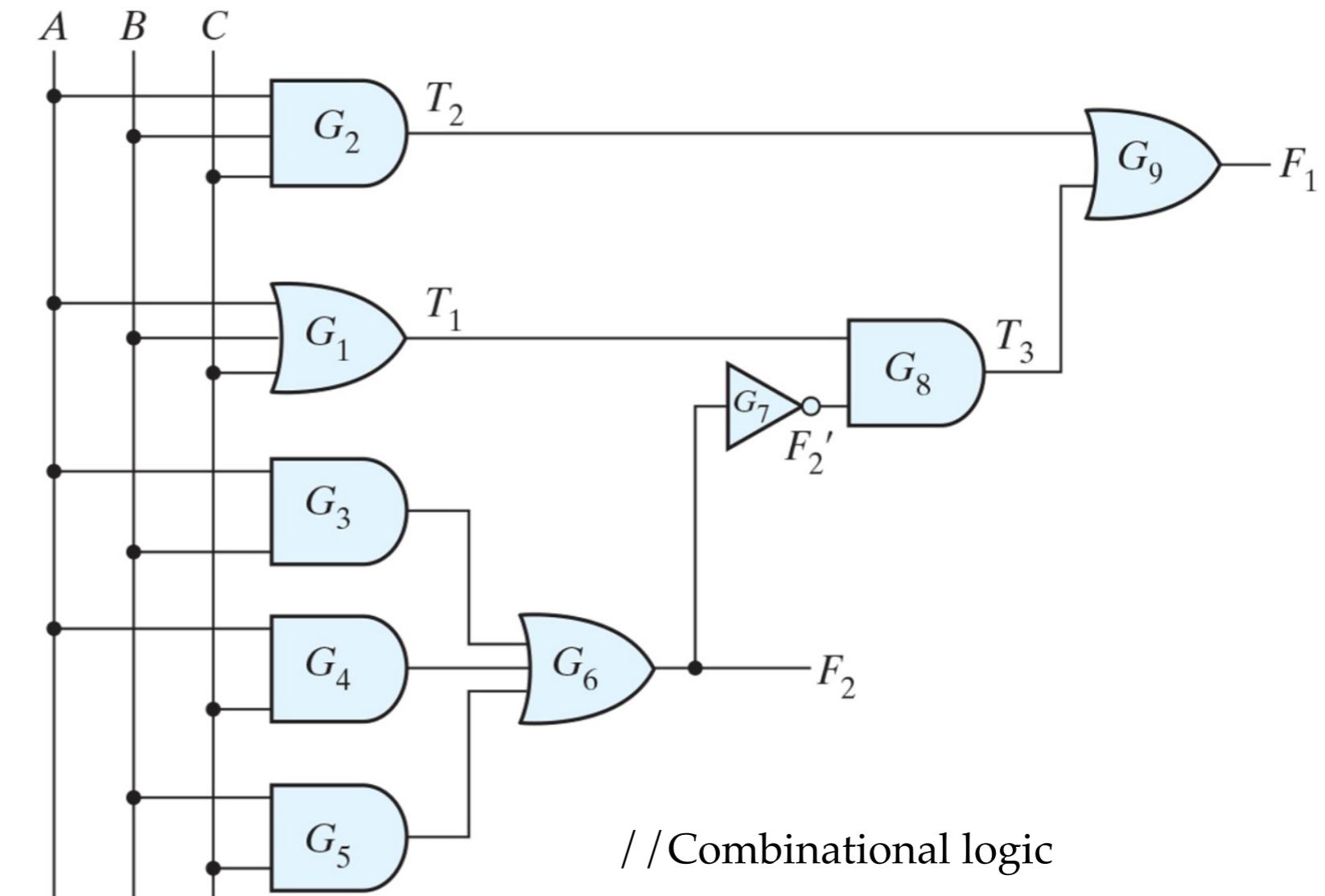- Example

- List all functions
 - $F_2 = AB + AC + BC$
 - $T_1 = A + B + C$
 - $T_2 = ABC$
 - $T_3 = F_2' T_1$
 - $F_1 = T_3 + T_2$



- $F_1 = T_3 + T_2 = F_2' T_1 + ABC = (AB + AC + BC)'(A + B + C) + ABC = A'BC' + A'B'C + AB'C' + ABC$
- Full adder (F_1 : sum, F_2 : carry)

Derivation of Truth Table (1/2)

- For n input variables
 - List all the 2^n input combinations from 0 to 2^n-1 .
 - Partition the circuit into small single-output blocks and label the output of each block.
 - Obtain the truth table of the blocks depending on the input variables only.
 - Proceed to obtain the truth tables for other blocks that depend on previously defined truth tables.

Derivation of Truth Tables (2/2)

- Example

A	B	C	F_2	F'_2	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Design Procedure

Design Procedure

- 1 • **Specification:** From the *specifications*, determine the inputs, outputs, and their symbols.
- 2 • **Formulation:** Derive the *truth table (functions)* from the relationship between the inputs and outputs
- 3 • **Optimization:** Derive the *simplified Boolean functions* for each output function. Draw a logic diagram or provide a netlist for the resulting circuits using AND, OR, and inverters.
- 4 • **Technology Mapping:** Transform the logic diagram or netlist to a new diagram or netlist using the available implementation technology.
- **Verification:** Verify the design.

最簡單的驗證法：input所有值看output是否和truth table一樣

A BCD-to-Excess-3 Code Converter (1/3)

- Spec 1

– input (ABCD), output (wxyz) (MSB to LSB)

– ABCD: 0000 ~ 1001 (0~9)

- Formulation 2

– $wxyz = ABCD + 0011$

// 教完verilog就會寫

$$w = f_1(A, B, C, D)$$

$$x = f_2(A, B, C, D)$$

$$y = f_2(A, B, C, D)$$

$$z = f_3(A, B, C, D)$$







Input BCD Output Excess-3 Code

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

don't care

A BCD-to-Excess-3 Code Converter (2/3)

- Optimization 3

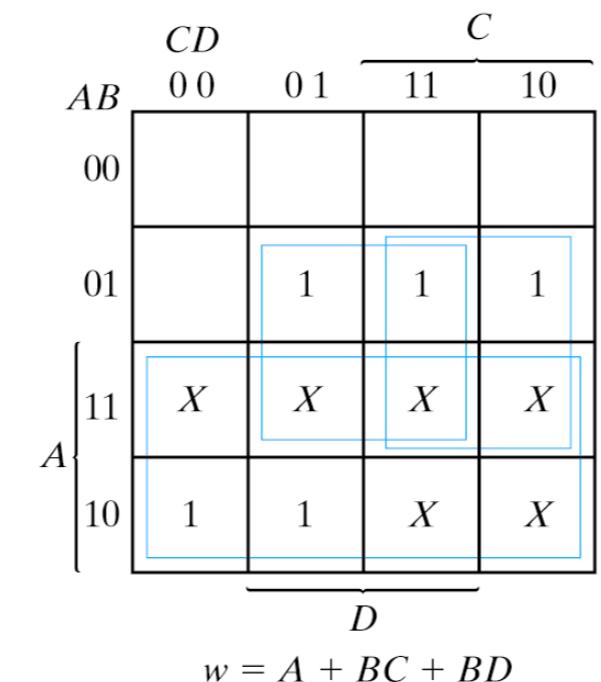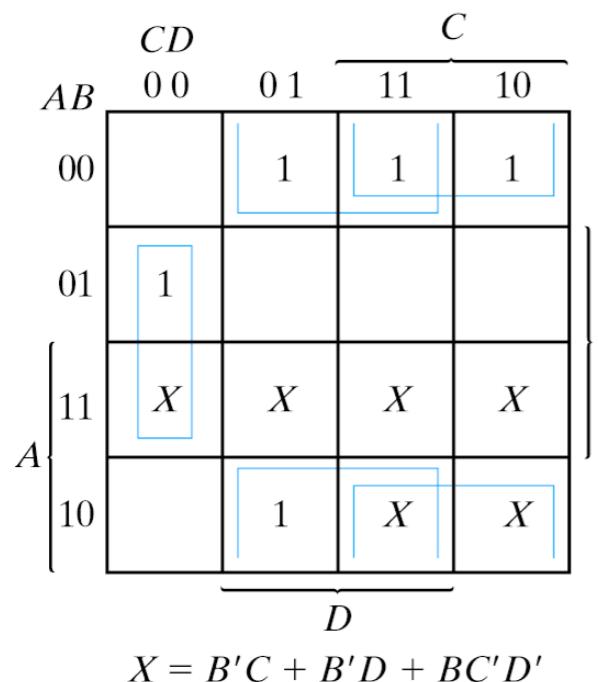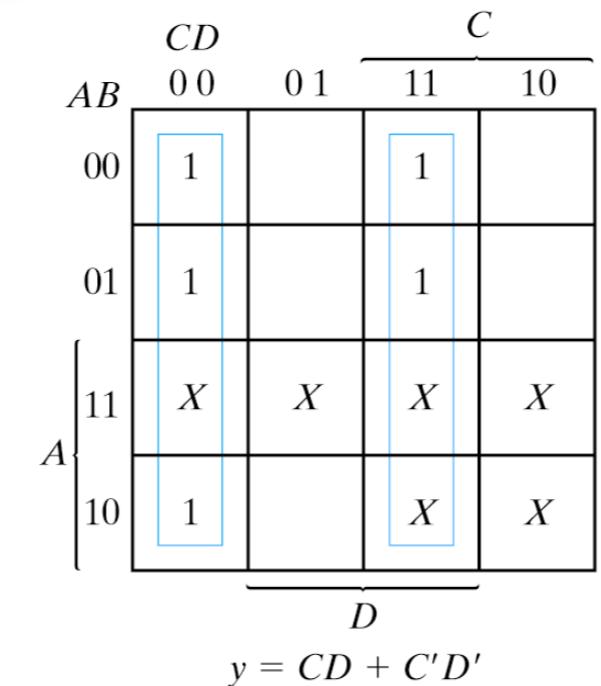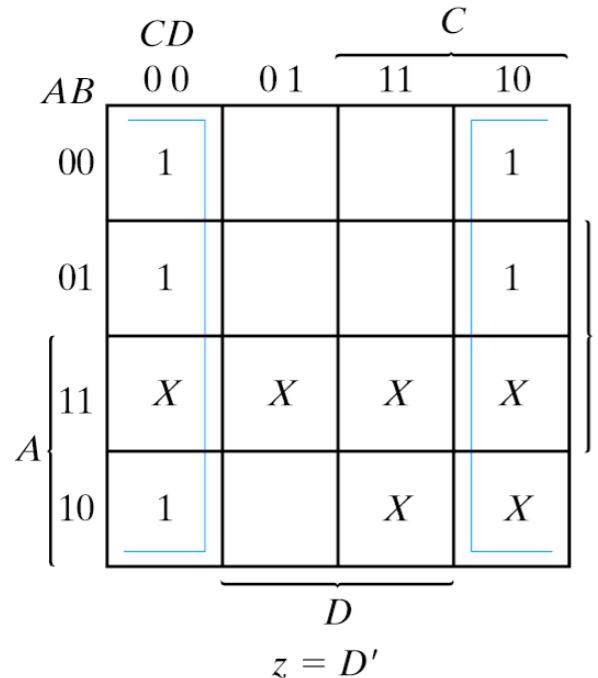

$$z = D'$$

$$y = CD + C'D'$$

$$x = B'C + B'D + BC'D'$$

$$w = A + BC + BD$$

from K-map

$$z = D'$$

$$y = CD + (C+D)'$$


$$x = B'(C+D) + BC'D'$$

$$w = A + B(C+D)$$

w, x, y 皆非standard form reduce gate numbers

A BCD-to-Excess-3 Code Converter (3/3)

4 4. Draw logic diagram

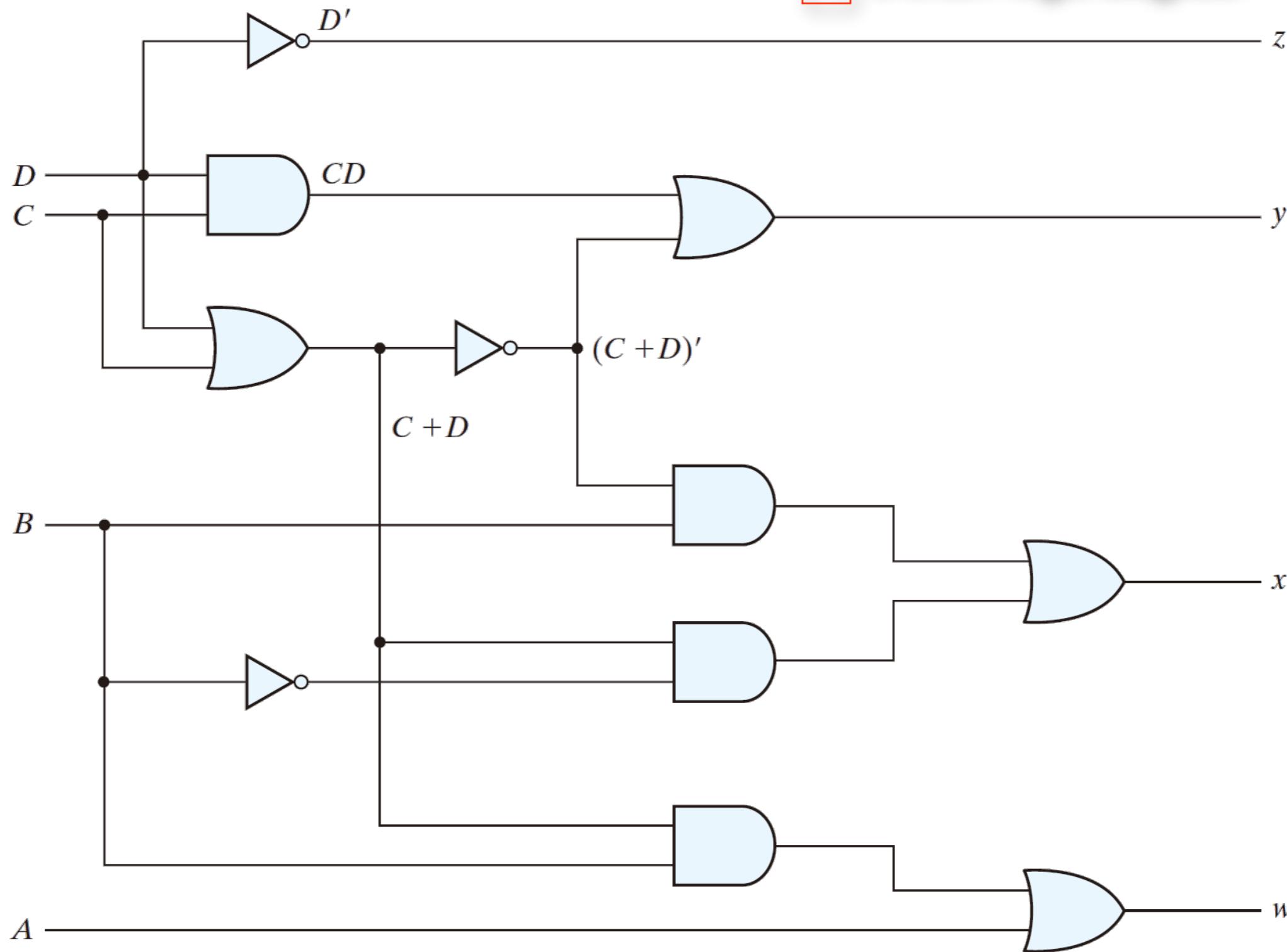

A BCD-to-Seven-Segment Display Decoder (1/2)

- Spec 1



- input (ABCD), output (abcdefg) (MSB to LSB)
- ABCD: 0000 ~ 1001 (0~9)

- Formulation 2

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

A BCD-to-Seven-Segment Decoder (2/2)

- Optimization 3

- 7x K-Map simplification
- $a = A'C + A'BD + B'C'D' + A'B'C'$
- $b = A'B' + A'C'D' + A'CD + AB'C'$
- $c = A'B + A'D + B'C'D' + AB'C'$
- $d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$
- $e = A'CD' + B'C'D'$
- $f = A'BC' + A'C'D' + A'BD' + AB'C'$
- $f = A'CD' + A'B'C + A'BC' + AB'C'$

- Technology Mapping 4

Binary Adder-Subtractor

Binary Half Adder & Full Adder (1/3)

- Half adder

- Inputs: x, y 進位

- Outputs: C (carry), S(sum)

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$


- Full adder

- Inputs: x, y, z(carry from previous lower significant bit)


- Outputs: C(carry), S(sum)

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + yz + zx$$

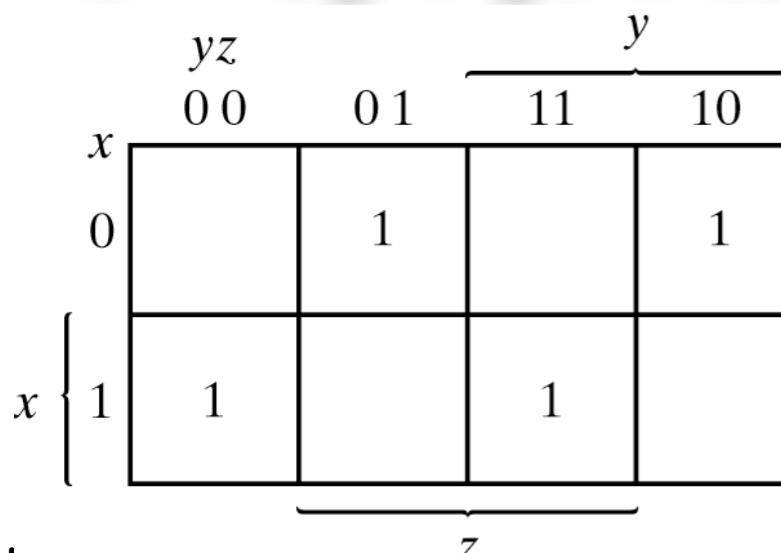

3

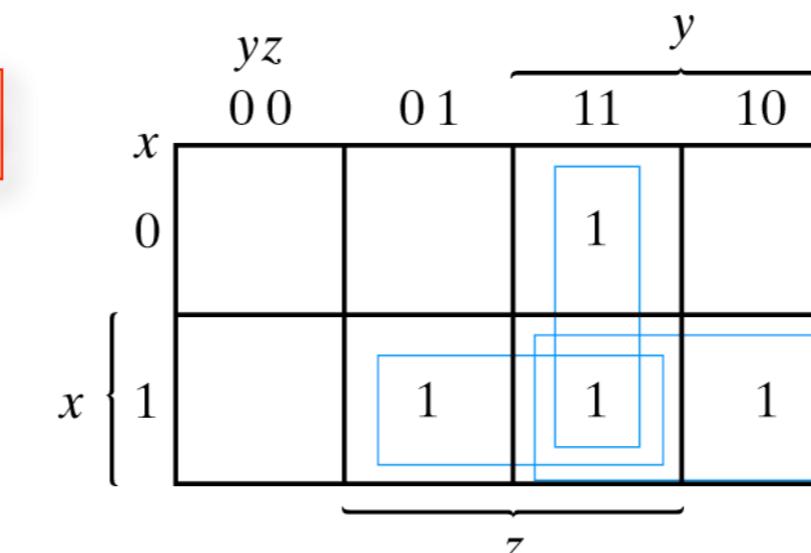

3


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	1	1

Binary Half Adder & Full Adder (2/3)

- Logic diagram 4



$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

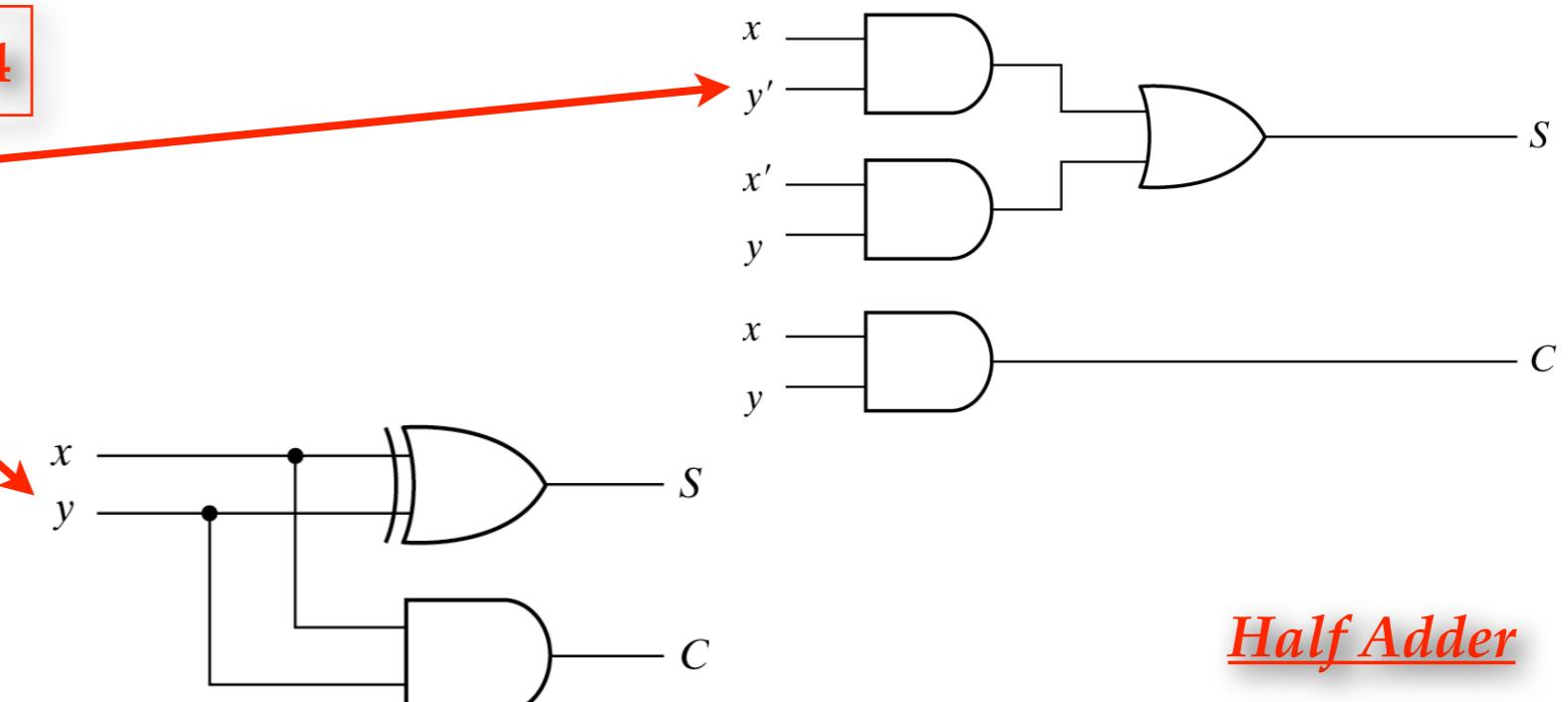

$$S = x'y'z + x'yz' + xy'z' = x \oplus y \oplus z$$

$$C = xy + yz + zx$$

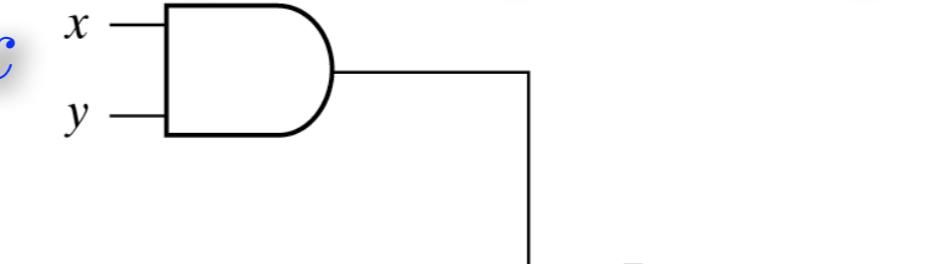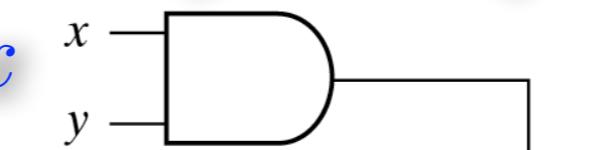


Full Adder

Binary Half Adder & Full Adder (3/3)

- Full adder implemented with half adders
 - Two half adders and one OR gate


$$S = z \oplus (x \oplus y)$$

$$C = z(xy' + x'y) + xy$$

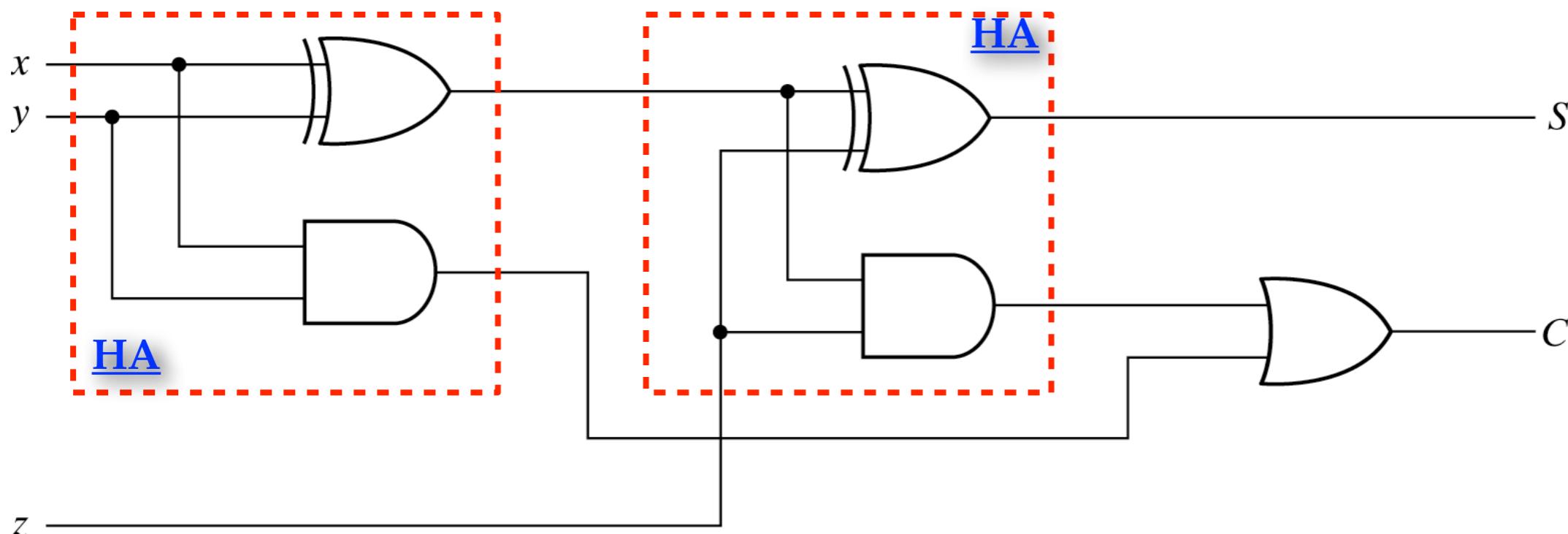

Verilog Description
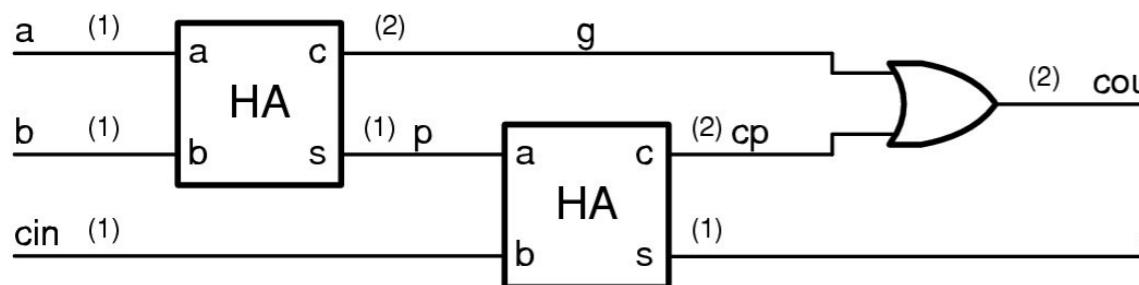
```
module HalfAdder(a, b, c, s);
  input a, b;
  output c, s; // carry and sum
  assign s = a ^ b;
  assign c = a & b;
endmodule
```







```
module FullAdder(a, b, cin, cout, s);
  input a, b, cin;
  output cout, s; // carry and sum
  wire g, p; // generate and propagate
  wire cp;
  HalfAdder ha1(.a(a), .b(b), .c(g), .s(p));
  HalfAdder ha2(.a(cin), .b(p), .c(cp), .s(s));
  assign cout = g | cp;
endmodule
```

Ripple-Carry Adder (1/4)

unsigned addition

$$(C_{n+1}S_nS_{n-1}\dots S_1) = (A_nA_{n-1}\dots A_1) + (B_nB_{n-1}\dots B_1)$$

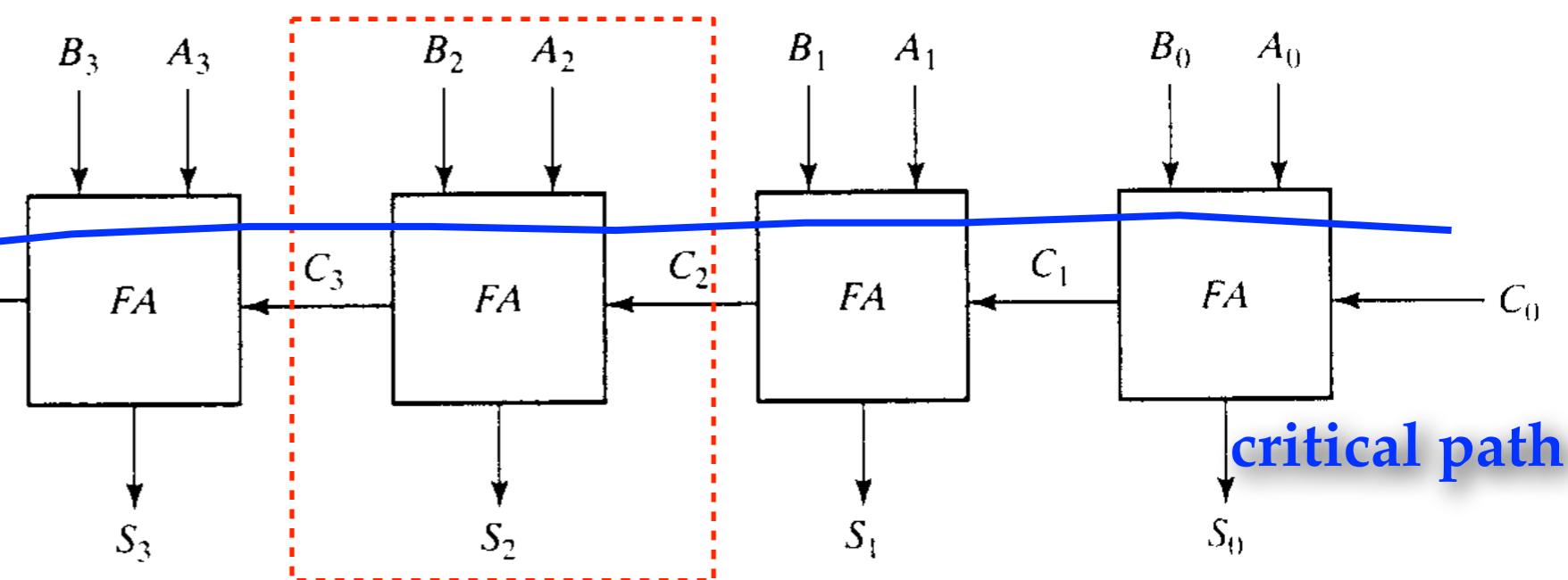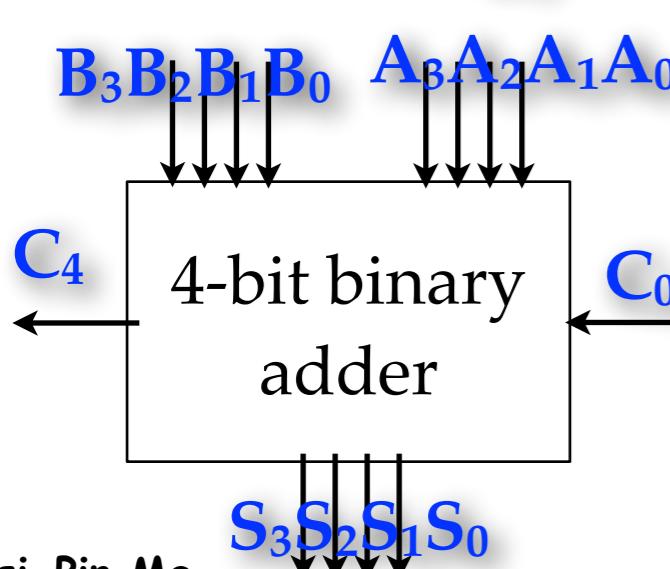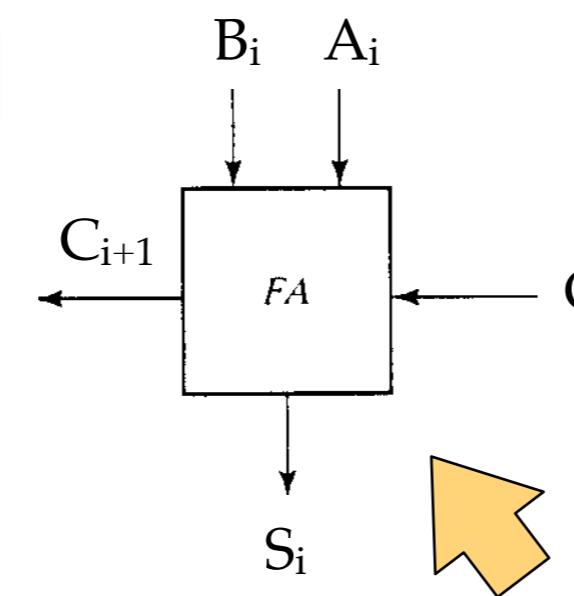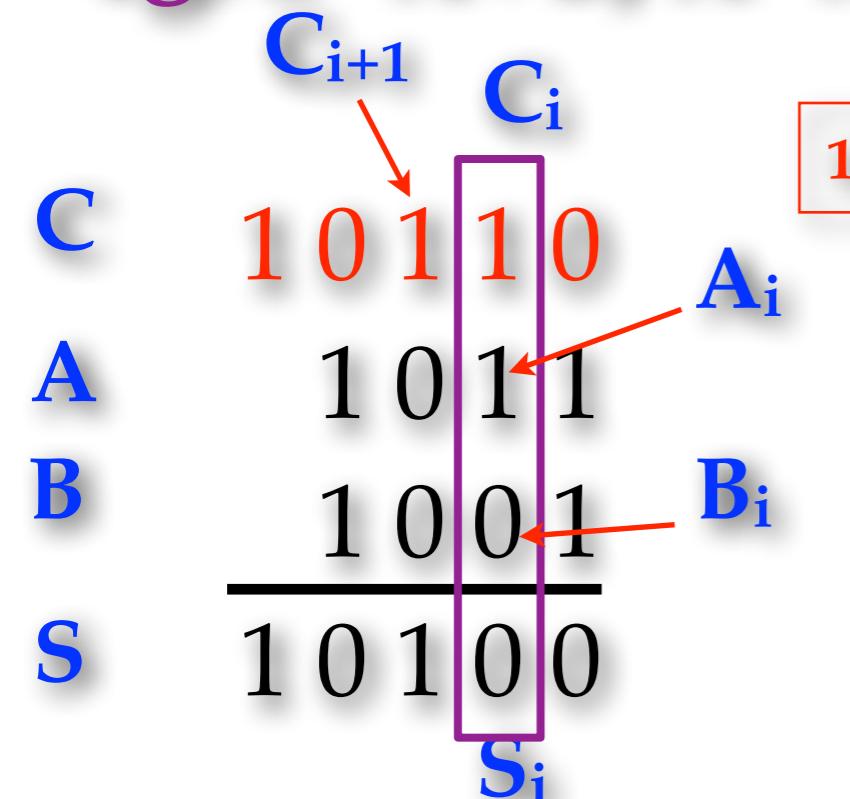
eg. $S=A+B$, $A=A_3A_2A_1A_0$, $B=B_3B_2B_1B_0$, $S=S_3S_2S_1S_0$



The computation time of a ripple-carry adder grows linearly with word length n

$T=O(n)$ due to **carry chain**

Ripple-Carry Adder (2/4)

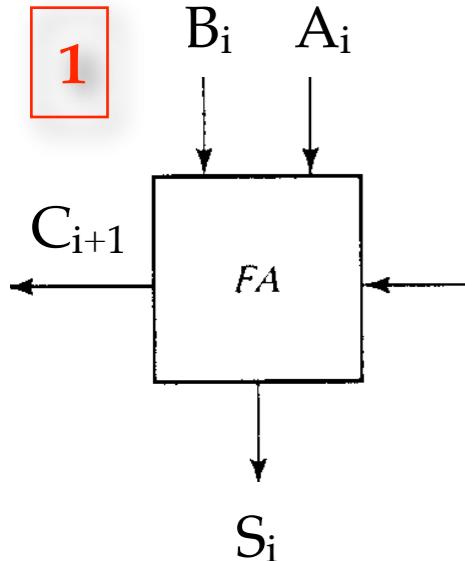

2


		A_iB_i	00	01	11	10
		C_i	0	1	3	2
		0	0	1		1
		1	4	5	7	6
			1	1	1	1
$S_i = A_i \oplus B_i \oplus C_i$						

3

		A_iB_i	00	01	11	10
		C_i	0	1	3	2
		0	0	1	1	
		1	4	5	7	6
			1	1	1	1
$C_{i+1} = A_iB_i + C_i(A_i \oplus B_i)$						

2

A_i	B_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

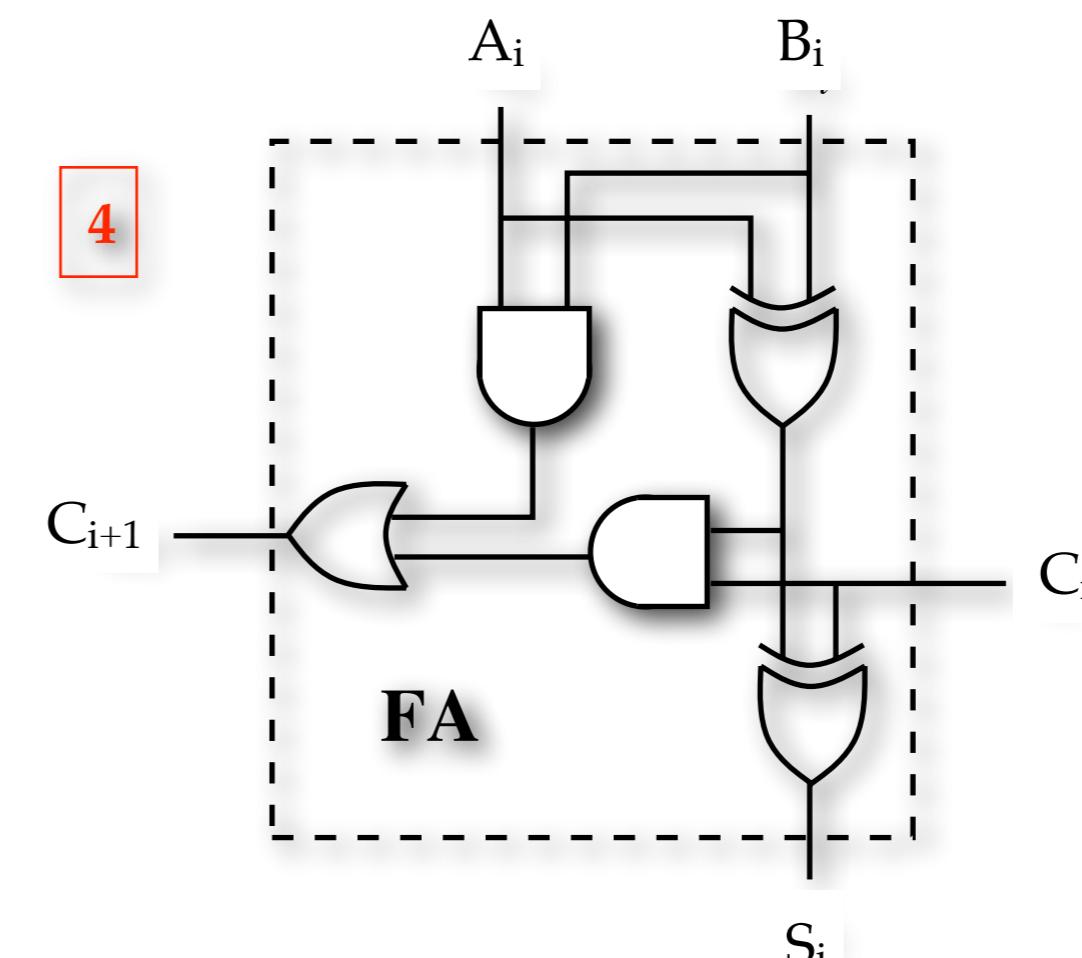

Ripple-Carry Adder (3/4)

define

$$S_i = f(A_i, B_i, C_i) = A_i \oplus B_i \oplus C_i$$
$$C_{i+1} = g(A_i, B_i, C_i) = A_i \cdot B_i + B_i \cdot C_i + C_i \cdot A_i$$

$$S_0 = f(A_0, B_0, C_0)$$
$$C_1 = g(A_0, B_0, C_0)$$


$$S_1 = f(A_1, B_1, C_1)$$
$$C_2 = g(A_1, B_1, C_1)$$

$$S_2 = f(A_2, B_2, C_2)$$
$$C_3 = g(A_2, B_2, C_2)$$

$$S_3 = f(A_3, B_3, C_3)$$
$$C_4 = g(A_3, B_3, C_3)$$


Multi-bit Notation

- Multi-bit signal or a bus

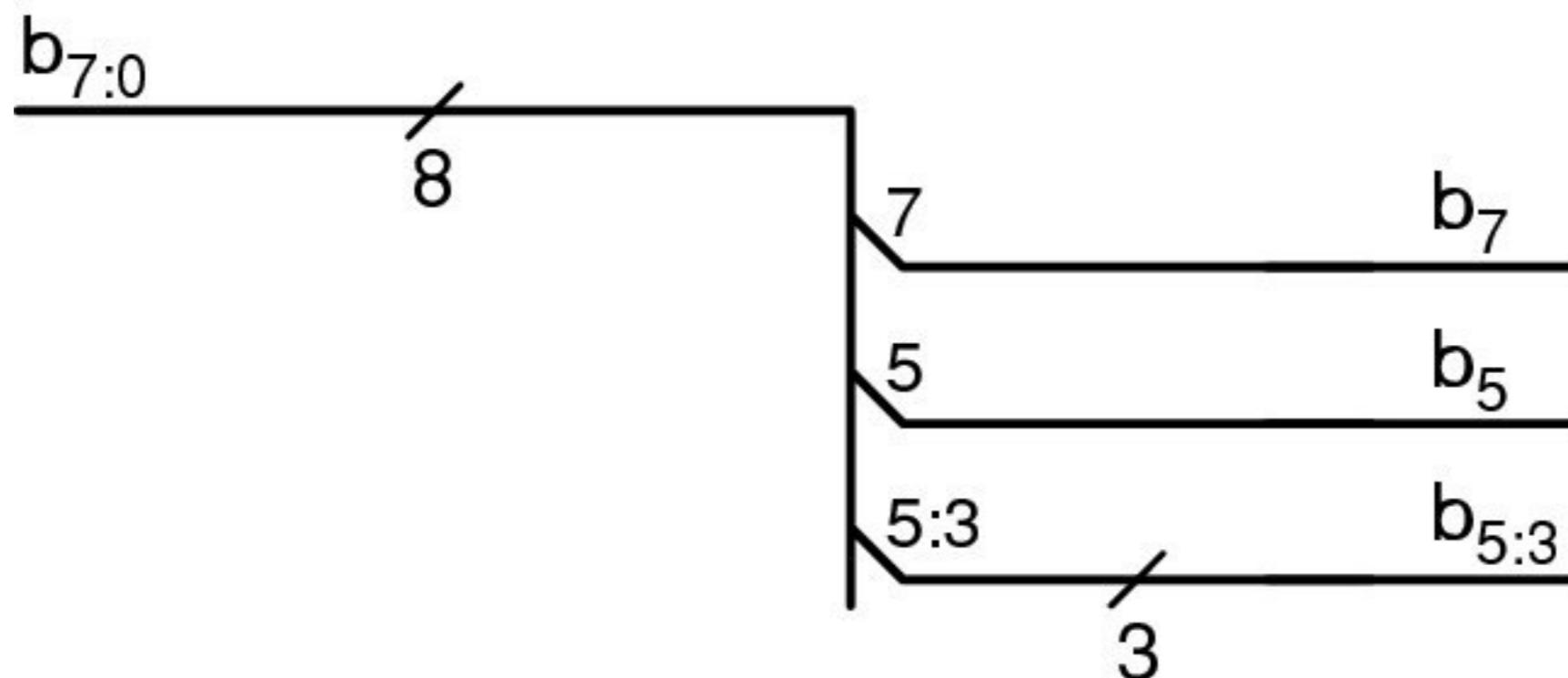

- Verilog bit-select (bit-slice) or part-select
 - $b[7:0]$
 - $b[7]$
 - $b[5:3]$

Ripple-Carry Adder (4/4)

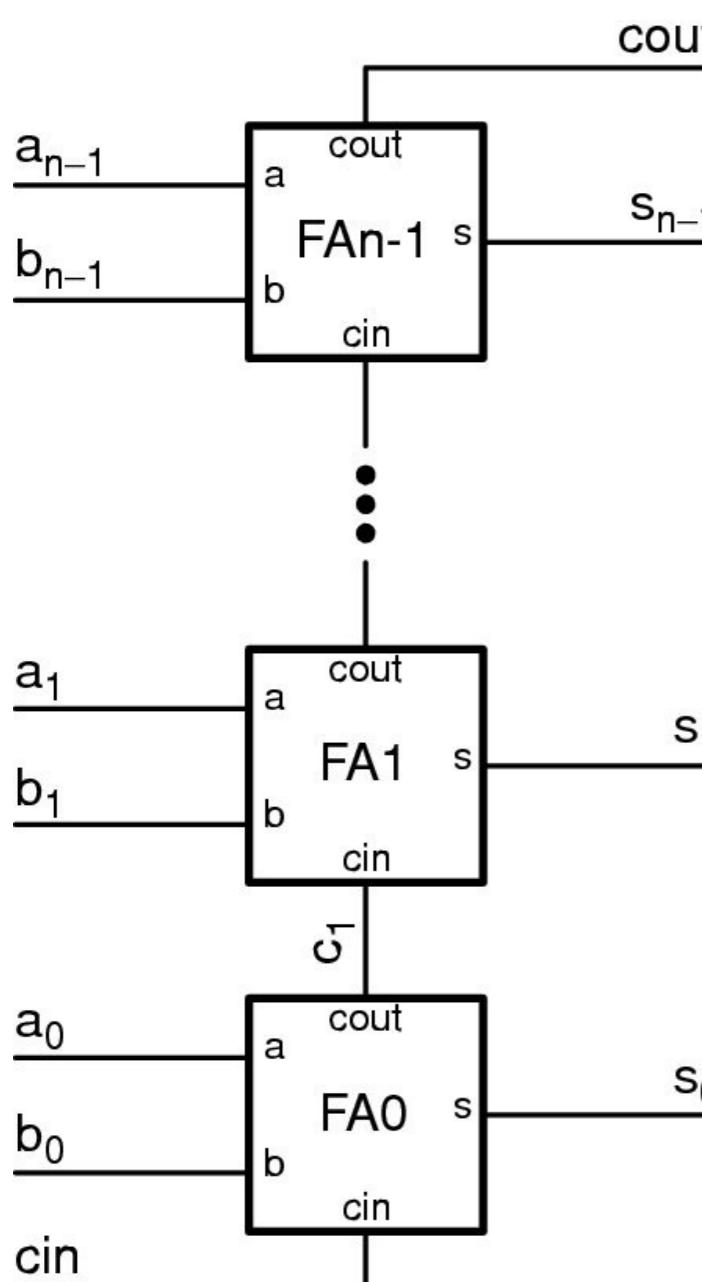

```

module adder(a, b, cin, cout, s);
parameter n=4;
input [n-1:0] a, b;
input cin;
output reg [n-1:0] s;
output cout;
reg [n:0] c;
integer i;

```

```

assign cout = c[n];
always @*
    c[0] = cin;
always @*
for (i=0;i<n;i=i+1)
    {c[i+1],s[i]} = a[i] + b[i] + c[i];

```

```


assign {c[1],s[0]} = a[0] + b[0] + c[0];
assign {c[2],s[1]} = a[1] + b[1] + c[1];
assign {c[3],s[2]} = a[2] + b[2] + c[2];
assign {c[4],s[3]} = a[3] + b[3] + c[3];

```



endmodule

Multi-bit Binary Adder

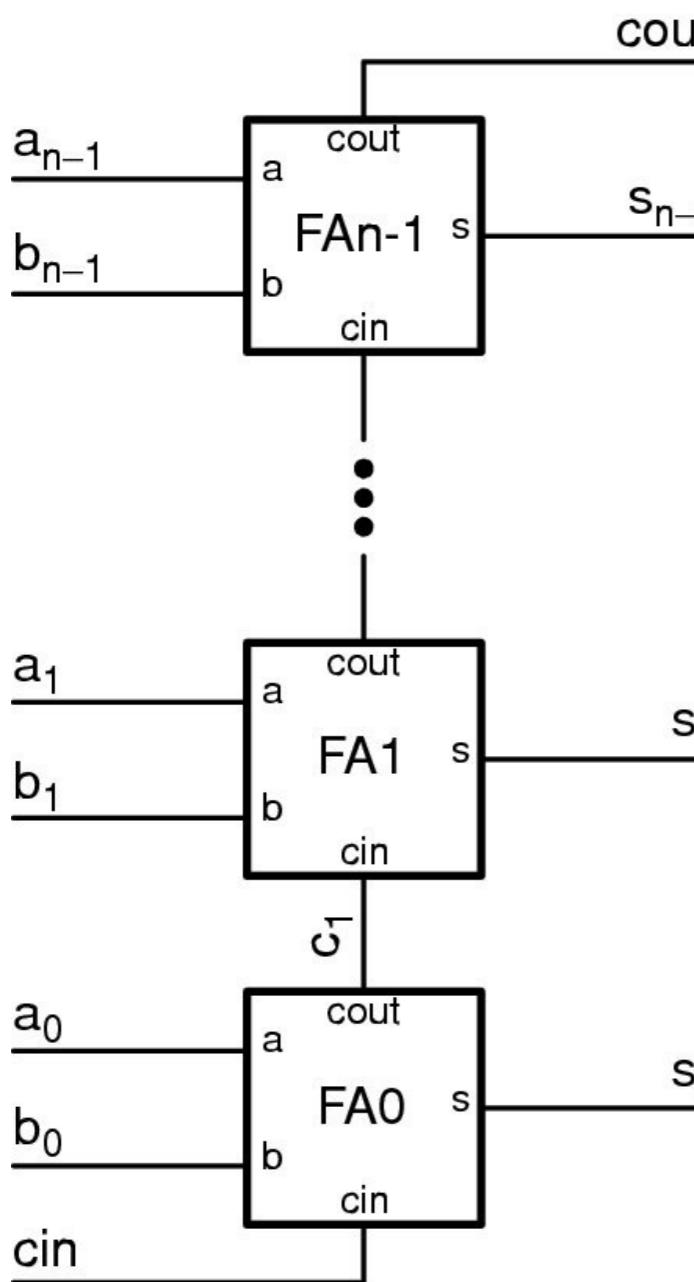

behavioral model

```
module Adder1(a, b, cin, cout, s);
parameter n=8;
input [n-1:0] a, b;
input cin;
output [n-1:0] s;
output cout;

assign {cout, s} = a + b + cin;

endmodule
```

Carry Lookahead Adder (1/3)

- For a full adder, define what happens to carry

1 – Carry-generate: $C_{out}=1$ independent of C_{in}

- $G_i = A_i \cdot B_i$

– Carry-propagate: $C_{out}=C_{in}$

- $P_i = A_i \oplus B_i$ (sometimes $A_i + B_i$)

– Carry-kill: $C_{out}=0$ independent of C_{in}

- $K_i = A'_i \cdot B'_i$

- Use the above info

- 3
- $C_{i+1} = A_i B_i + B_i C_i + A_i C_i = A_i B_i + (A_i + B_i) C_i = \underline{G_i + P_i C_i}$
 - $S_i = A_i \oplus B_i \oplus C_i = \underline{P_i \oplus C_i}$




A_i	B_i	G_i	P_i	K_i
0	0	0	0	1
0	1	0	1	0
1	0	0	1	0
1	1	1	0	0

Carry Lookahead Adder (2/3)

- Do not have to wait for C_i to compute C_{i+1}
 - $C_{i+1} = G_i + P_i C_i$
 - $C_{i+2} = G_{i+1} + P_{i+1} C_{i+1} = G_{i+1} + P_{i+1} G_i + P_{i+1} P_i C_i$
 - $C_{i+3} = G_{i+2} + P_{i+2} C_{i+2} = G_{i+2} + P_{i+2} G_{i+1} + P_{i+2} P_{i+1} G_i + P_{i+2} P_{i+1} P_i C_i$
- $C_{i+4} = G_{i+3} + P_{i+3} C_{i+3} = G_{i+3} + P_{i+3} G_{i+2} + P_{i+3} P_{i+2} G_{i+1} + P_{i+3} P_{i+2} P_{i+1} G_i + P_{i+3} P_{i+2} P_{i+1} P_i C_i$
- Fixed delay time for each carry (but not the same for every gate!)
- Fanout of G_i & P_i also affect the overall delay => usually be limited to 4 bits

Carry Lookahead Adder (3/3)

4

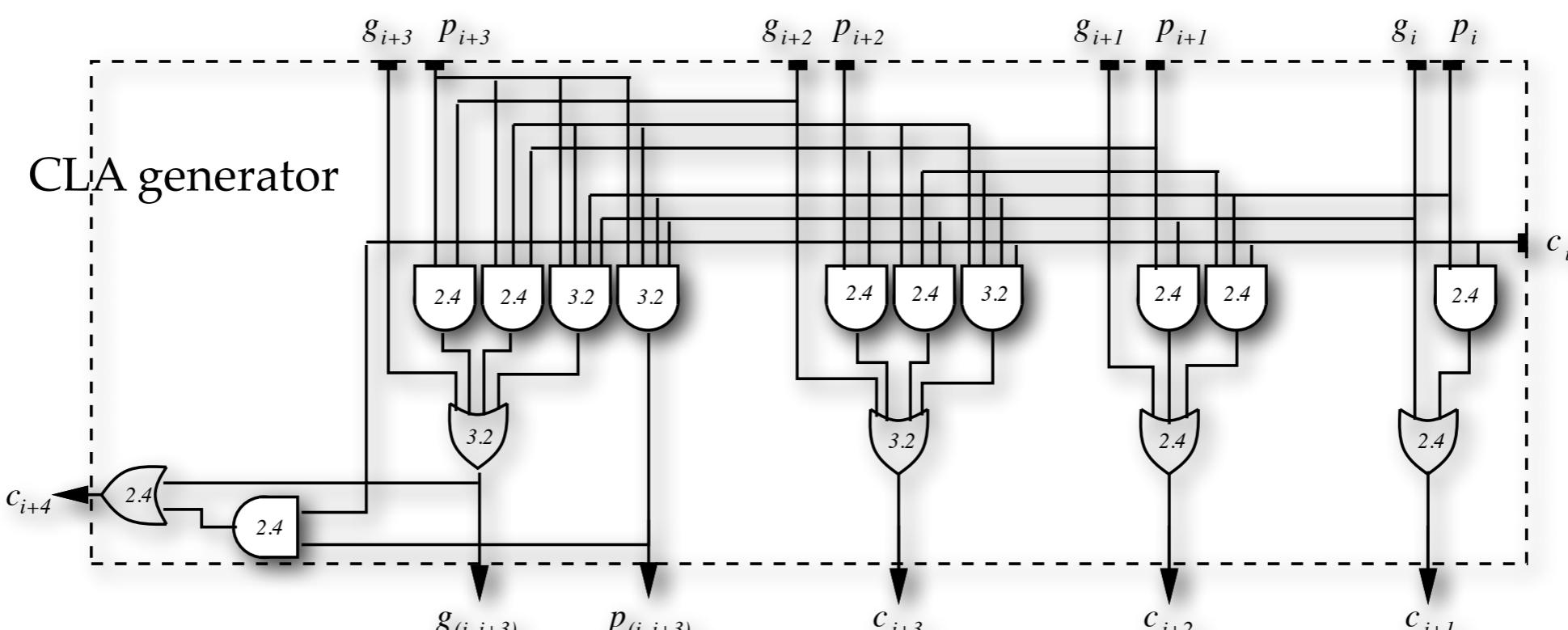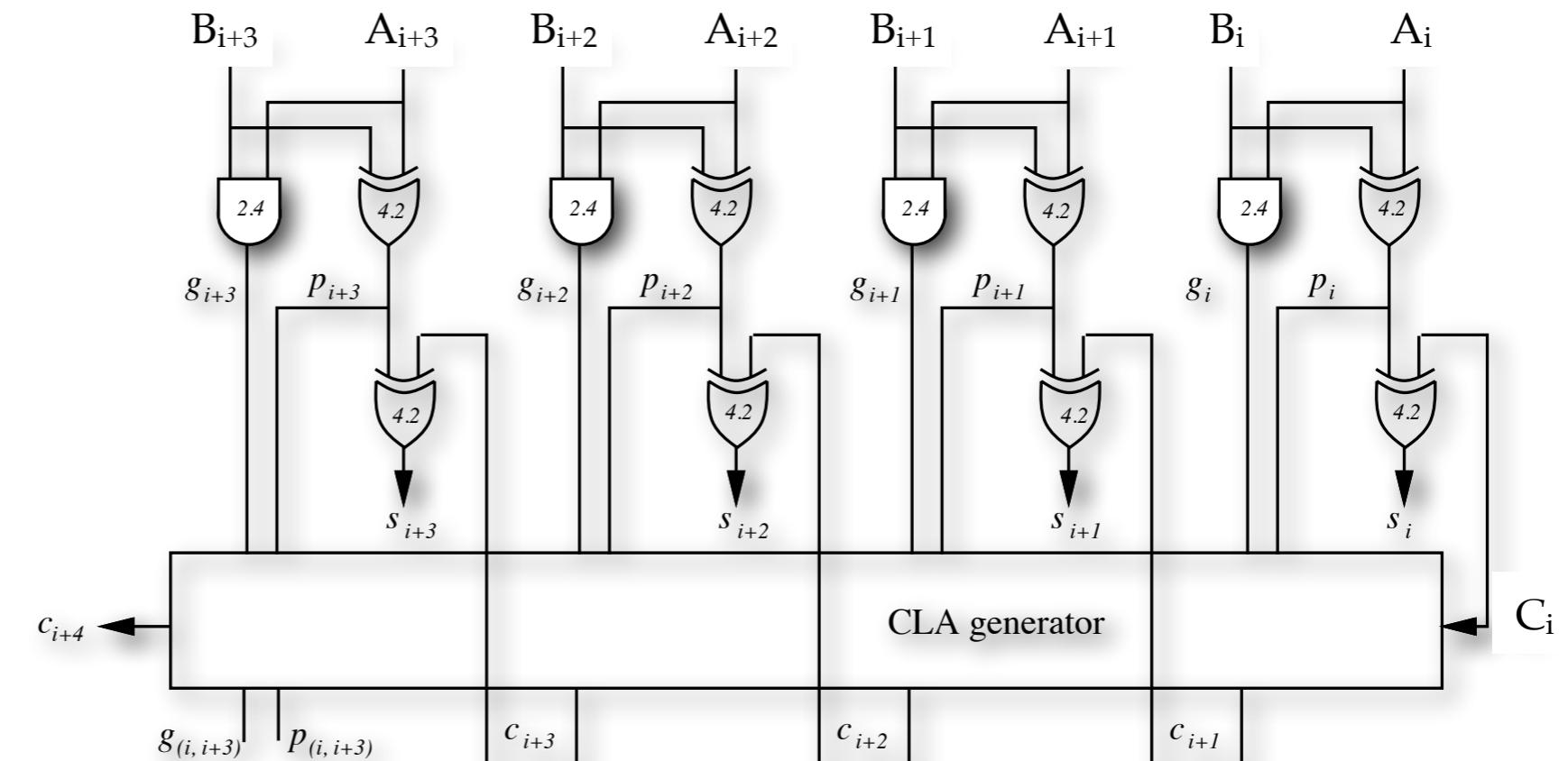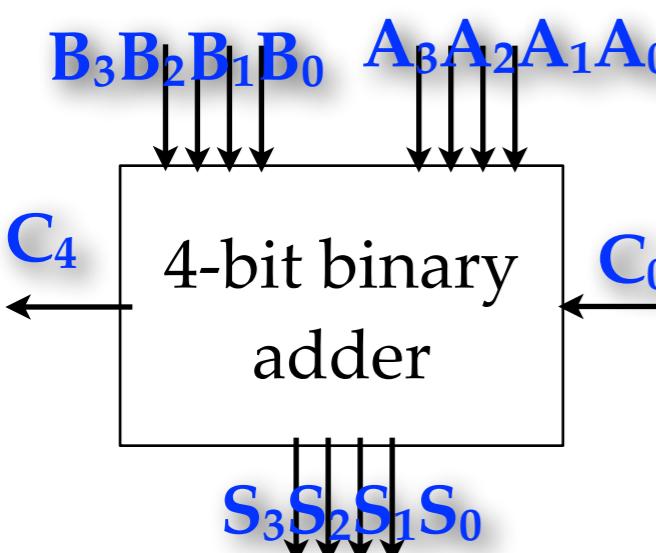




Binary Adders/Subtractors

- Binary subtraction normally is
 - 1 performed by adding the minuend to the 2's complement of the subtrahend.

M	Function	Comments
0	$S=A+B$	addition
1	$S=A+B'+1$	subtraction

2 3

overflow detection

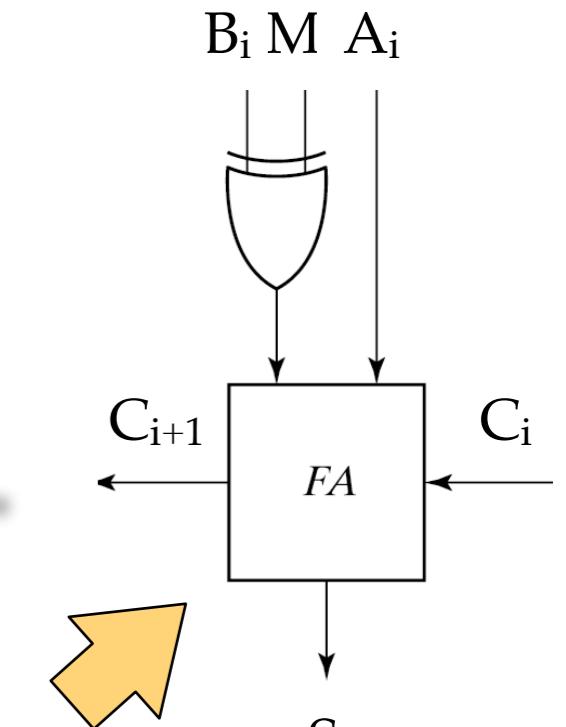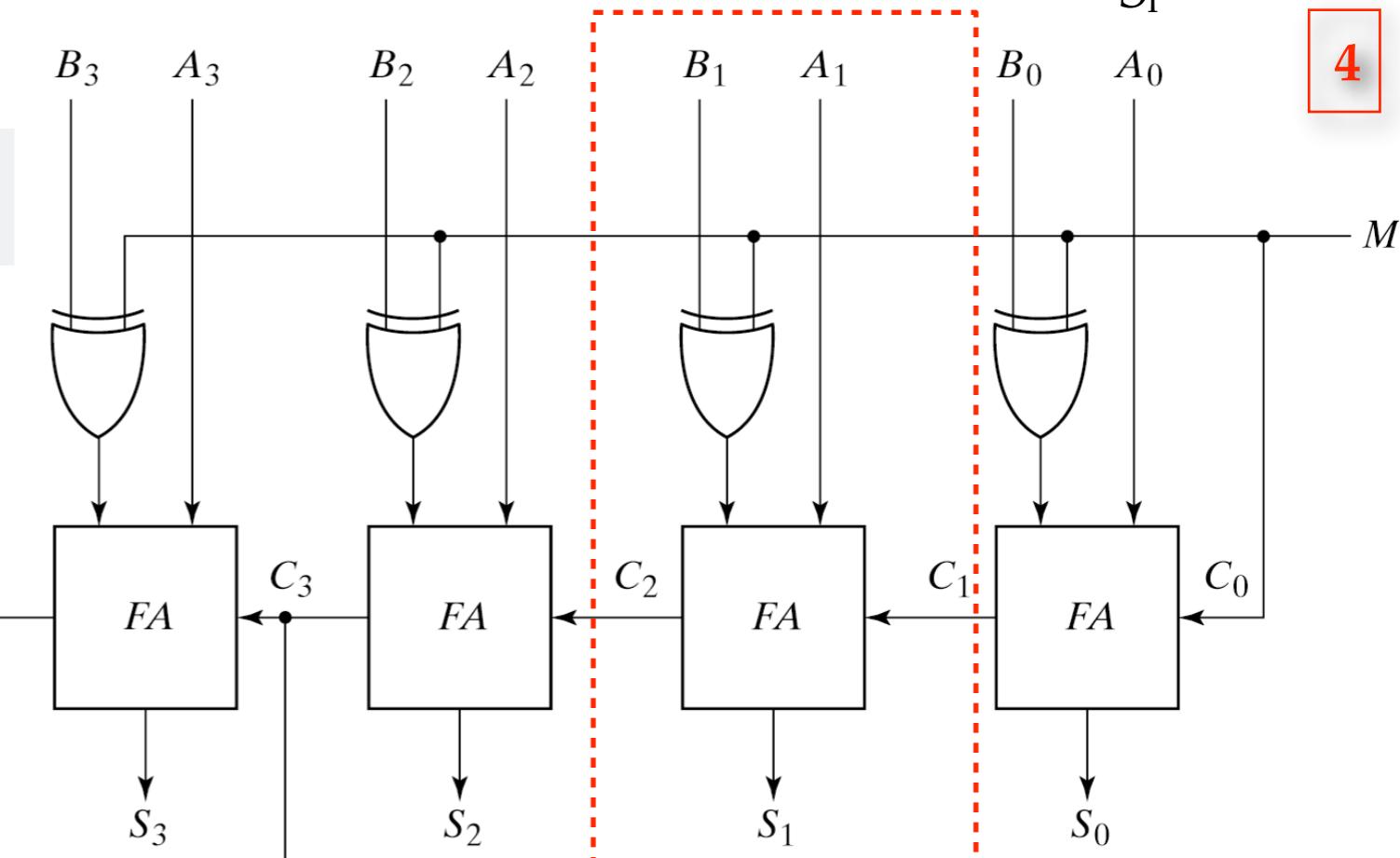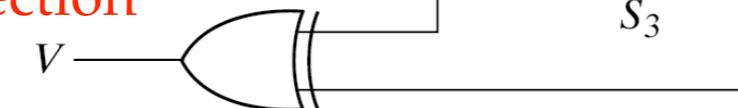

4

Decimal Adder

Decimal Adders (1/3)

- Addition of 2 decimal digits in BCD

$$- \{C_{out}, S\} = A + B + C_{in}$$

1 • $S = S_8 S_4 S_2 S_1$, $A = A_8 A_4 A_2 A_1$, $B = B_8 B_4 B_2 B_1$

- A digit in BCD cannot exceed 9, add 6 (0110) for final correction.

$$\begin{array}{r}
 & 10 \\
 & 8_{10} \text{ A} \\
 & 9_{10} \text{ B} \\
 \hline
 17_{10} \text{ KZ}
 \end{array}
 \quad
 \begin{array}{r}
 10000 \\
 1000_2 \\
 1001_2 \\
 \hline
 10001_2 \\
 \hline
 0110_2
 \end{array}$$

藍色為個位數 紅色為十位數

2 3


binary coded results
if >9 , add 6
BCD coded results

Decimal symbol	BCD digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001


Decimal Adders (2/3)

	Z_8	Z_4	Z_2	Z_1
2	0	0	0	0
3	0	0	0	1
	0	0	1	0
	0	0	1	1
	0	1	0	0
	0	1	0	1
	0	1	1	0
	0	1	1	1
	1	0	0	0
	1	0	0	1


Z₈Z₄ Z₈Z₂

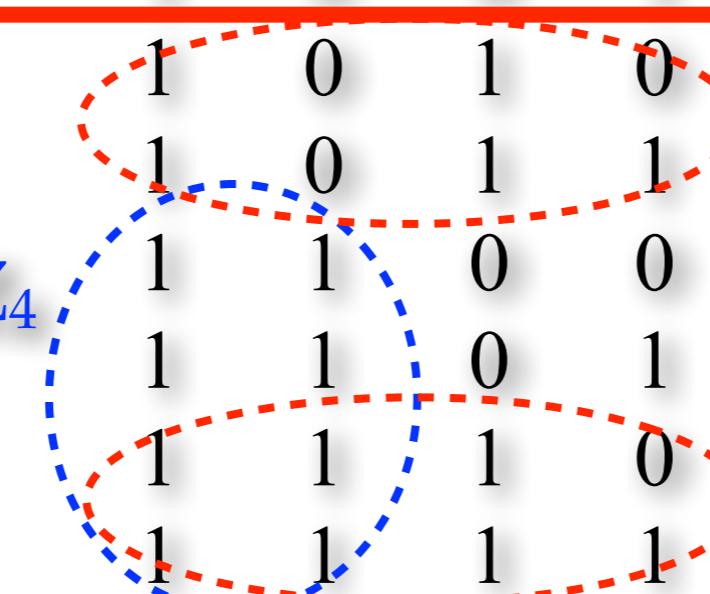

Decimal Adders (3/3)

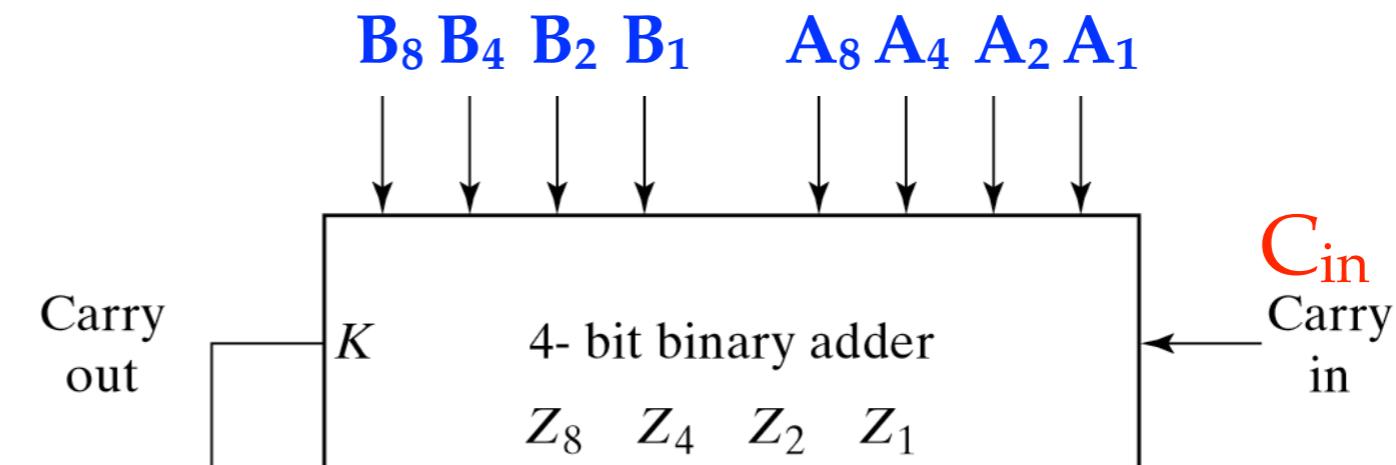

3 $C_{out} = K + Z_8Z_4 + Z_8Z_2$

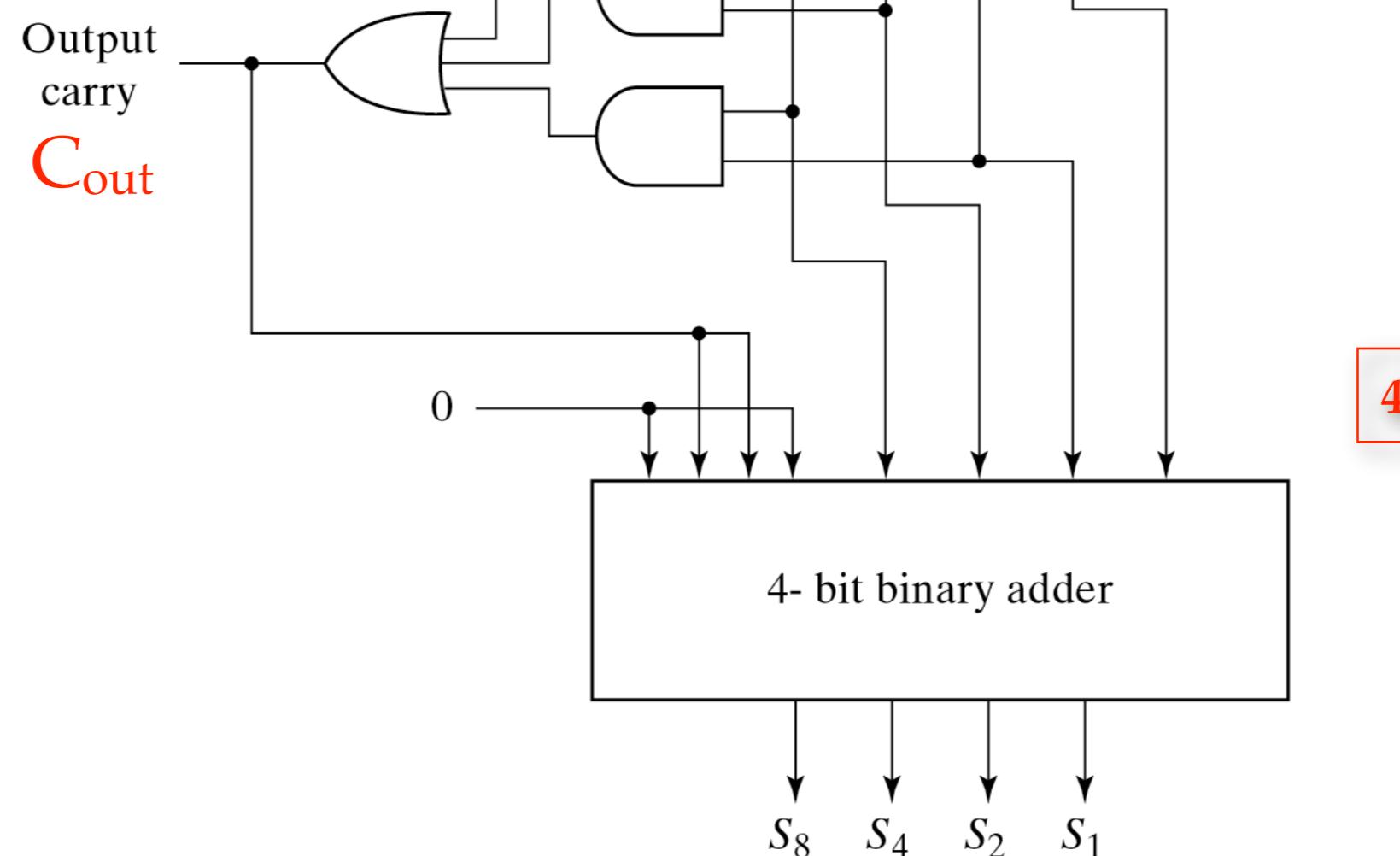

Binary Multiplier

Multiplication

- Multiplication consists of
 - Generation of partial products
 - Accumulation of shifted partial products

$$\begin{array}{r} 1100 \quad 12_{10} \quad \text{Multiplicand} \\ \times \quad 0101 \quad 5_{10} \quad \text{Multiplier} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 0111100 \quad 60_{10} \quad \text{Product} \end{array}$$

Binary multiplication equivalent to AND operation



Partial Product

M-bit x N-bit Multiplication

$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$



	y_5	y_4	y_3	y_2	y_1	y_0	Multiplicand
	x_5	x_4	x_3	x_2	x_1	x_0	Multiplier
	$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
	$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$	
	$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$	
	$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$	Partial Products
	$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$	
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$	
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4
p_3	p_2	p_1	p_0				Product

2-bit x 2-bit Binary Multiplier

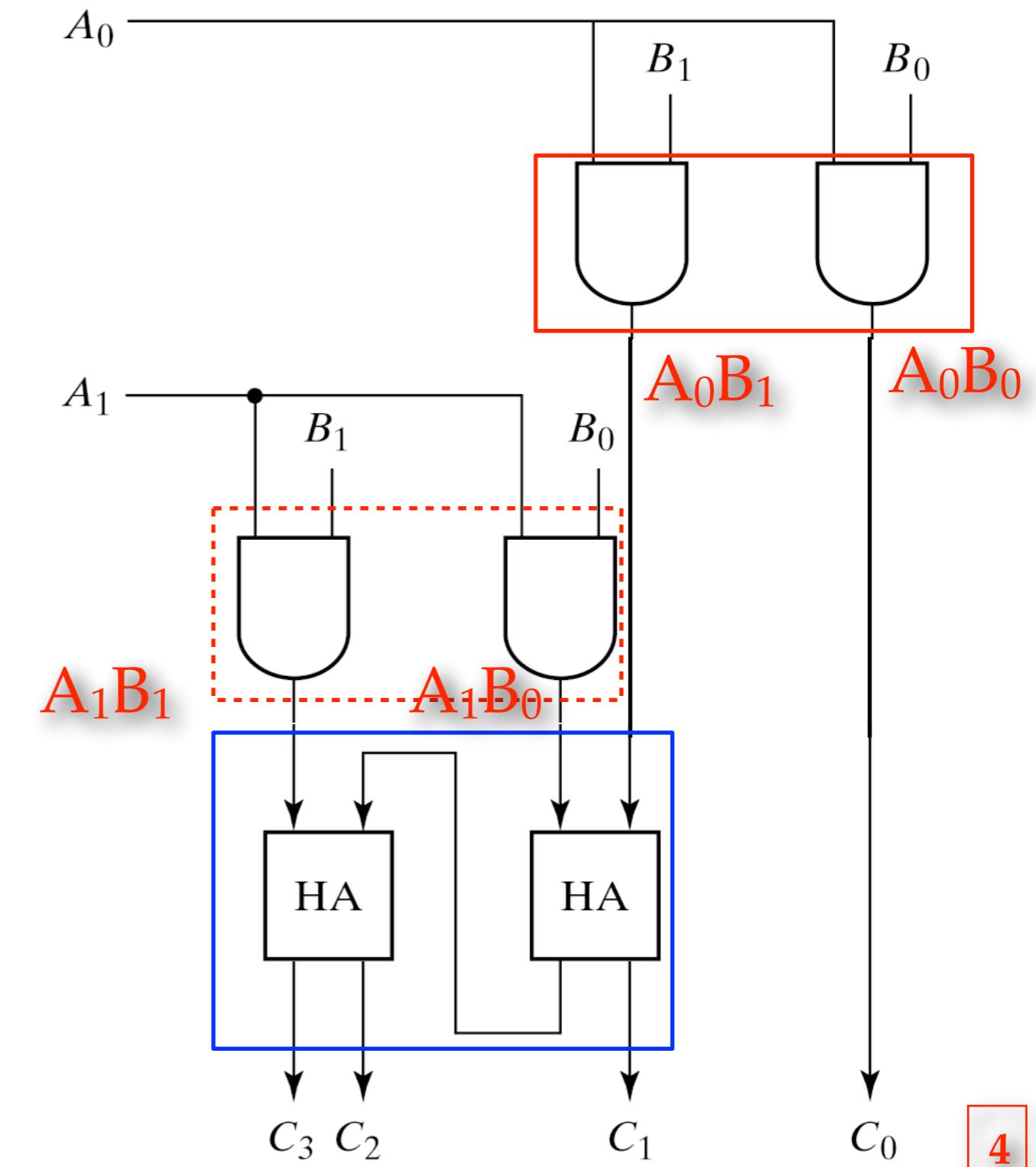
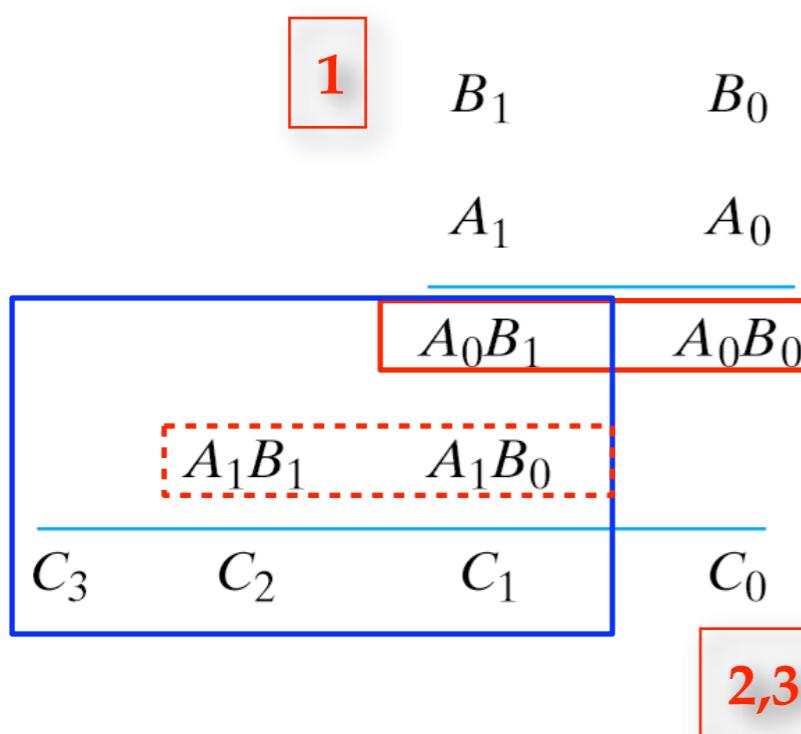


4

4-bit x 3-bit Binary Multiplier

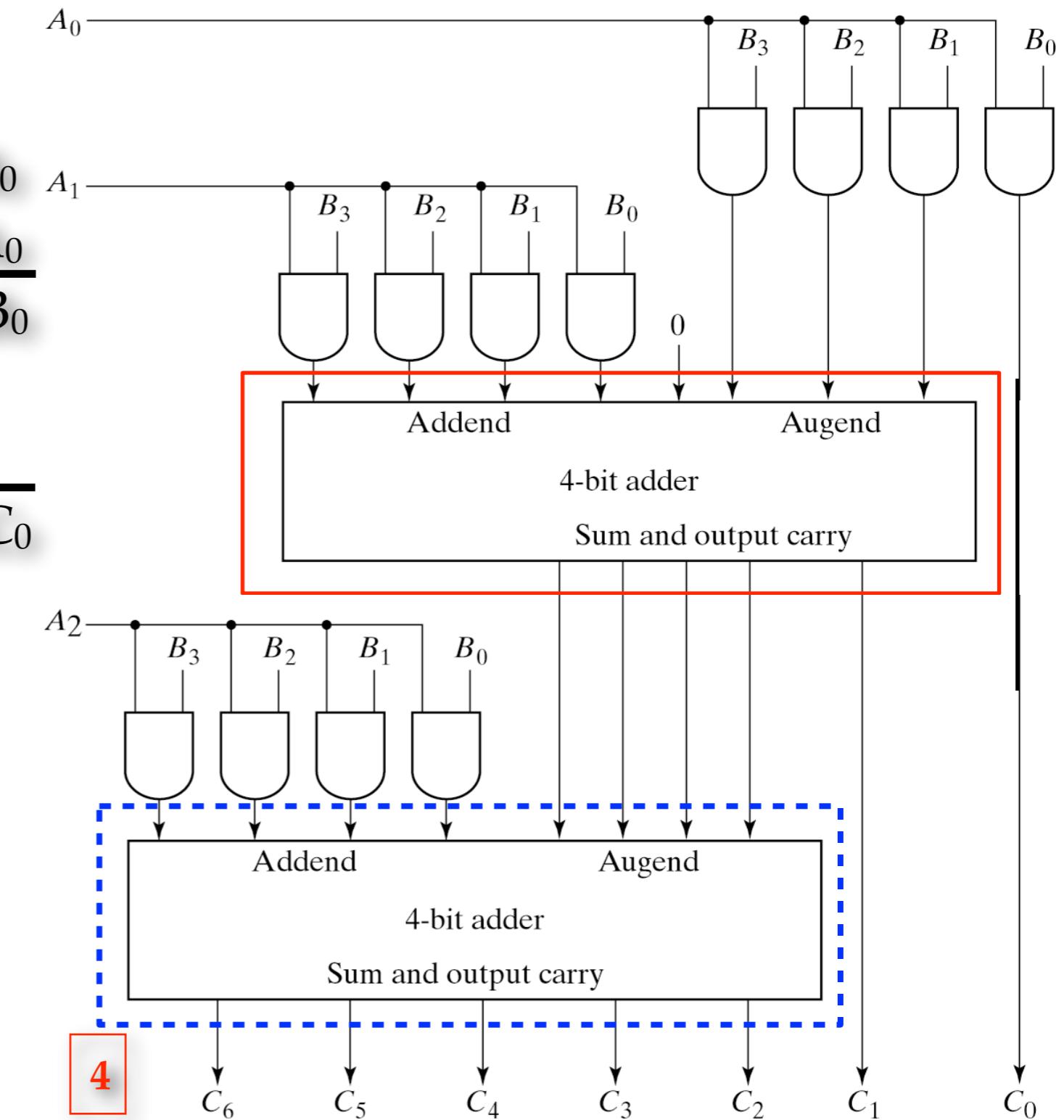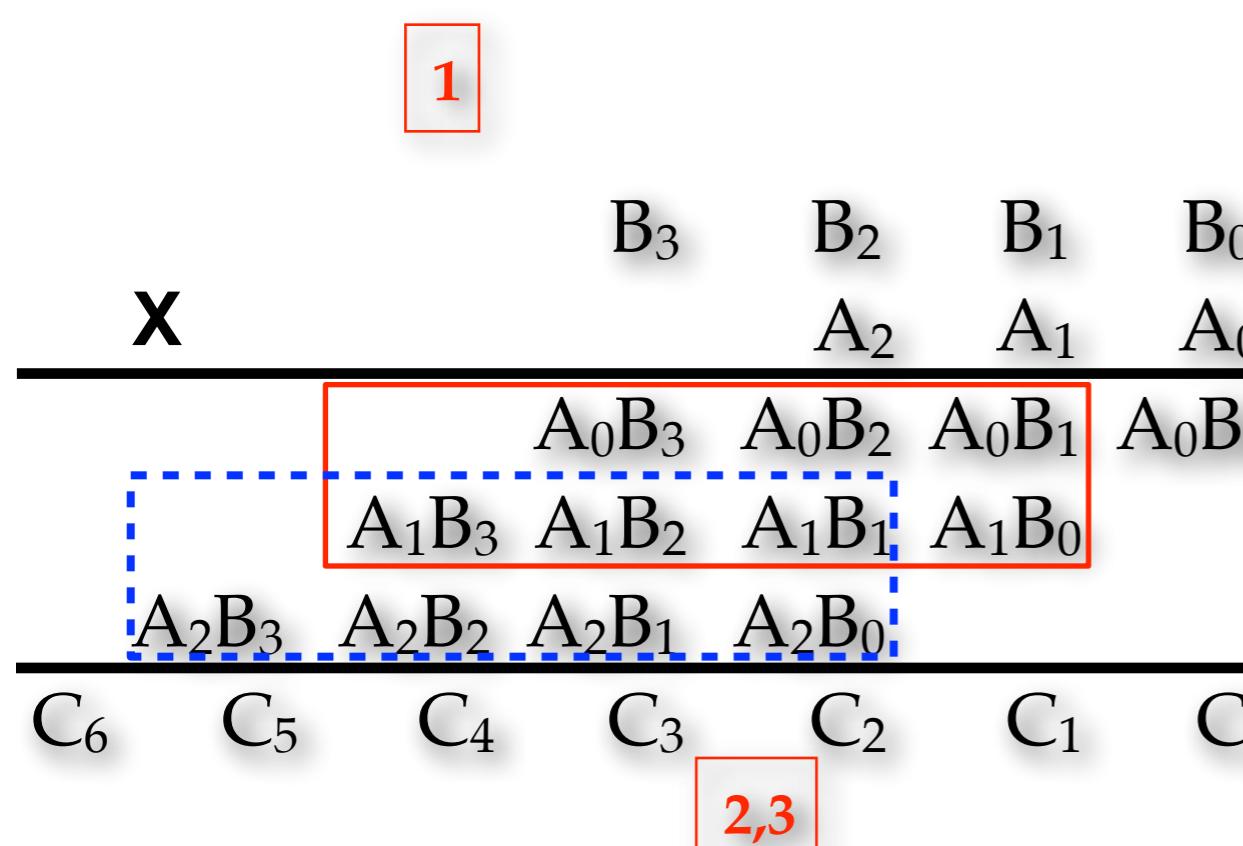

Array Multiplier

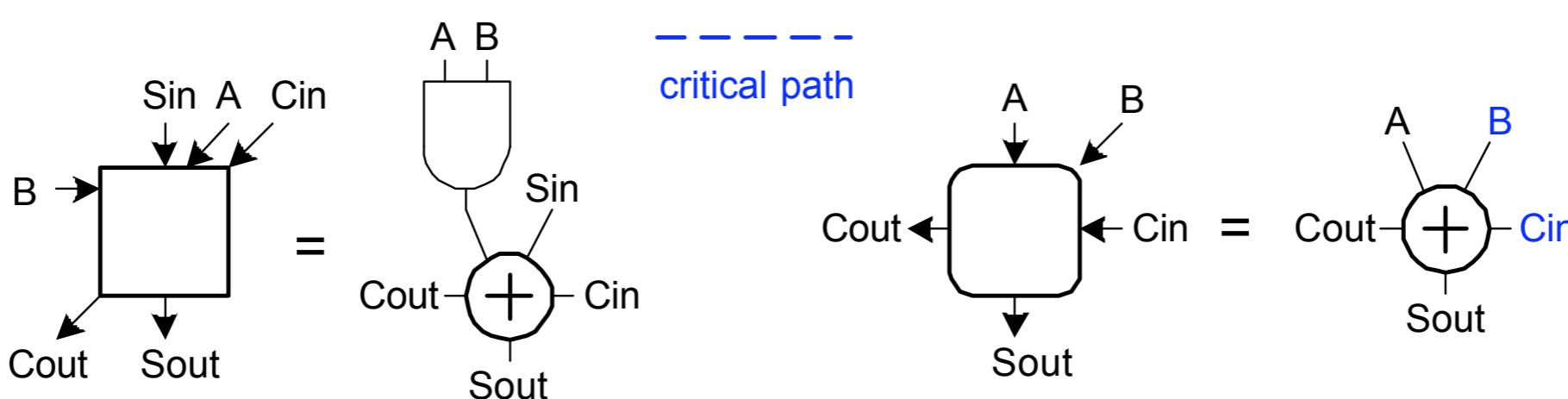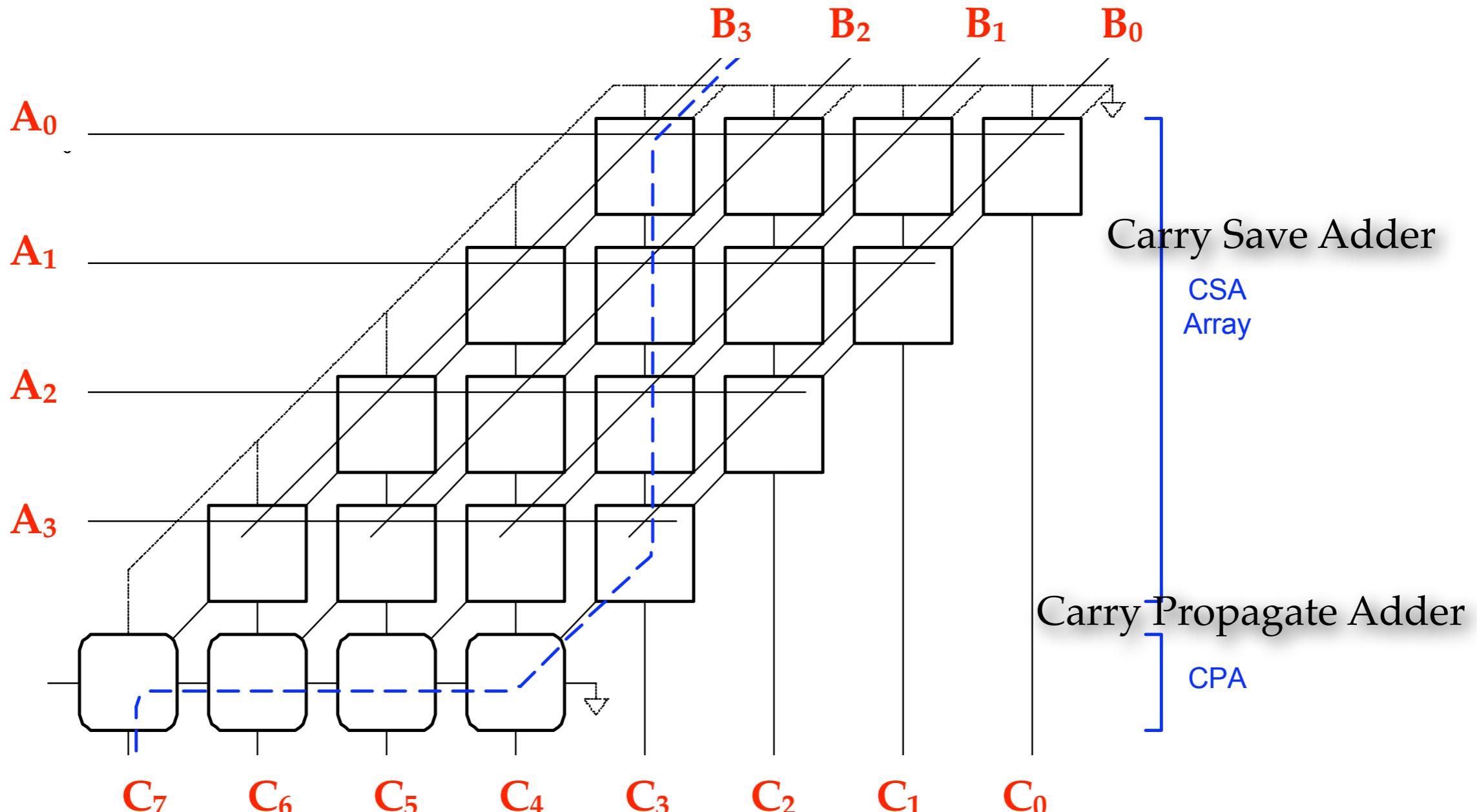

4-bit Array Multiplier

```
module mul4(a, b, p);
    input [3:0] a, b;
    output [7:0] p;

    // form partial products
    wire [3:0] pp0 = a & {4{b[0]} }; // x1 weighting
    wire [3:0] pp1 = a & {4{b[1]} }; // x2 weighting
    wire [3:0] pp2 = a & {4{b[2]} }; // x4 weighting
    wire [3:0] pp3 = a & {4{b[3]} }; // x8 weighting

    // sum up partial products
    wire cout1, cout2, cout3;
    wire [3:0] s1, s2, s3;
    Adder1 #(4) a1(pp1, {0,pp0[3:1]}, 1'b0, cout1, s1);
    Adder1 #(4) a2(pp2, {cout1,s1[3:1]}, 1'b0, cout2, s2);
    Adder1 #(4) a3(pp3, {cout2,s2[3:1]}, 1'b0, cout3, s3);

    // collect the result
    wire [7:0] p = {cout3, s3, s2[0], s1[0], pp0[0]};

endmodule
```

4-bit Array Multiplier Testbench

```
module test3;  
reg [3:0] in0, in1;  
wire [7:0] out;  
  
Mul4 mul(.a(in0),.b(in1),.p(out));  
  
initial  
begin  
in0=4'b0;  
repeat (16)  
begin  
in1=4'b0;  
repeat (in0+1)  
begin  
#100 $display("%03d * %03d = %03d", in0, in1, out);  
in1=in1 + 1;  
end  
in0 = in0 + 1 ;  
end  
end  
  
endmodule
```

Other Arithmetic Functions


- It is convenient to design the functional blocks by *contraction*
 - Removal of redundancy from circuit to which input fixing has been applied
- Functions
 - Increment
 - Decrement
 - Multiplication by constant
 - Division by constant
 - Zero fill and extension

Design by Contraction


- Simplify the logic in a functional block to implement a different function
 - The new function must be realizable from the original function by applying rudimentary functions to its inputs
 - Contraction is treated here only for application of 0s and 1s (not for X and X').
 - After application of 0s and 1s, equations or the logic diagram are simplified

Design by Contraction Example

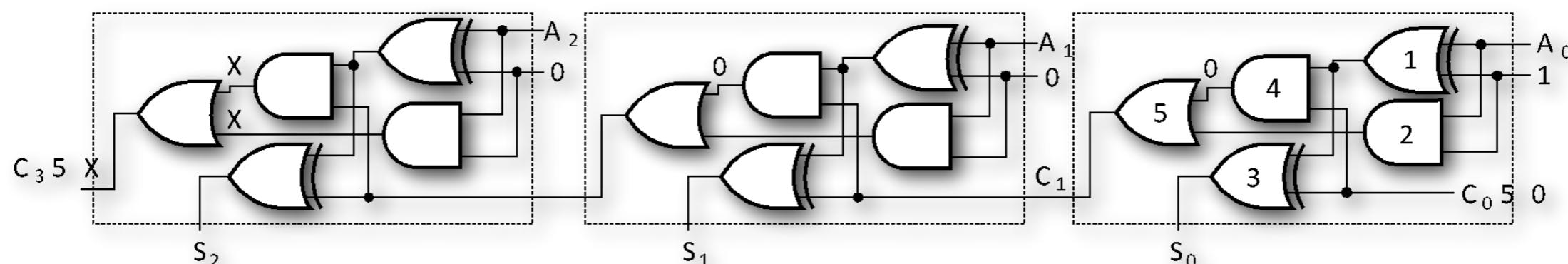- Contraction of a ripple carry adder to incrementer for n=1 (Set B=001)



(a)

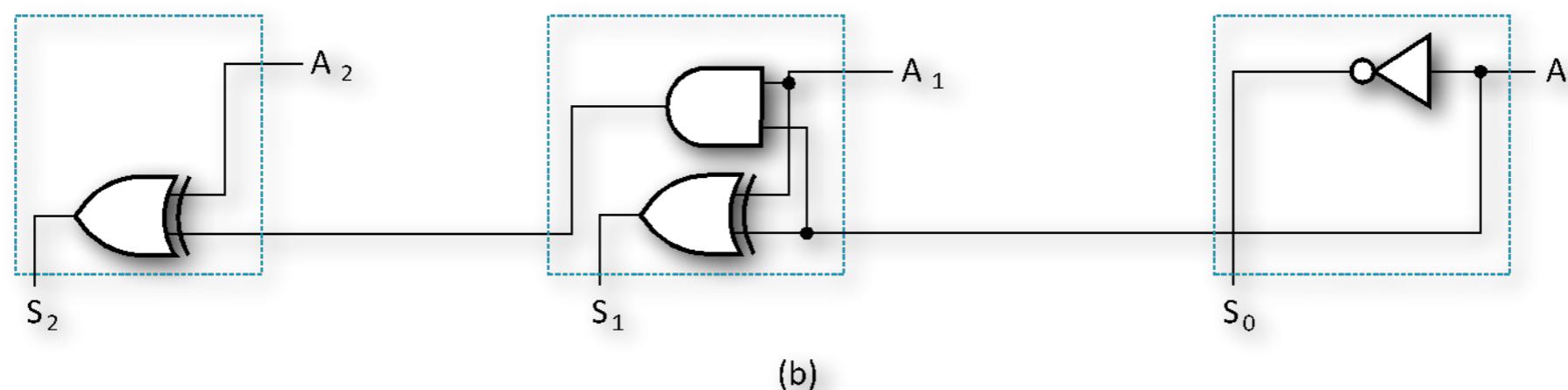

(b)

Incrementing and Decrementing

• Incrementing



- Ass a fixed value to an arithmetic variable
- Fixed value is often 1, called counting up
 - A+1, B+4
- Functional block is called incrementer

• Decrementing


- Subtracting a fixed value from an arithmetic variable
- Fixed value is often 1, called counting down
 - A-1, B-4
- Functional block is called decrementer

Multiplication/Division by 2^n

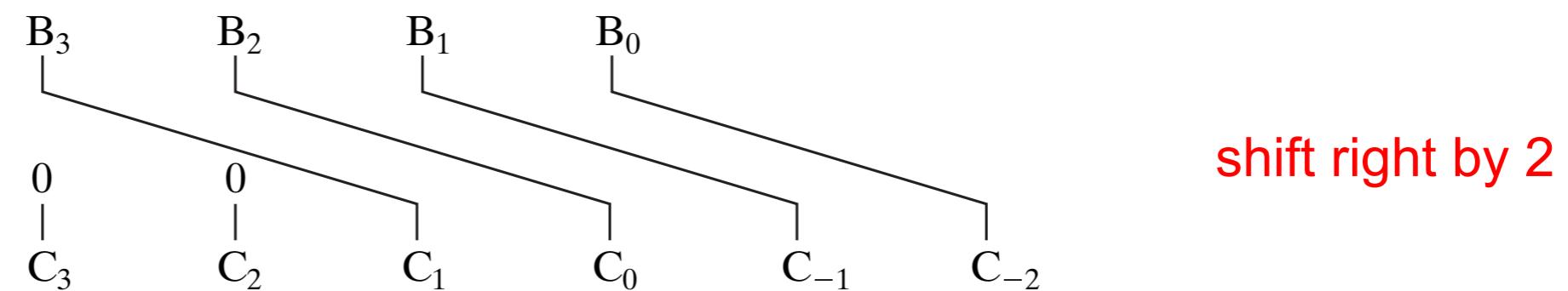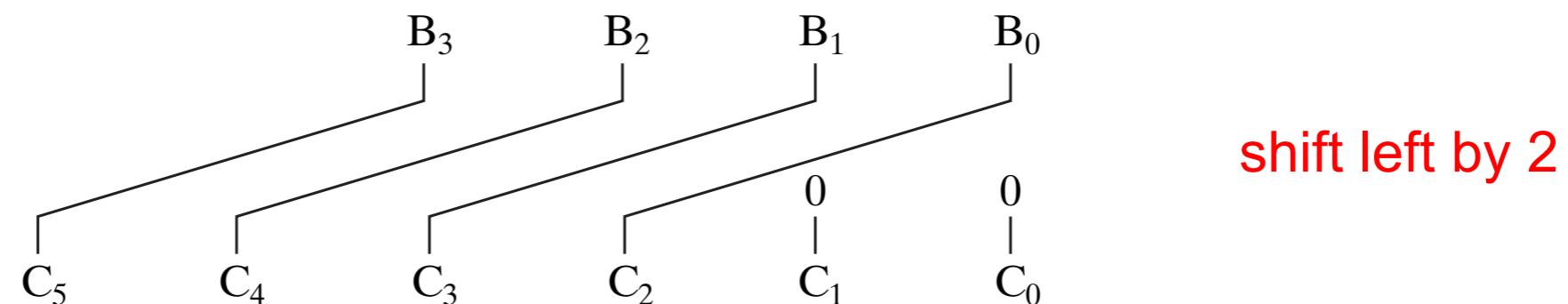- Shift left (multiplication) or right (division)



Multiplication by a Constant

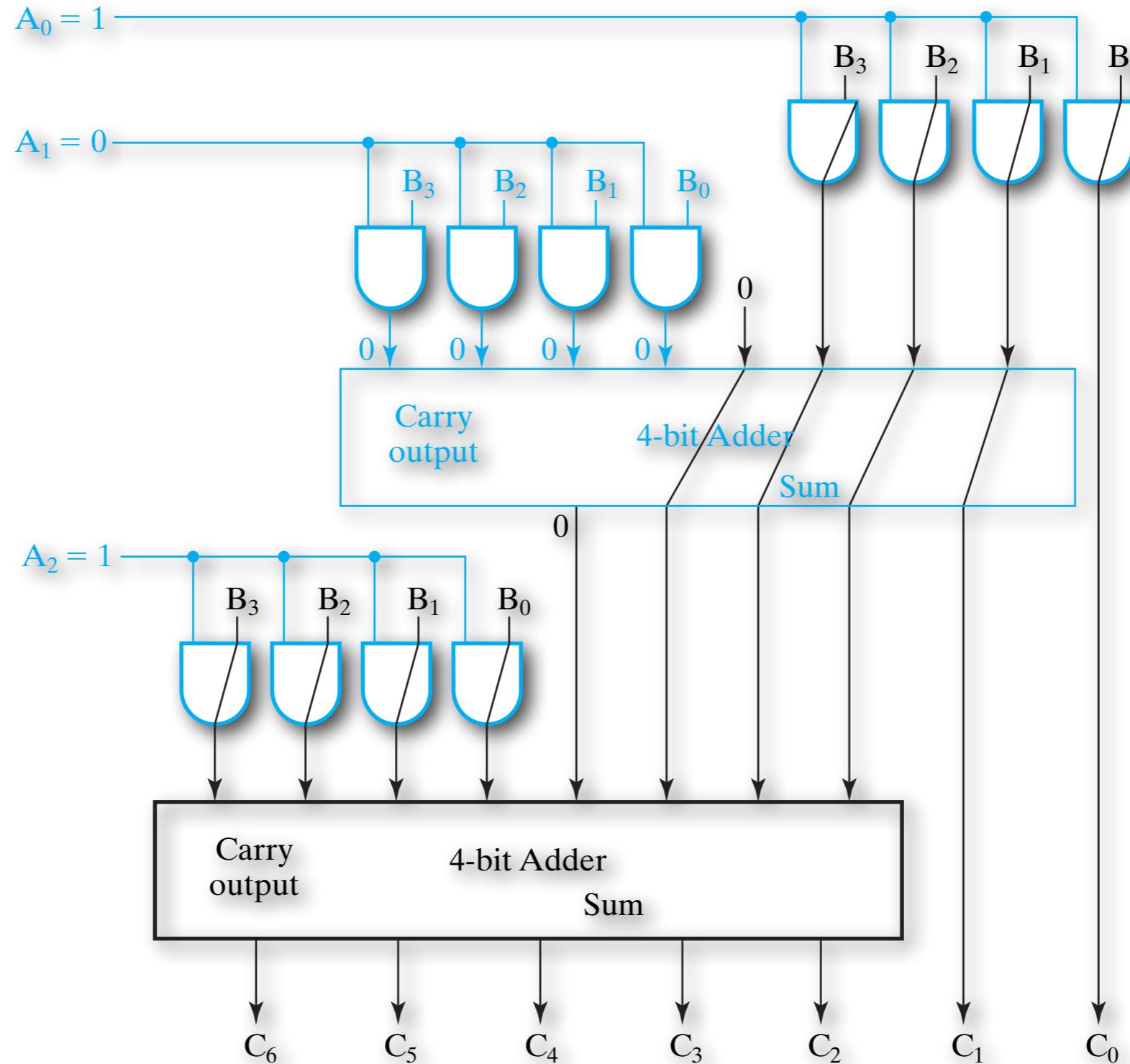

Zero Fill

- Fill an m -bit operand with 0s to become an n -bit operand with $n > m$.
- Filling usually is applied to the MSB end of the operand, but can also be done on the LSB end.
- 11110101 filled to 16 bits
 - MSB end: 0000000011110101 $\quad \{\{8\{0\}\}11110101\}$
 - LSB end: 1111010100000000 $\quad \{11110101\{8\{0\}\}\}$

Extension

- Increase in the number of bits at the MSB end of an operand by using a complement representation
 - Copies the MSB of the operand into the new positions
 - 01110101 extended to 16 bits
 - **0000000001110101** $\{{\color{red}8\{a_7\}}\}a_71110101\}$
 - 11110101 extended to 16 bits
 - **1111111111110101**

Magnitude Comparator

A 4-bit Equality Comparator

- Spec 1




- input A(3:0), B(3:0); output E (1/0 for equal/unequal)

- Formulation 2

- Bypass the truth table approach due to its size (8 inputs)
- By algorithm to build a regular circuit
 - $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$
 - $A == B$, if $(A_3 == B_3) \text{ AND } (A_2 == B_2) \text{ AND } (A_1 == B_1) \text{ AND } (A_0 == B_0)$
 - bit equality $x_i = A_iB_i + A_i'B_i'$, $(A == B) = x_3x_2x_1x_0$

A 4-bit Equality Comparator

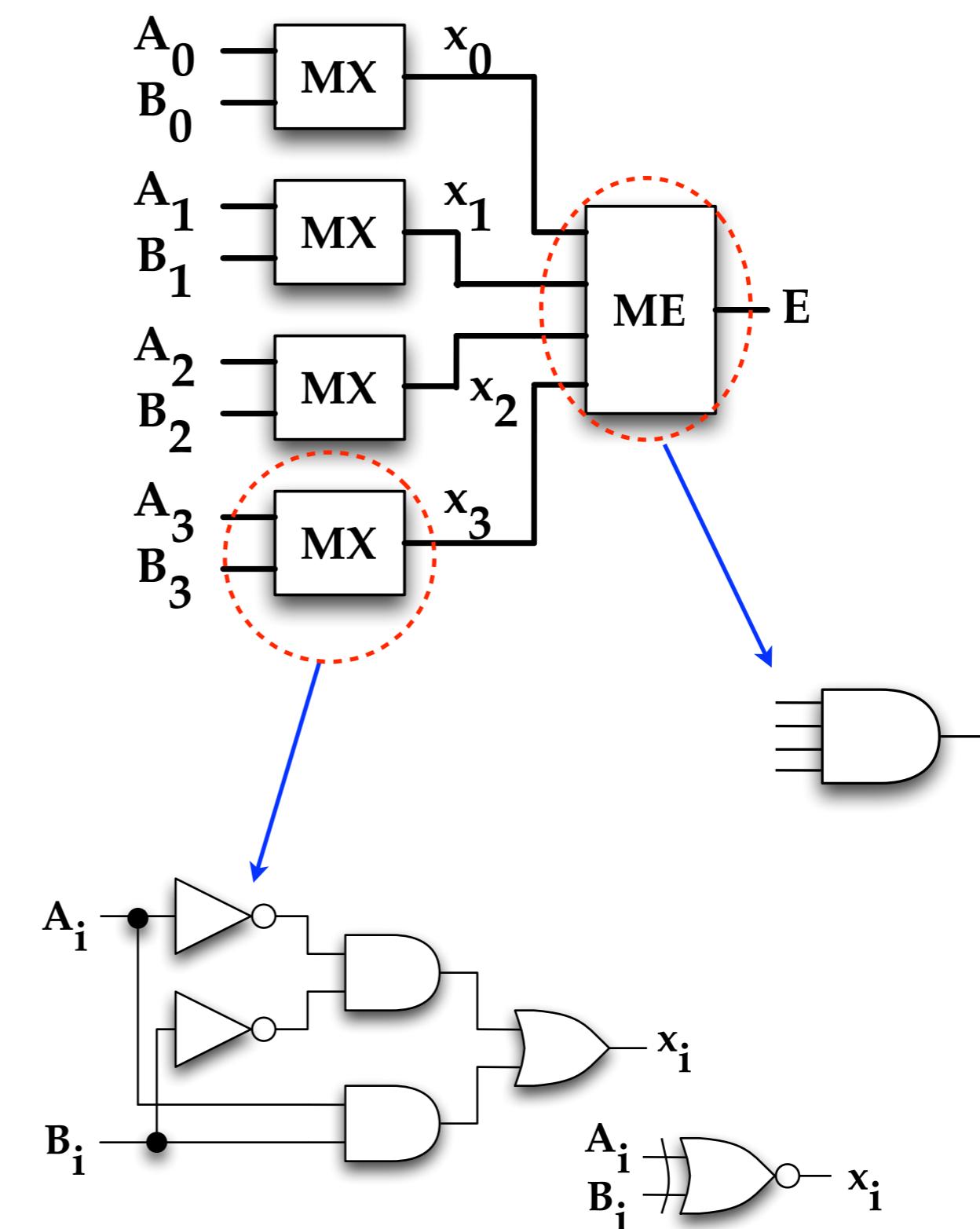- Optimization
 - Regularity 3
 - Reuse 4




Magnitude Comparator



- Comparison of two numbers, three possible results (A>B, A=B, A<B)
- Design approaches (for n -bit numbers)
 - By truth table: 2^{2n} rows => not practicable 2 x
 - By algorithm to build a regular circuit
 - 3 • $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$
 - $A == B$, if $(A_3 == B_3) \text{ AND } (A_2 == B_2) \text{ AND } (A_1 == B_1) \text{ AND } (A_0 == B_0)$
 - equality $x_i = A_iB_i + A_i'B_i'$, $(A=B) = x_3x_2x_1x_0$
 - $(A > B) = A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
 - $(A < B) = A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$

Magnitude Comparator

4

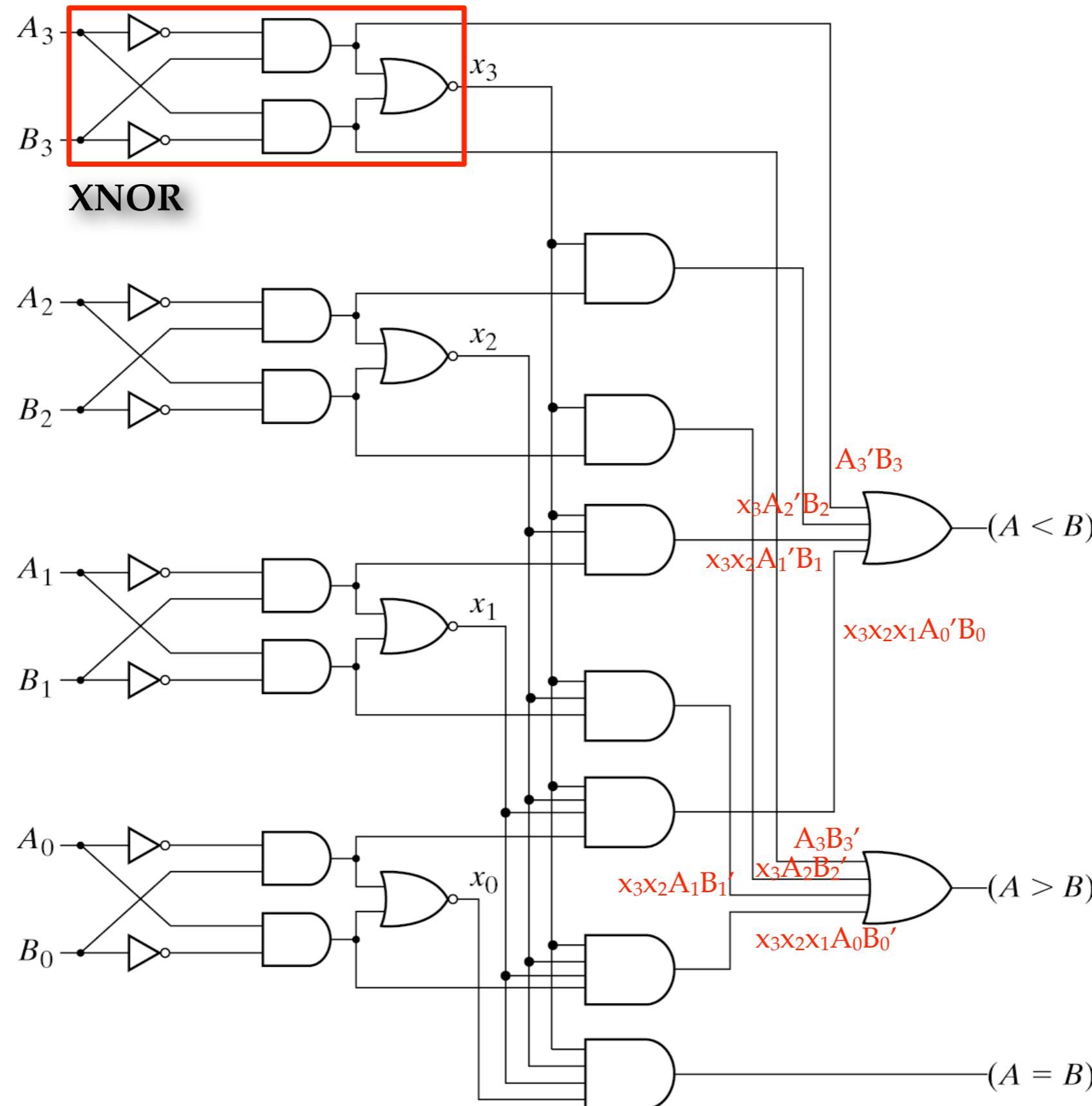

Equality Comparator

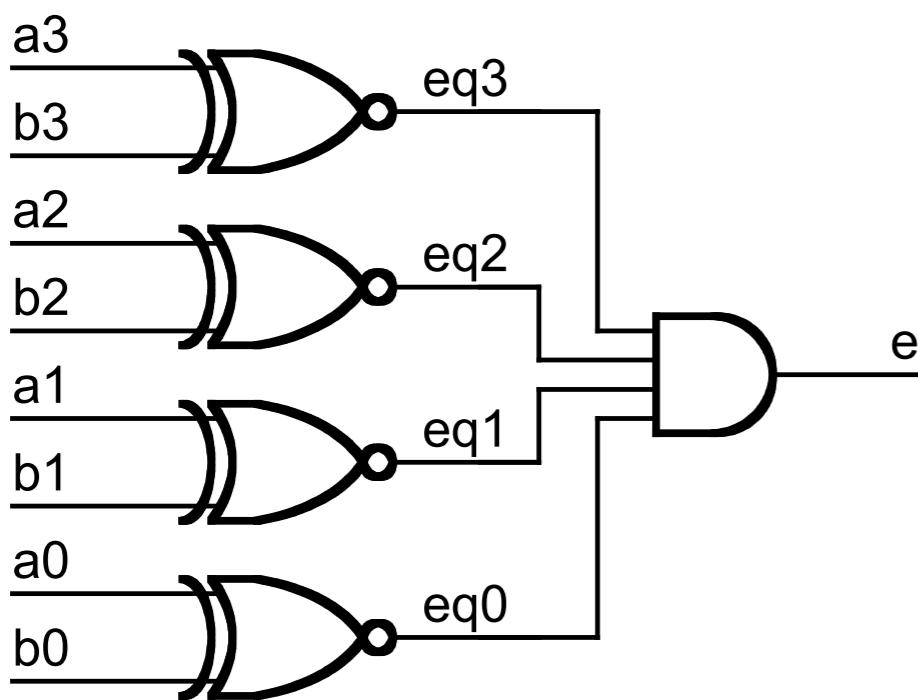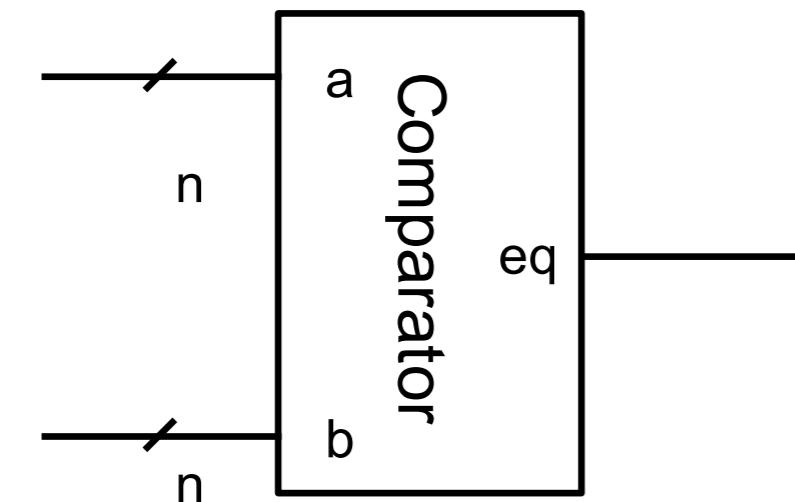

```
module EqComp(a, b, eq);
```

```
parameter k=8;
```

```
input [k-1:0] a, b;
```


```
output eq;
```

```
assign eq = (a == b); // eq = &(a~^b);
```

```
endmodule
```

Maximum Unit

$$y = \max\{a, b\}$$

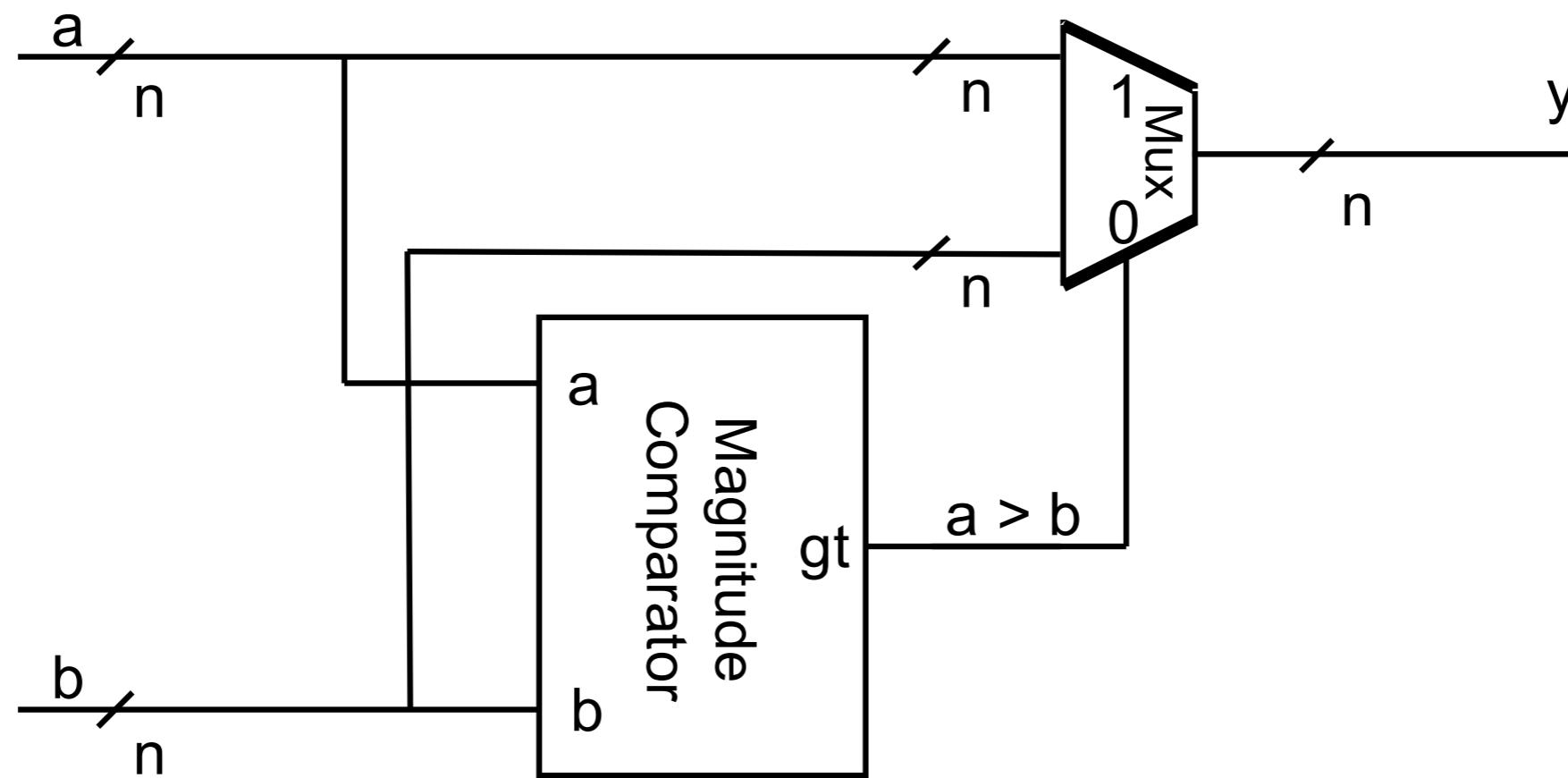

Magnitude Comparator

```
module MagComp_b(a, b, gt);
parameter k=8;
input [k-1:0] a, b;
output gt;

assign gt = (a > b) ? 1 : 0;

endmodule
```

Decoders

One-hot Representation


- Represent a set of N elements with N bits
- Exactly one bit is set

Binary	One-hot
000	00000001
001	00000010
010	00000100
011	00001000
100	00010000
101	00100000
110	01000000
111	10000000

Decoder

- A decoder is a combinational circuit that converts binary information from n input lines to m (maximum of 2^n) *unique* output lines

– n -to- m -line decoder

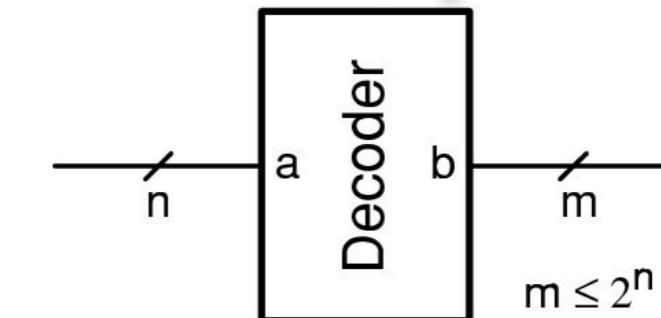

- A binary one-hot decoder converts a symbol from binary code to a one-hot code


– Output variables are *mutually exclusive* because only one output can be equal to 1 at any time (the very 1-minterm)

– Example


- binary input a to one-hot output b

$$b[i] = 1 \text{ if } a = i \quad \text{or} \quad b = 1 \ll a$$

1-to-2-Line Decoder

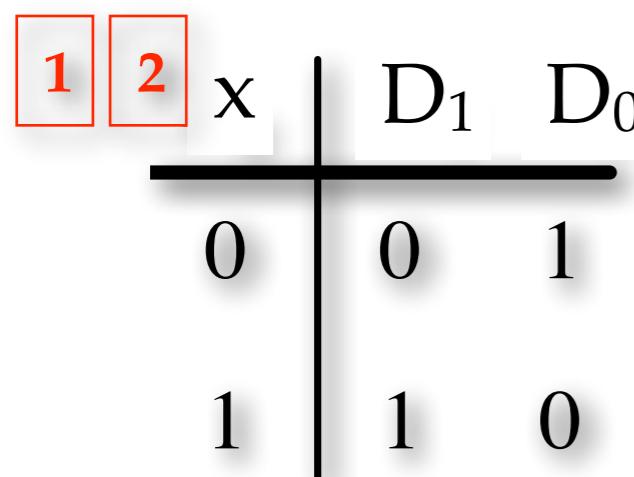

3 D₀=x'
 D₁=x

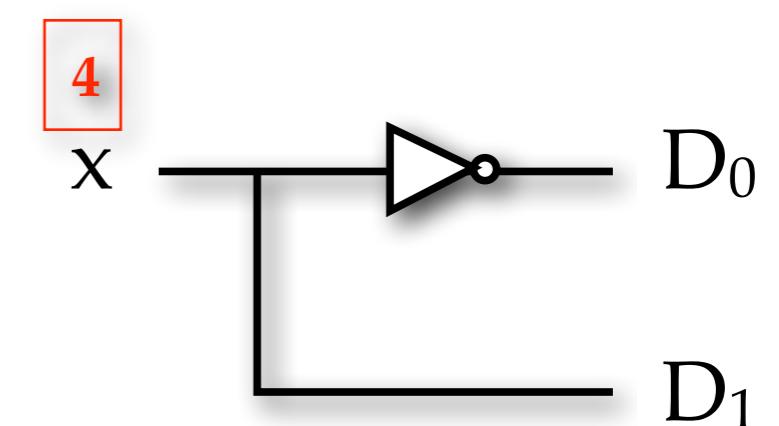

2-to-4-Line Decoder

1	2	a ₁	a ₀	b ₃	b ₂	b ₁	b ₀
0	0	0	0	0	0	1	
0	1	0	0	0	1	0	
1	0	0	1	0	0	0	
1	1	1	0	0	0	0	


3

$$b_3 = a_1 a_0$$

$$b_2 = a_1 a'_0$$


$$b_1 = a'_1 a_0$$

$$b_0 = a'_1 a'_0$$

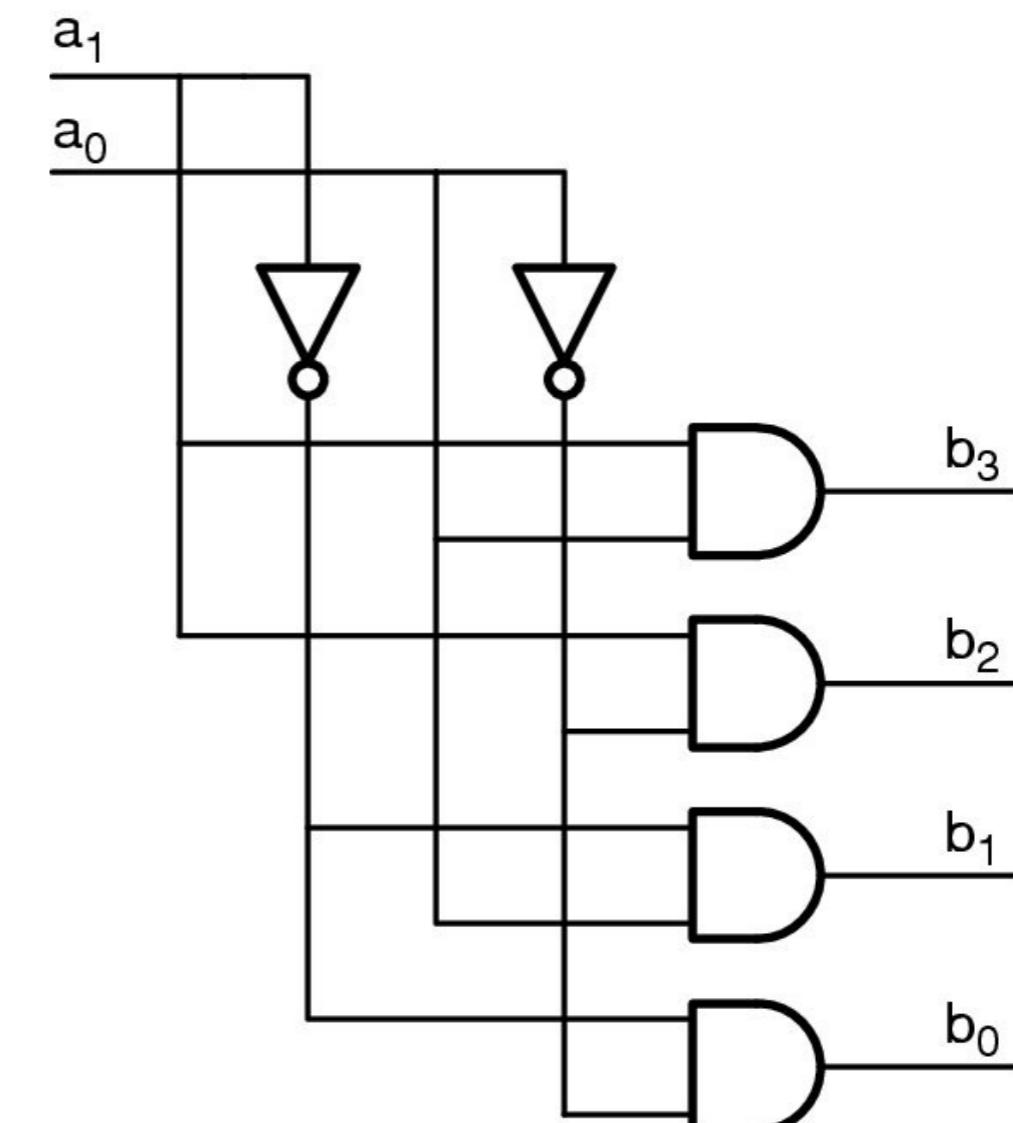

3-to-8-Line Decoder

3

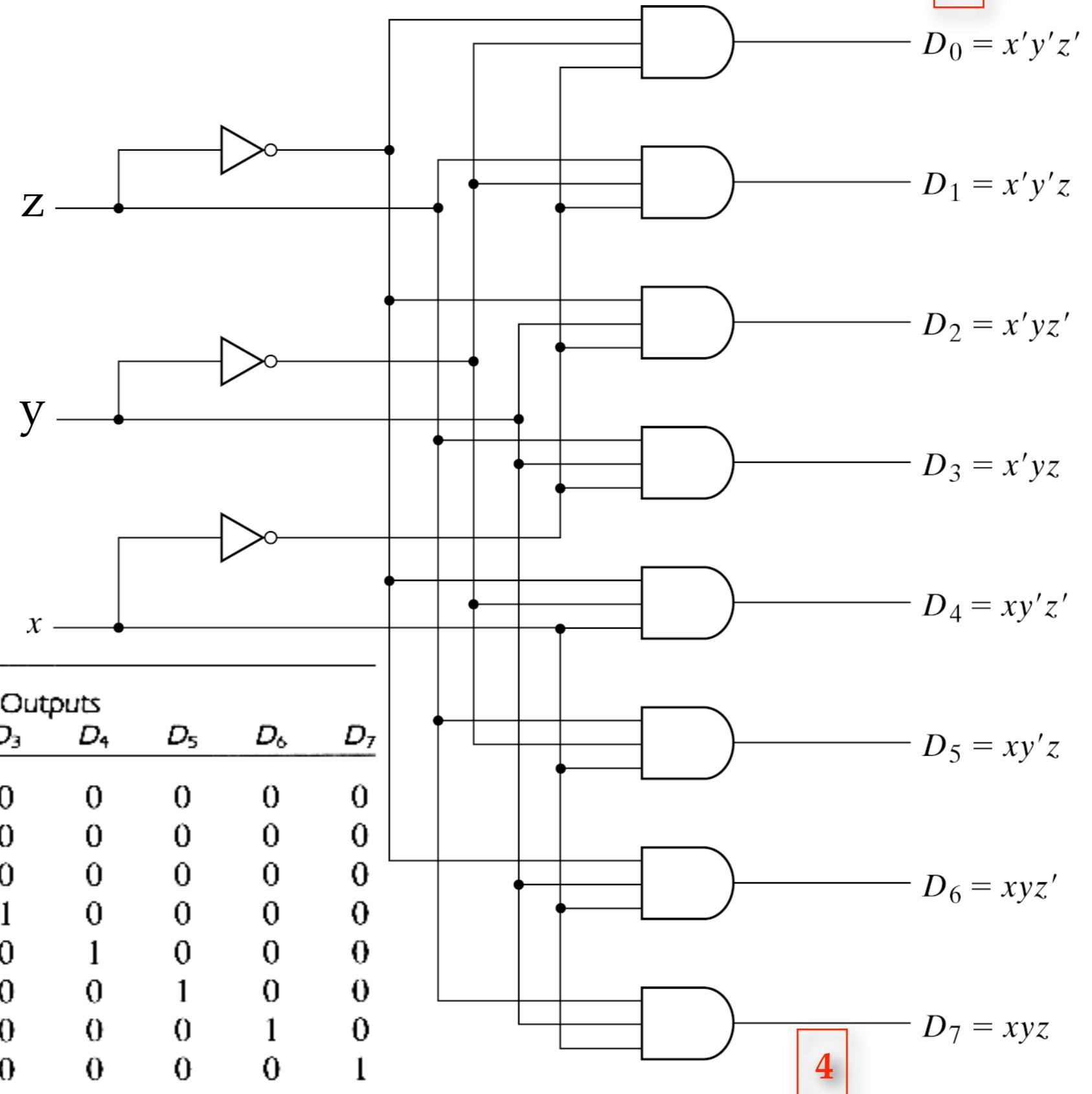


Inputs			1	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	Outputs
x	y	z	2									
0	0	0		1	0	0	0	0	0	0	0	
0	1	1		0	1	0	0	0	0	0	0	
0	1	0		0	0	1	0	0	0	0	0	
0	1	1		0	0	0	1	0	0	0	0	
1	0	0		0	0	0	0	1	0	0	0	
1	0	1		0	0	0	0	0	1	0	0	
1	1	0		0	0	0	0	0	0	1	0	
1	1	1	2	0	0	0	0	0	0	0	1	

4

Enabling

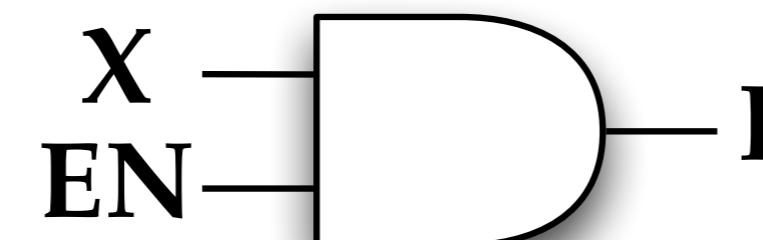- Enabling permits an input signal to pass through to an output.




$$F = \text{EN} \cdot X$$

EN	X	F
0	0	0
0	1	0
1	0	0
1	1	1

Decoder with Enable Input (1/3)

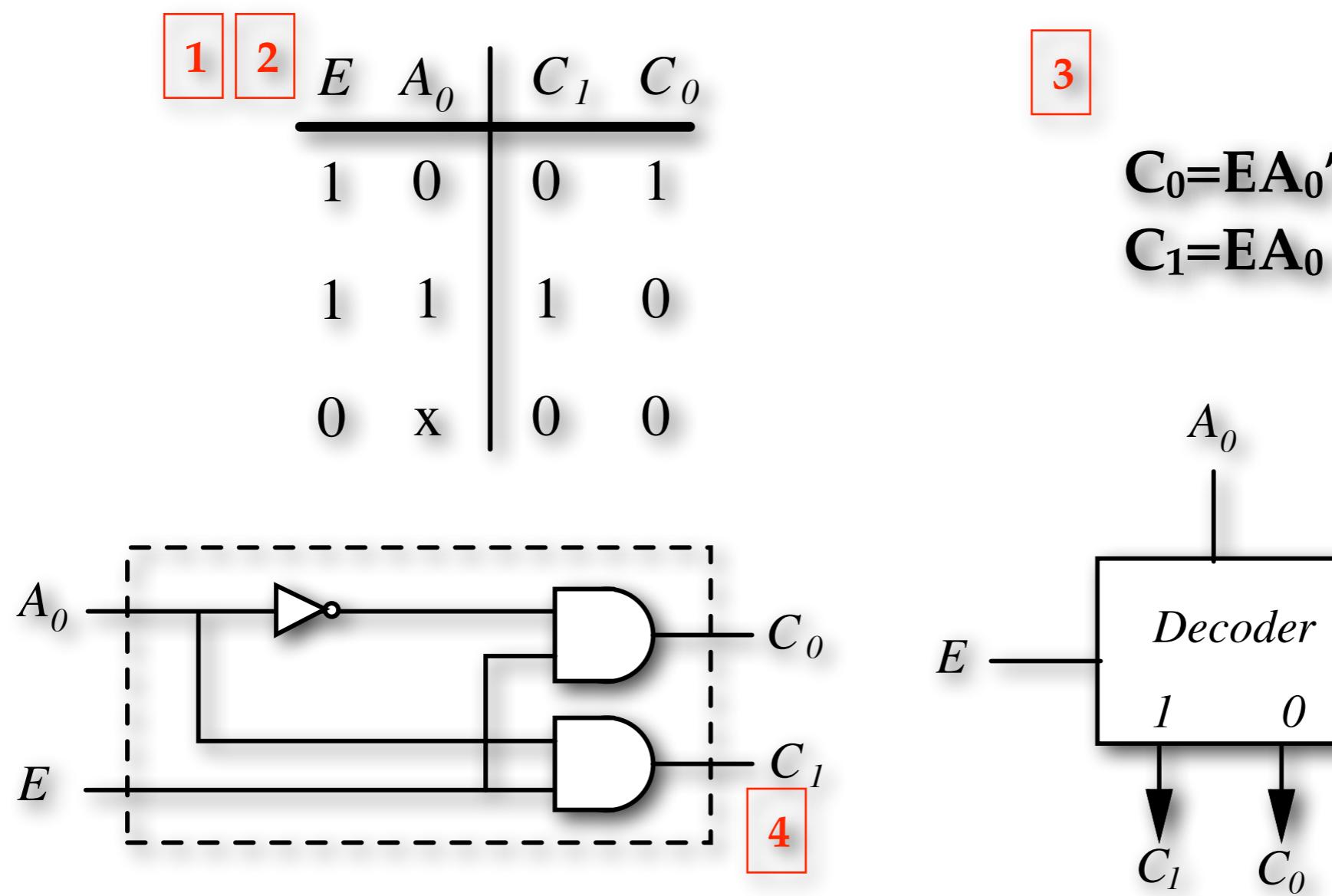- Line decoder with *enable* control (E)
- Also called demultiplexer (DMUX, DEMUX)



Decoder with Enable Input (2/3)


- Constructed with NAND gates

- decoder minterms in their complemented form (more economical)

1 2


E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

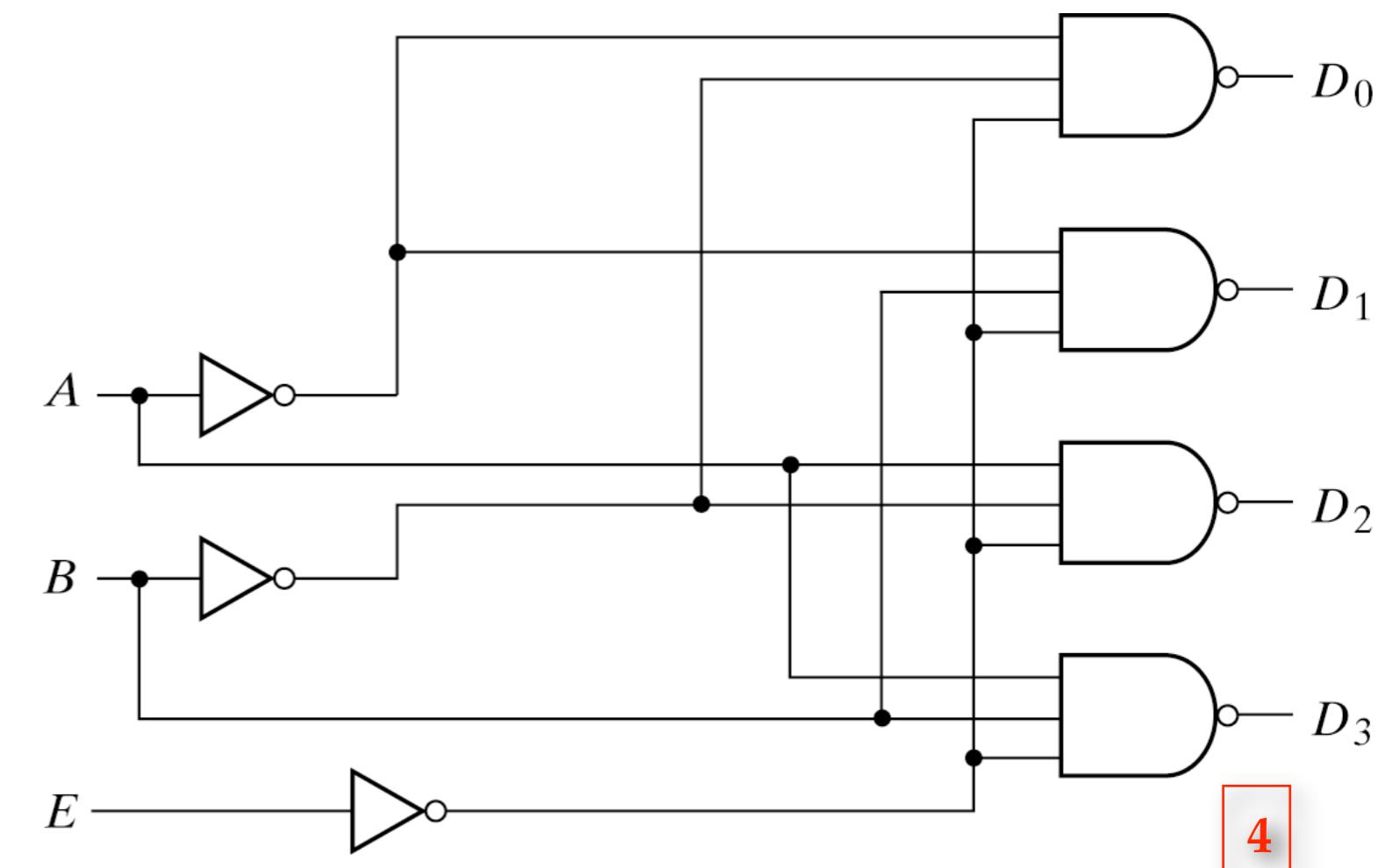3 D₀=(E'A'B')'
 D₁=(E'A'B')'
 D₂=(E'AB')'
 D₃=(E'AB)'




Decoder with Enable Input (3/3)

- decoder with enable vs. demultiplexer

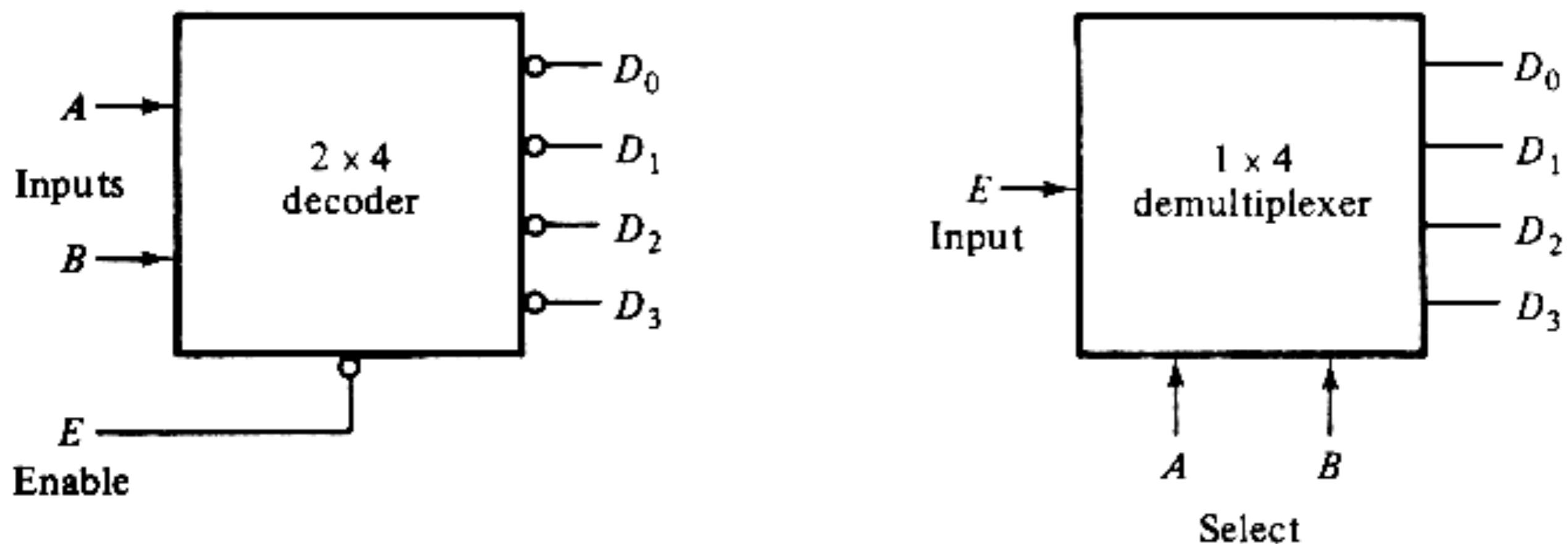

Decoder Expansion

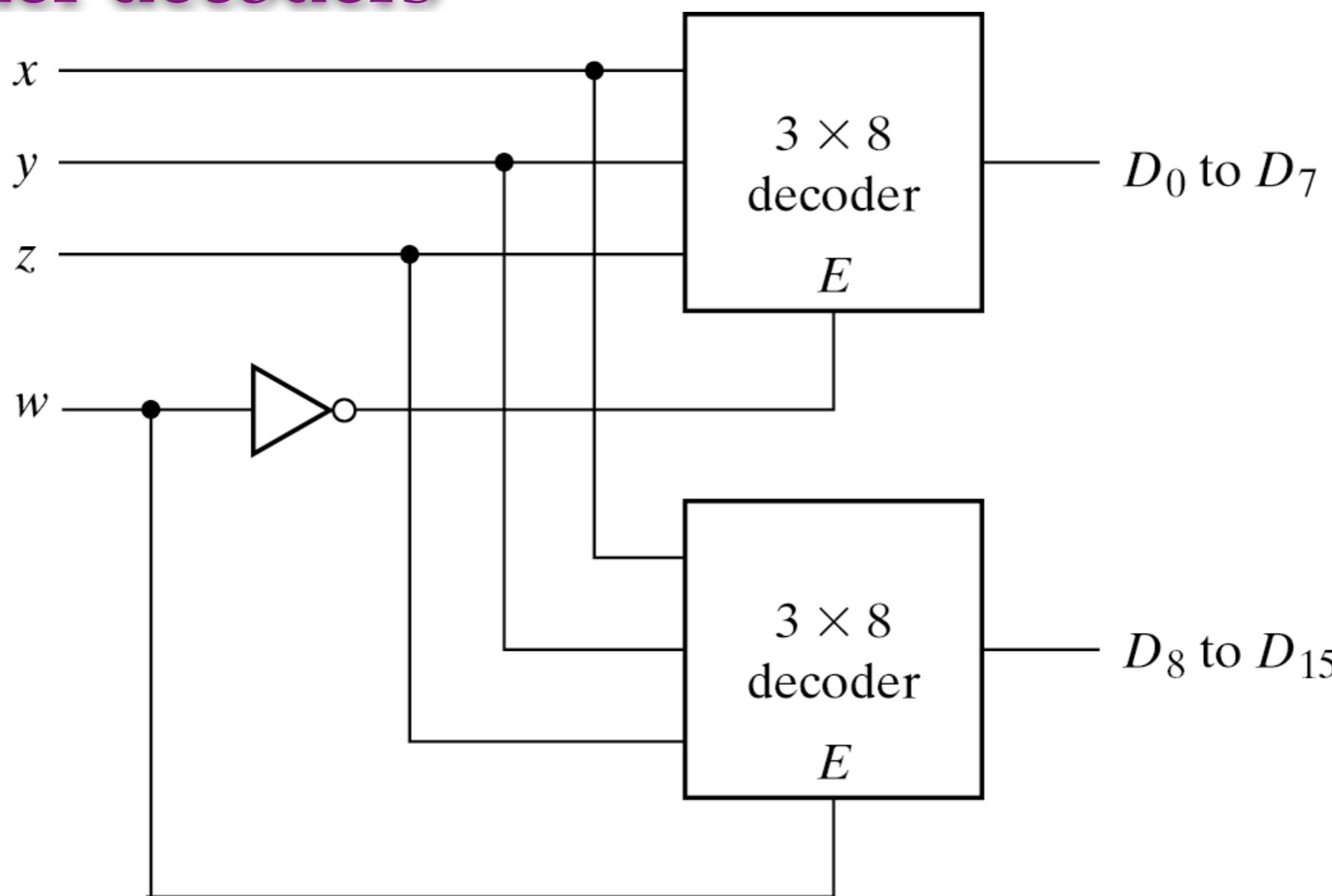- Larger decoders can be implemented with smaller decoders




A 4-to-16-line decoder from two 3-to-8-line decoders

Combinational Logic Implementation with Decoders

- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder in conjunction with m external OR gates

1	2	x	y	z	C	S
0	0	0	0	0	0	0
0	0	0	1	0	1	1
0	1	0	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	1
1	0	1	1	1	0	0
1	1	0	1	0	0	1
1	1	1	1	1	1	1

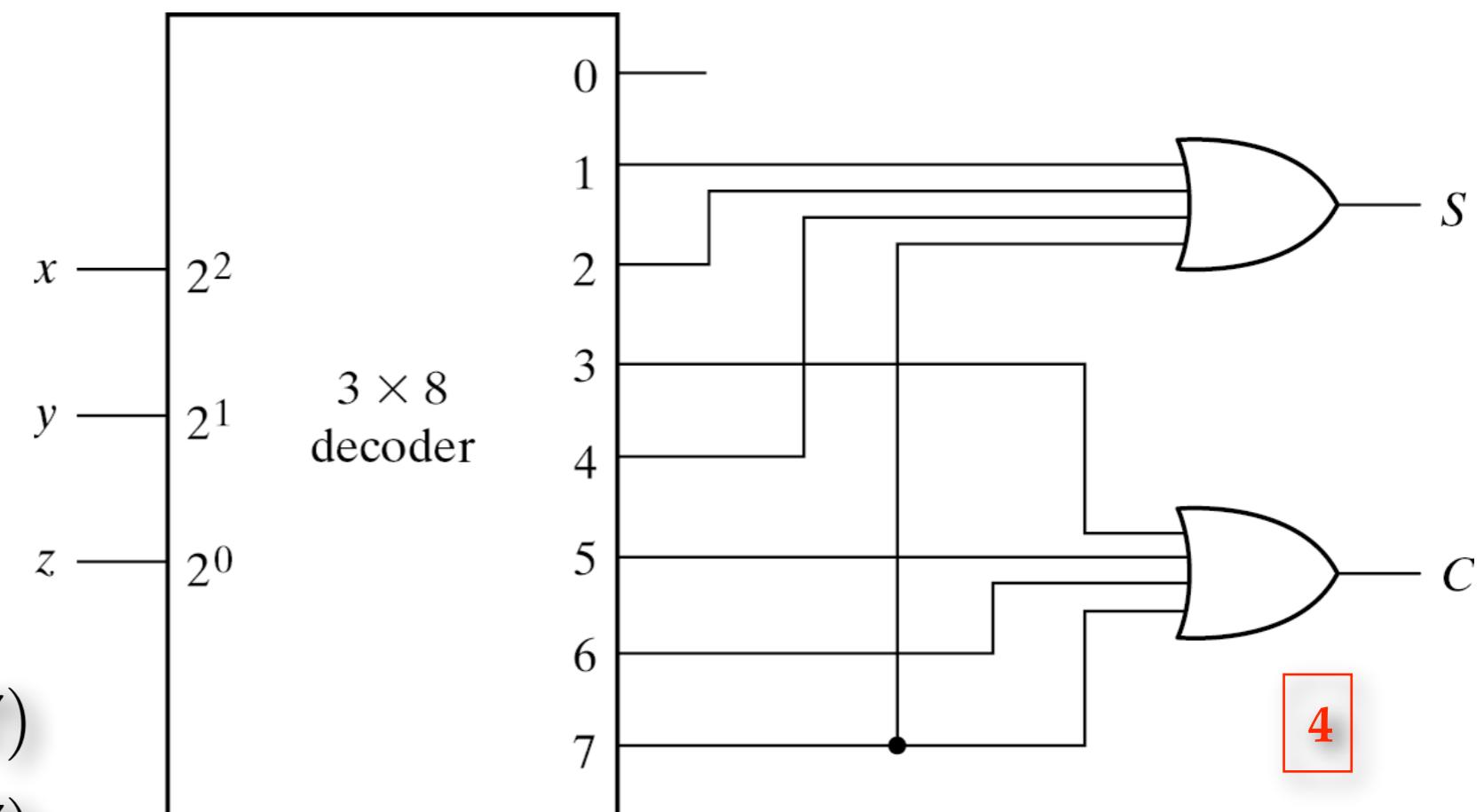


Encoders

Encoder

- An encoder is an inverse of a decoder.
- Encoder is a logic module that converts a *one-hot* input signal to a binary-encoded output signal
- Other input patterns are *forbidden* in the truth table.
- Example: a 4->2 encoder

a3	a2	a1	a0	b1	b0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

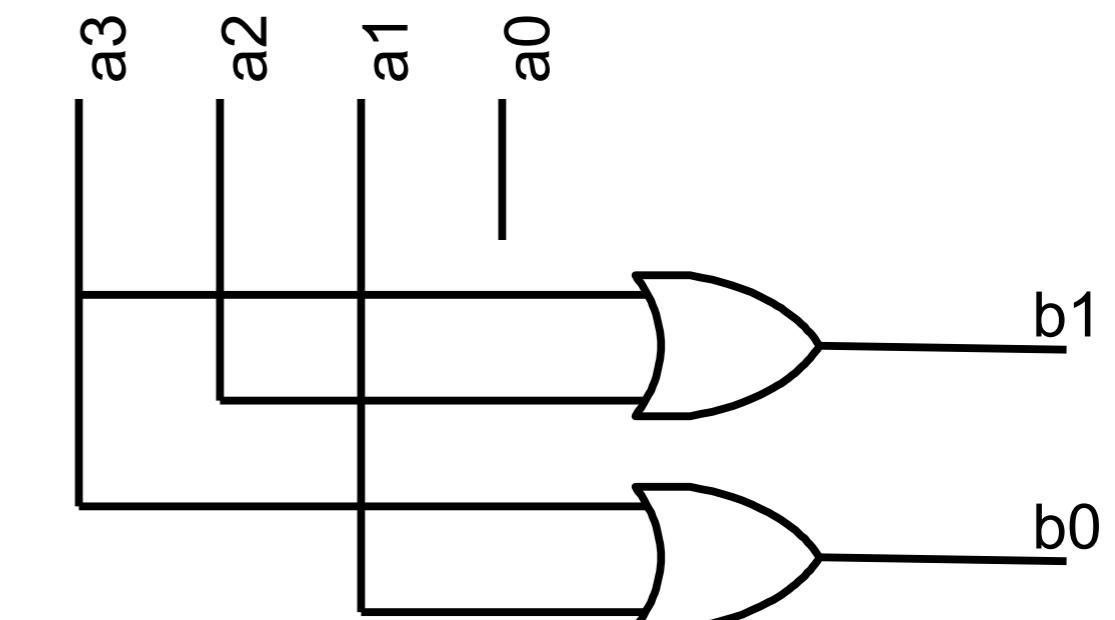

$$b_0 = a_3 + a_1$$

$$b_1 = a_3 + a_2$$


Encoder (1/2)

- A combinational logic that performs the inverse operation of a decoder
 - Only one input has value 1 at any given time
 - Can be implemented with OR gates

Truth Table of Octal-to-Binary Encoder

1 2		Inputs								Outputs			3
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z			
1	0	0	0	0	0	0	0	0	0	0	$x = D_4 + D_5 + D_6 + D_7$		
0	1	0	0	0	0	0	0	0	0	1	$y = D_2 + D_3 + D_6 + D_7$		
0	0	1	0	0	0	0	0	0	1	0	$z = D_1 + D_3 + D_5 + D_7$		
0	0	0	1	0	0	0	0	0	1	1			
0	0	0	0	1	0	0	0	1	0	0			
0	0	0	0	0	1	0	0	1	0	1			
0	0	0	0	0	0	1	0	1	1	0			
0	0	0	0	0	0	0	1	1	1	1			

Encoder (2/2)

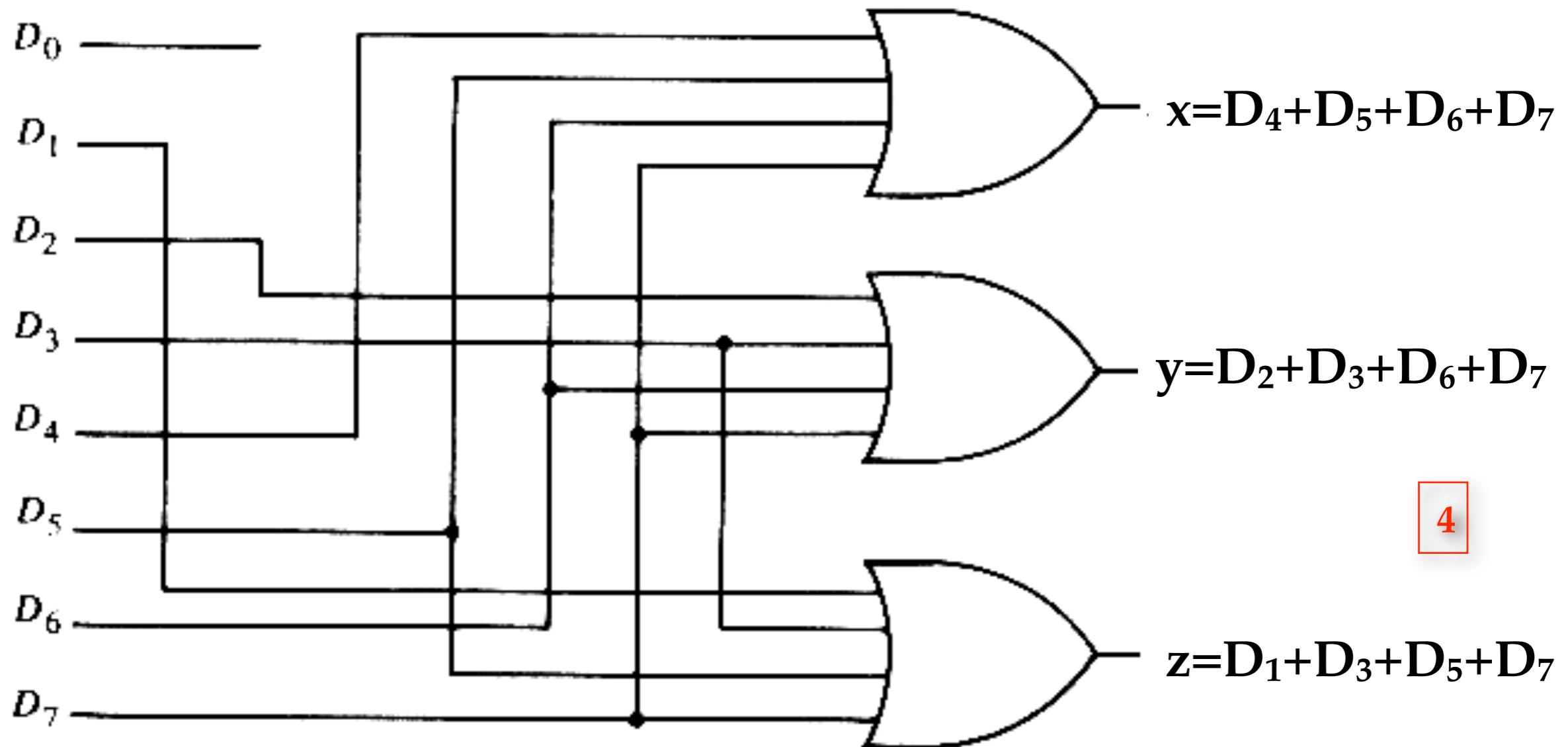

However, when both D_3 and D_6 goes 1,
 illegal inputs
 the output will be 111 (ambiguity)!!!

Use priority encoder!

Priority Encoder (1/2)



- Ensure only one of the input is encoded
- D_3 has the highest priority, while D_0 has the lowest priority.
- X is the don't care conditions, V is the valid output indicator.

<u>Inputs</u>				<u>Outputs</u>				
D_0	D_1	D_2	D_3	1	2	x	y	V
0	0	0	0			X	X	0
1	0	0	0			0	0	1
X	1	0	0			0	1	1
X	X	1	0			1	0	1
X	X	X	1			1	1	1

3

$V = D_0 + D_1 + D_2 + D_3$


Priority Encoder (2/2)

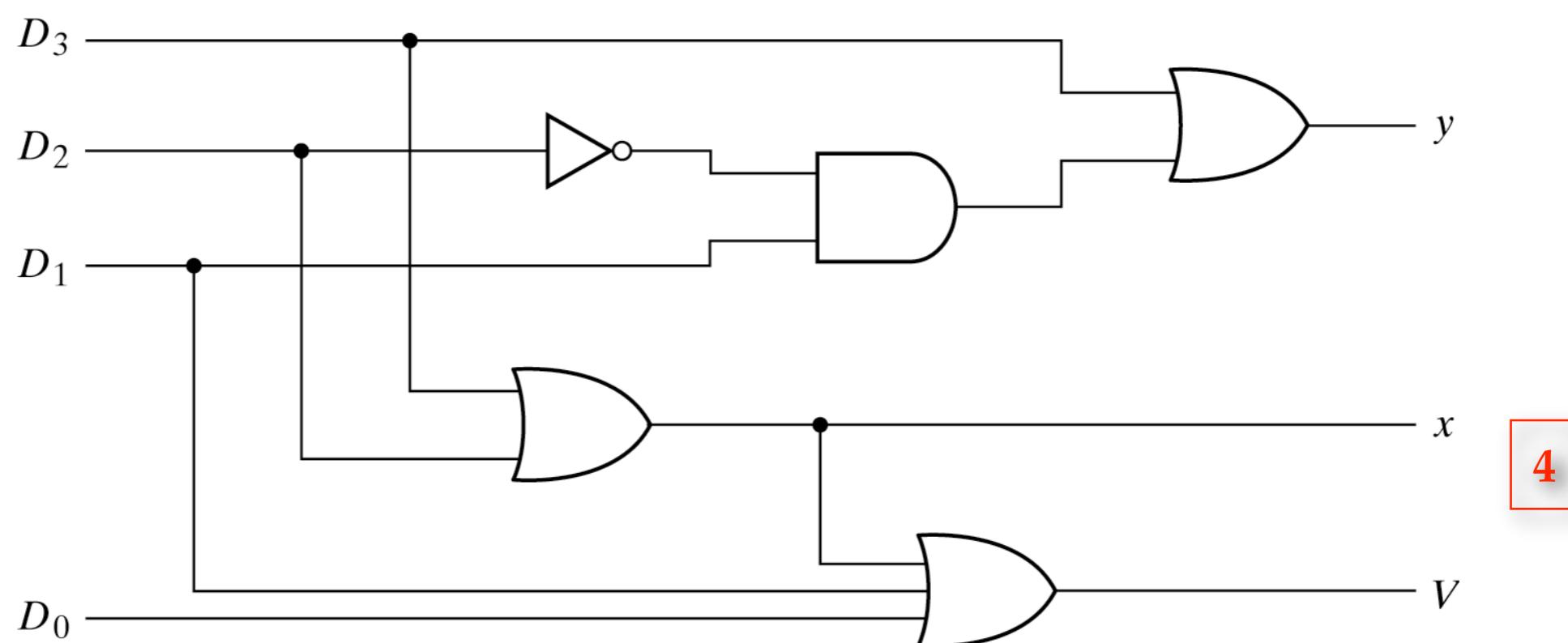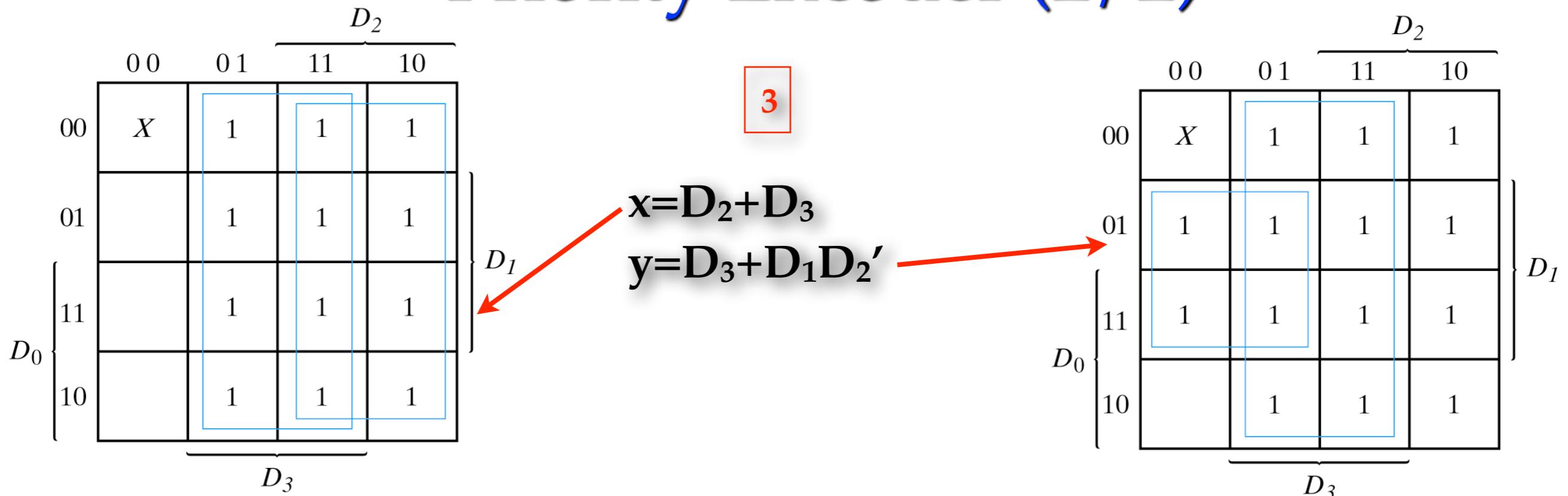

Arbiters and Priority Encoders


Arbiters

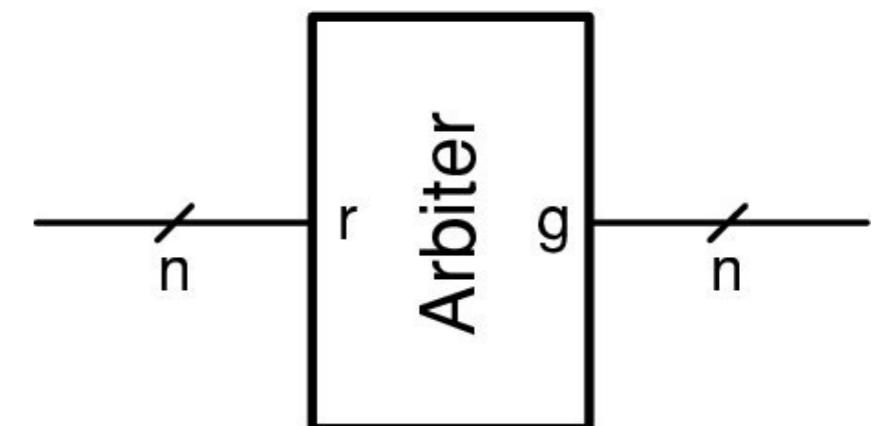- Arbiter handles requests from multiple devices to use a single resource
 - Also called *find-first-one* (FF1) unit
 - Accepts an arbitrary input signal (r), and outputs a one-hot signal (g) to indicate the least significant 1 (or the most significant 1) of the input
 - Example: input: 01011100
 - output: 00000100 (least significant 1)
 - output: 01000000 (most significant 1)




Finds the first “1” bit in r
 $g[i] = 1$ if $r[i] = 1$ and $r[j] = 0$ for $j < i$
 (for the least significant 1)


Implementation of Arbiters

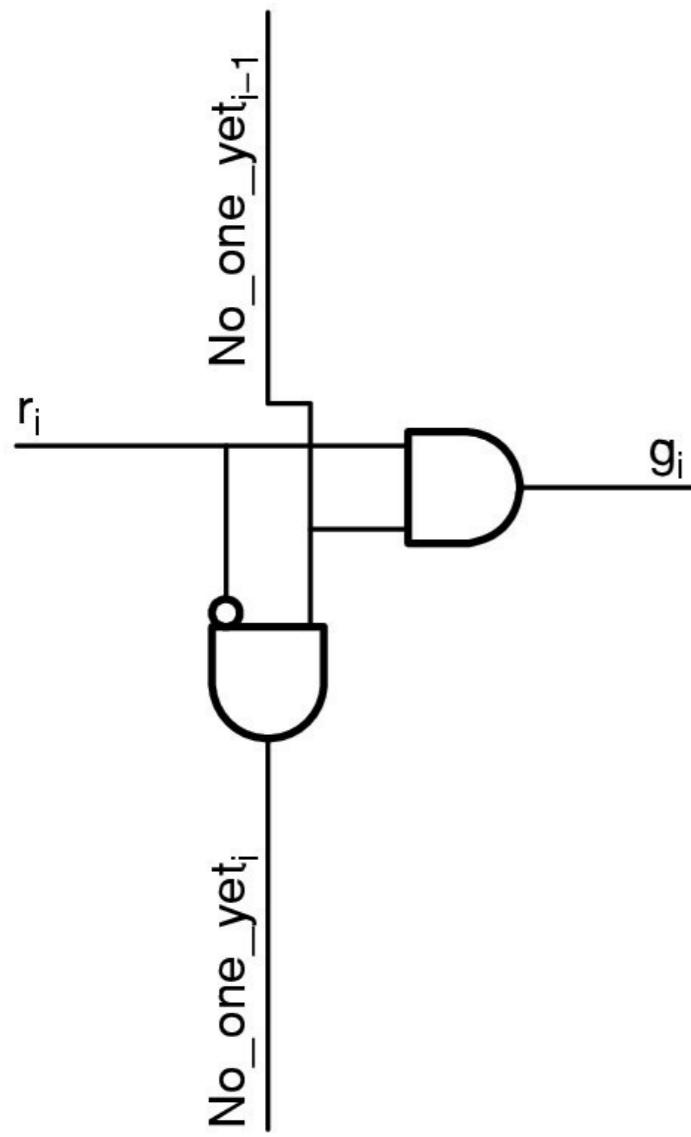

1 bit cell of arbiter

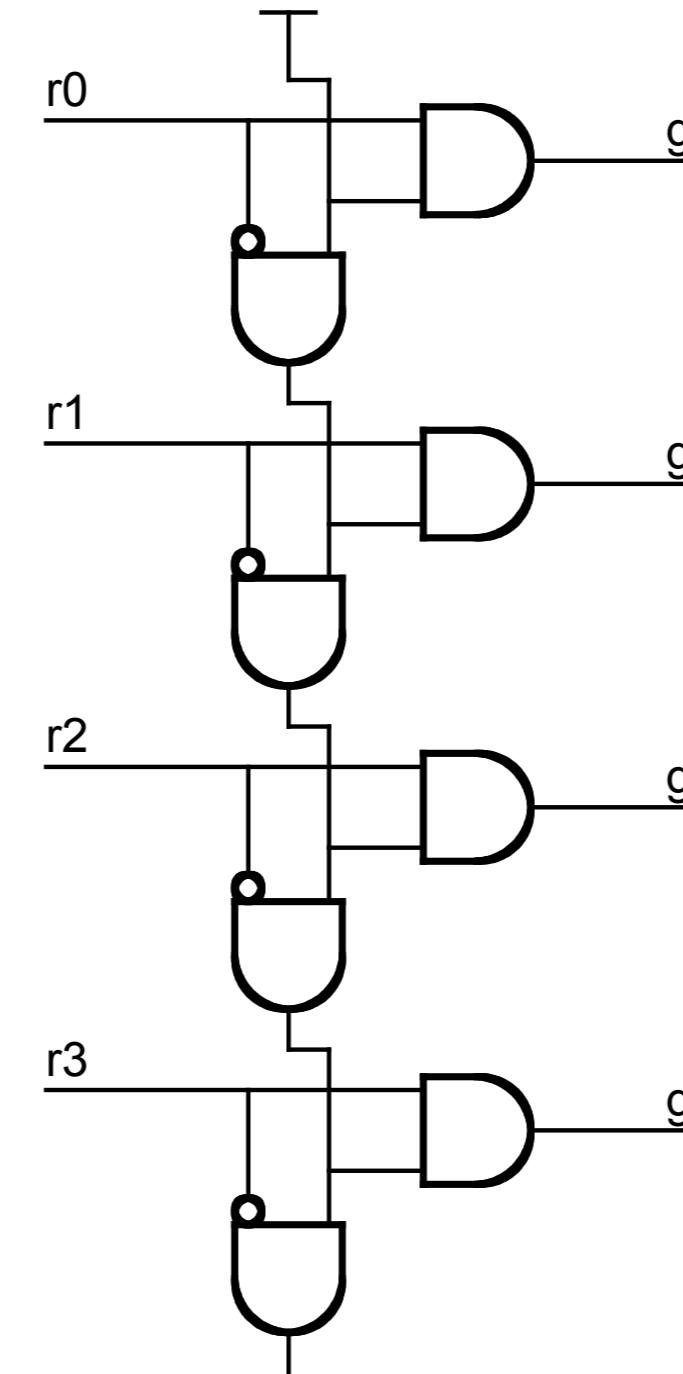


Using bit cell

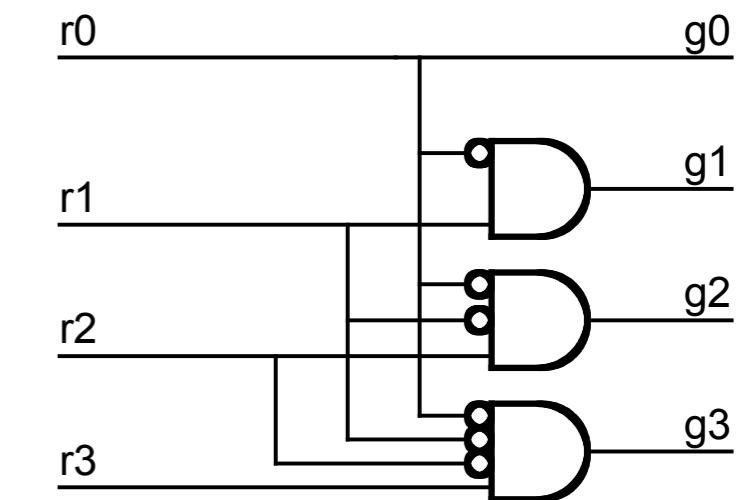

Using look ahead

Priority Encoder

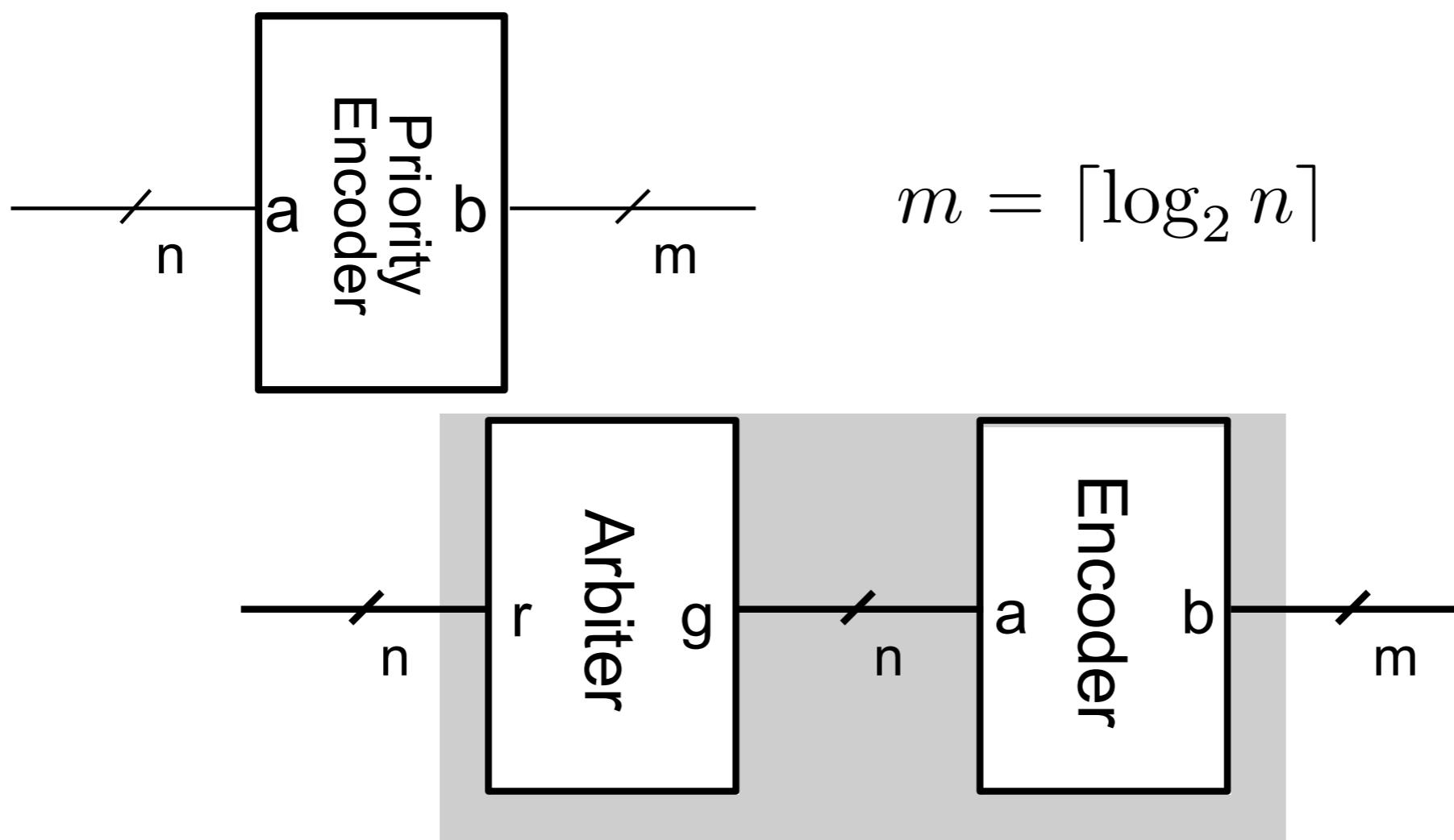
- n-bit one-hot input signal a
- m-bit output signal b
 - b indicates the position of the first 1 bit in a




Multiplexers

Multiplexers / Selectors

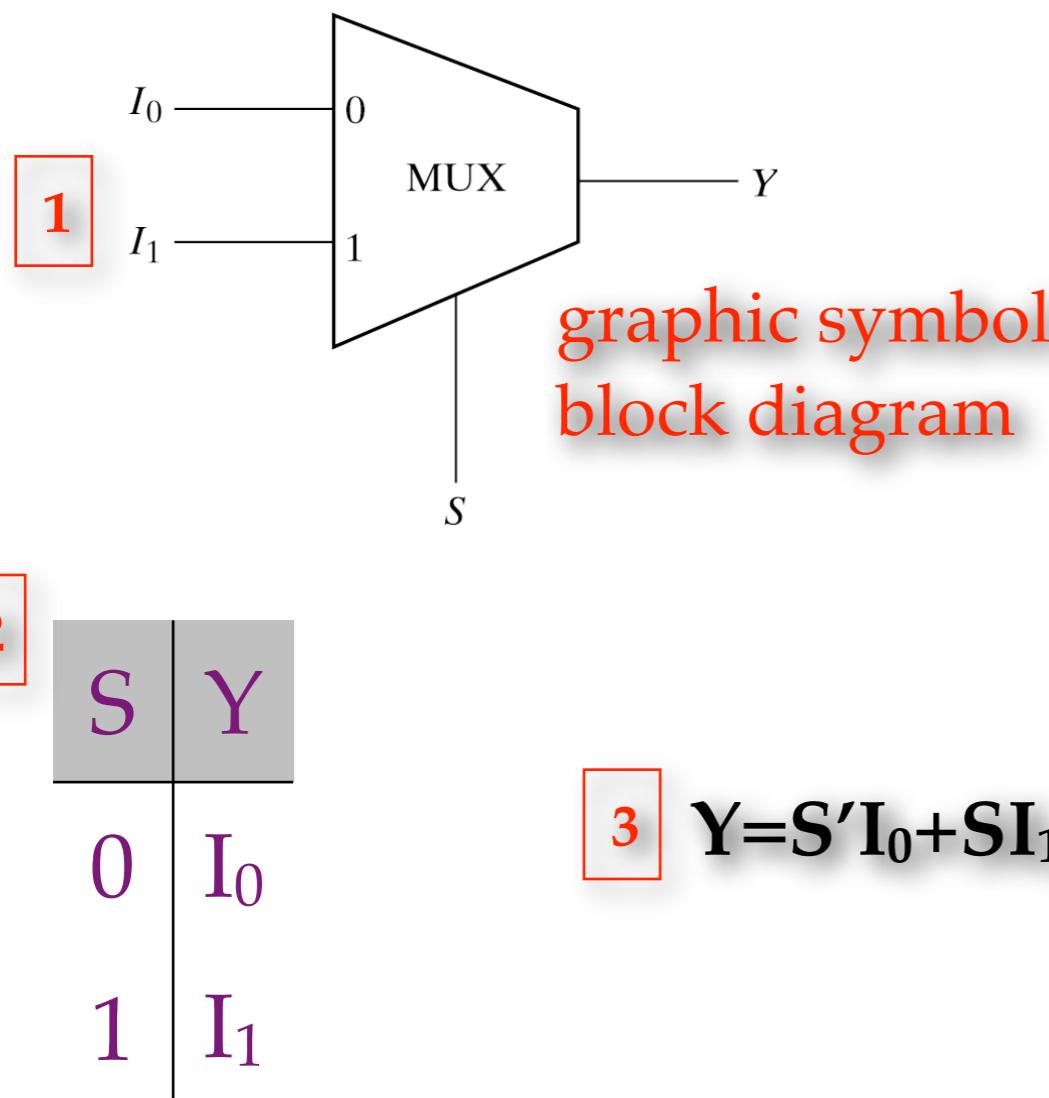
- A Multiplexer selects (usually by n select lines) binary information from one of many (usually 2^n) input lines and directs it to a single output line.



2:1 multiplexer

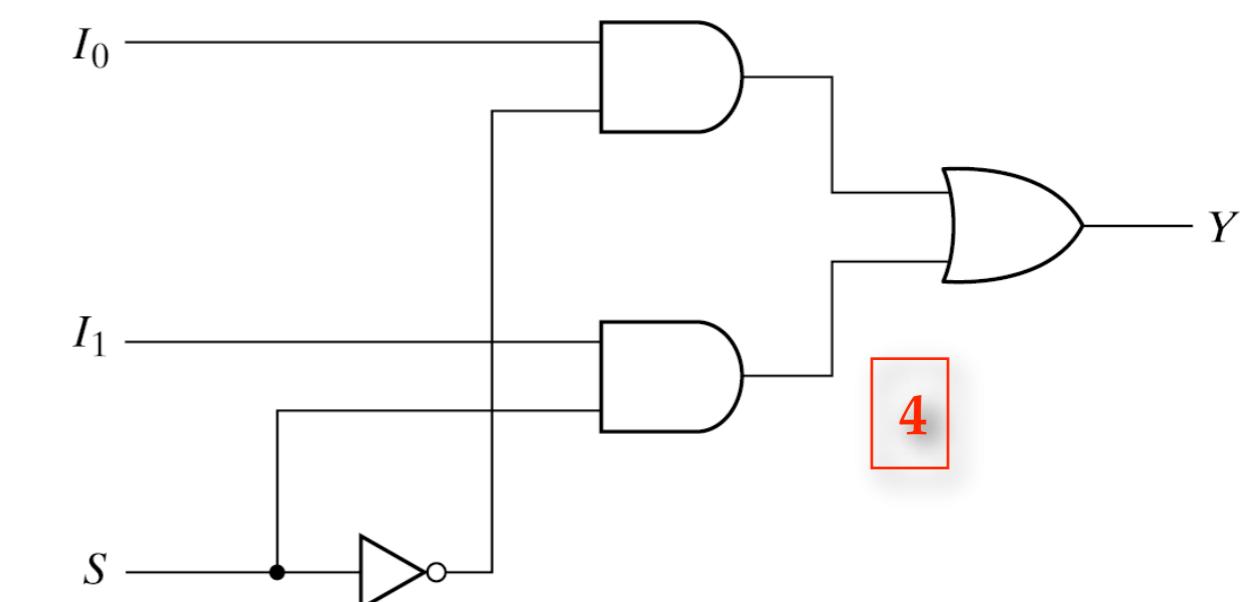

4:1 MUX

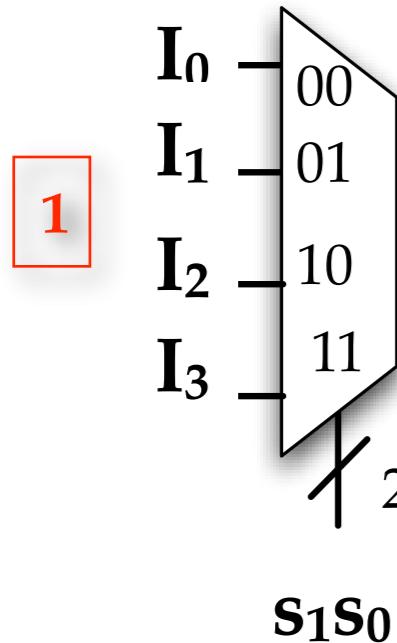


graphic symbol/
block diagram

2

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


$$Y = s_0' s_1' I_0 + s_0 s_1' I_1 + s_0' s_1 I_2 + s_0 s_1 I_3$$

3

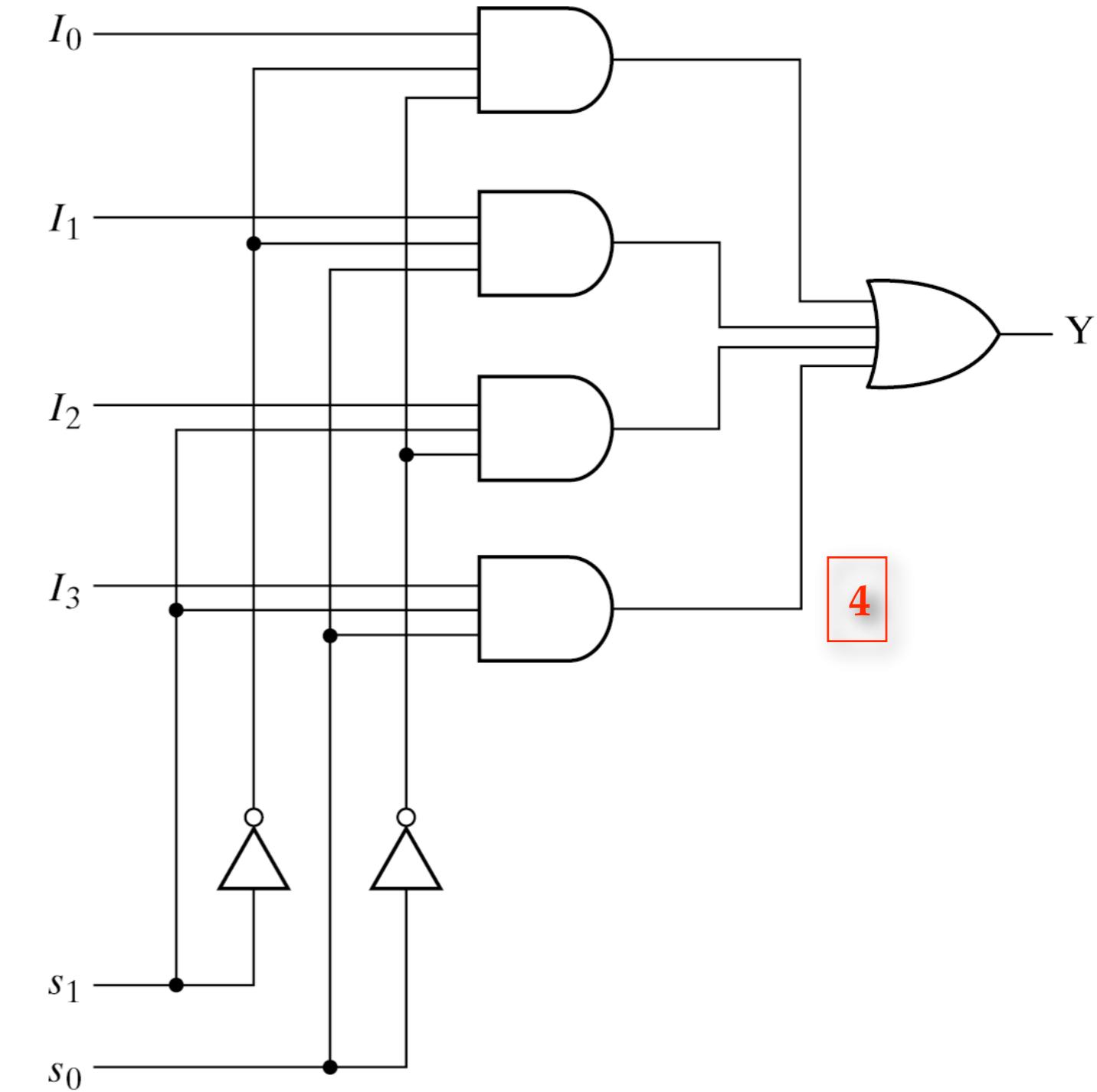


MUX as a Decoder

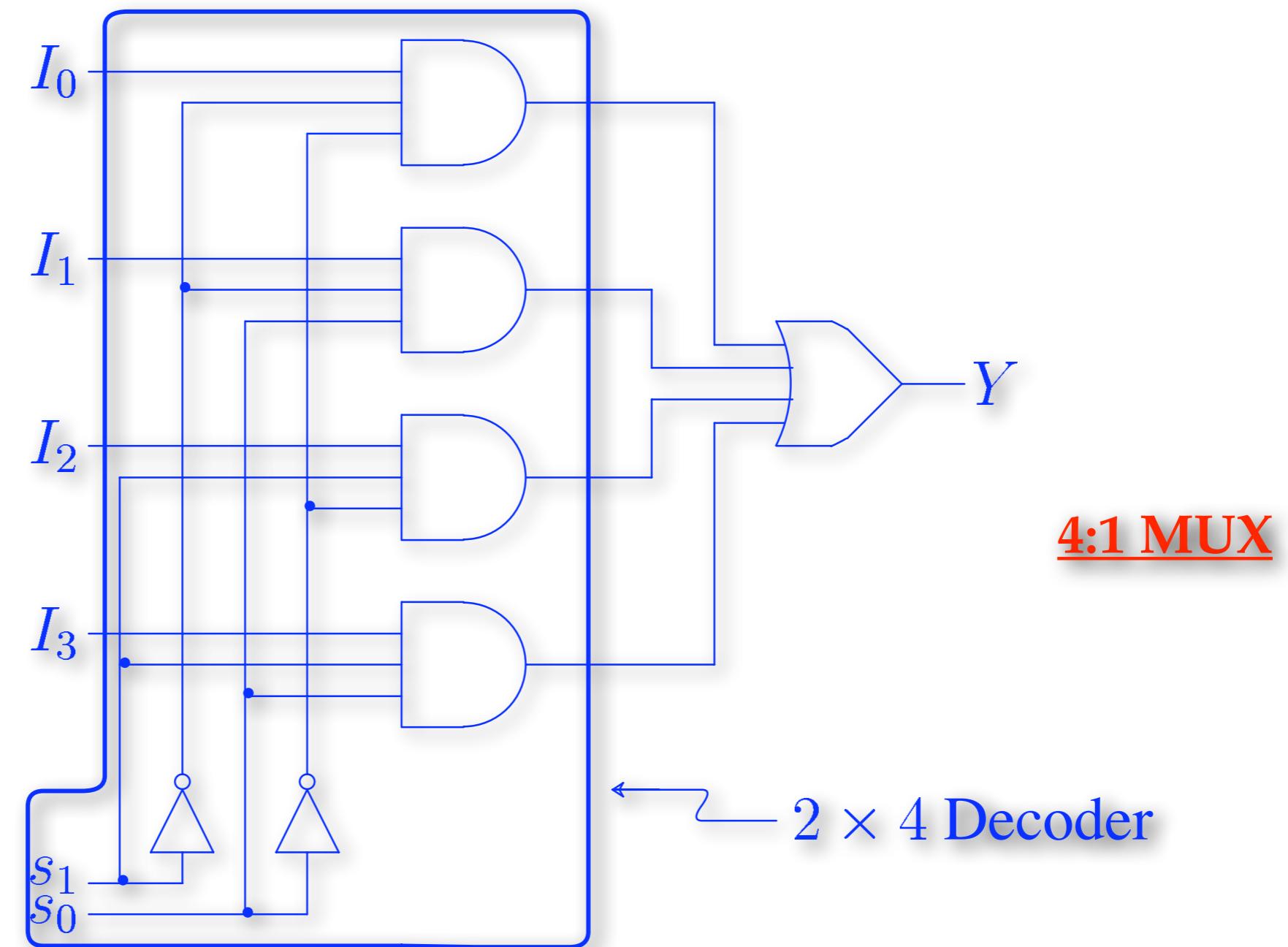- MUX = decoder + OR gate + enable (optional)




Multiplexer Implementation

- One-bit 4:1 multiplexer

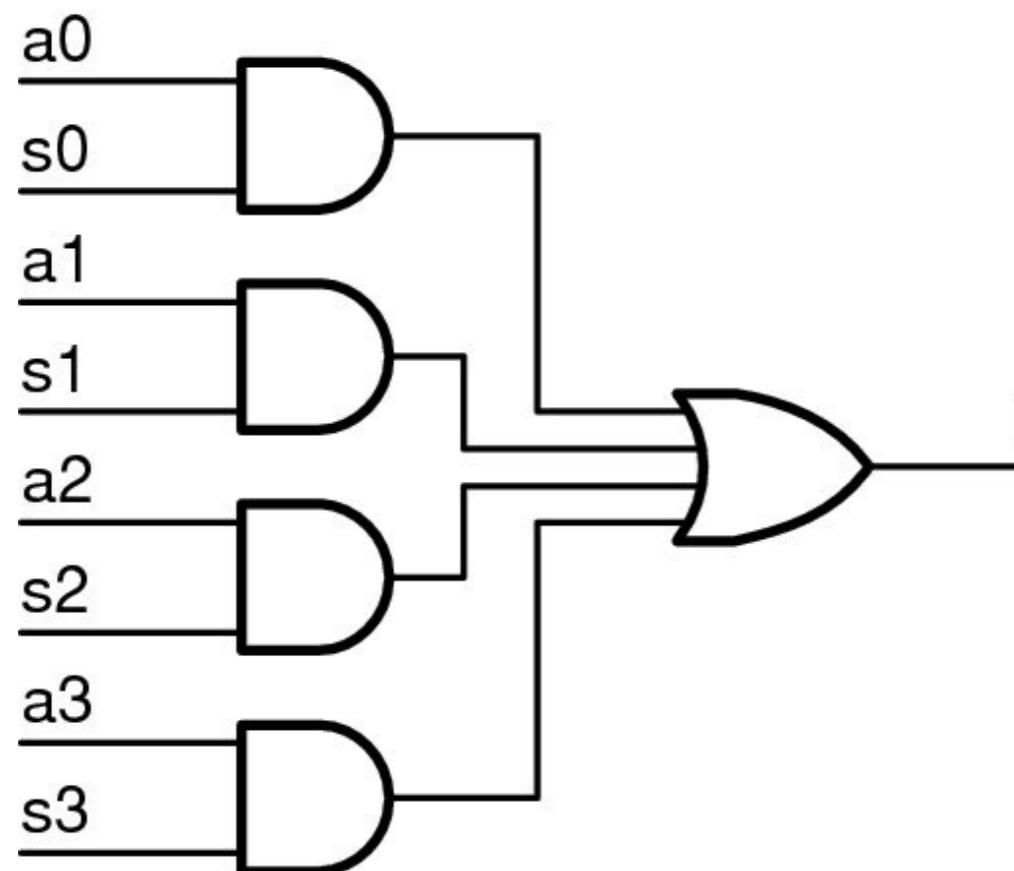

Using AND-OR circuit

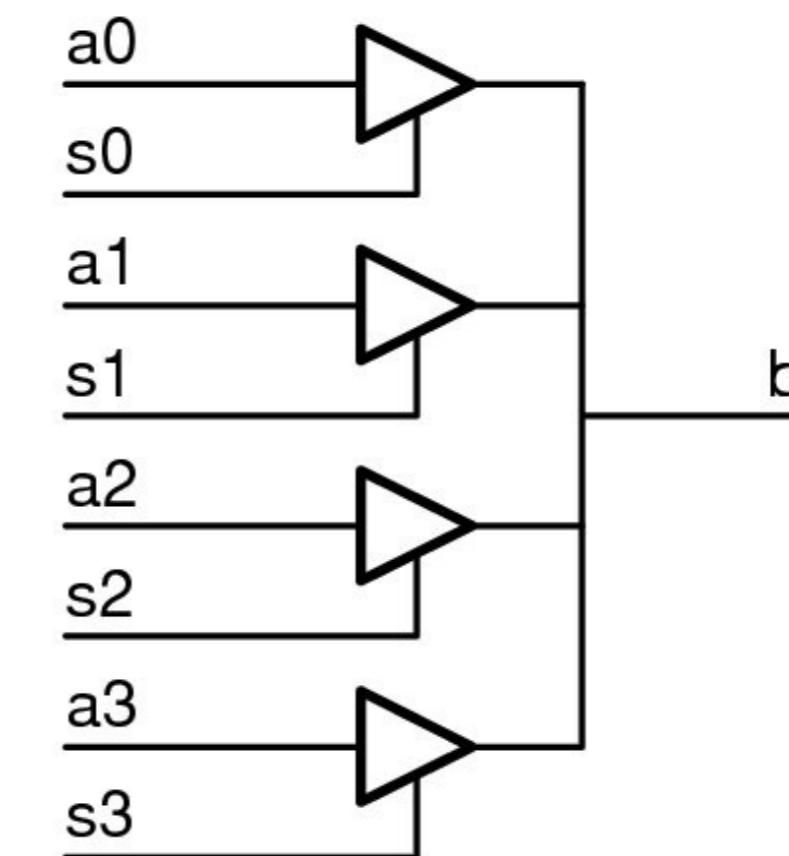


Using Tri-state buffer

Quadruple 2:1 MUX (4-bit 2:1 MUX)

Function table

E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B


four 2:1 MUX with enable

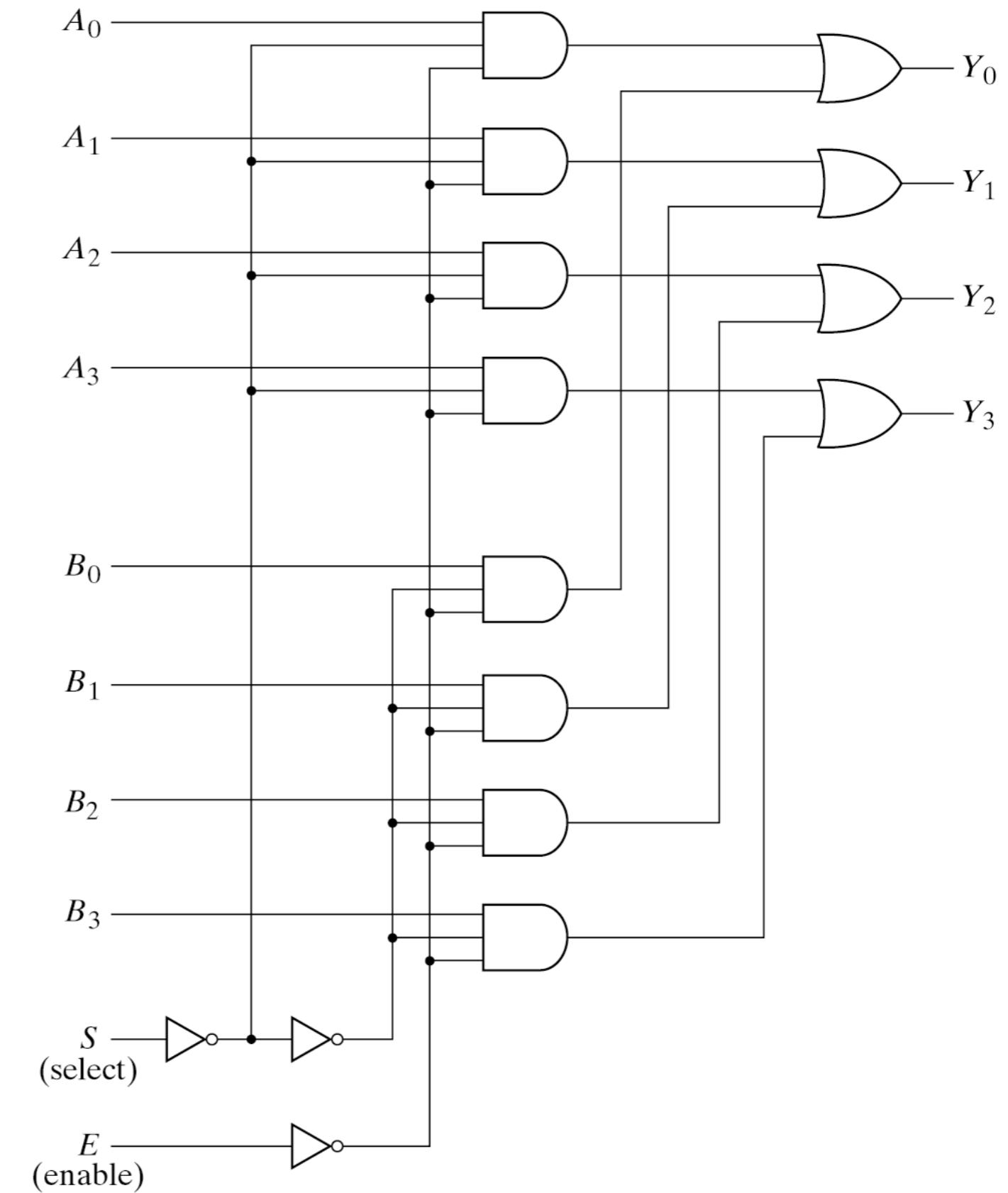

Boolean Function Implementation with a MUX (1/3)

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	2
1	0	1	0
1	1	0	3
1	1	1	1

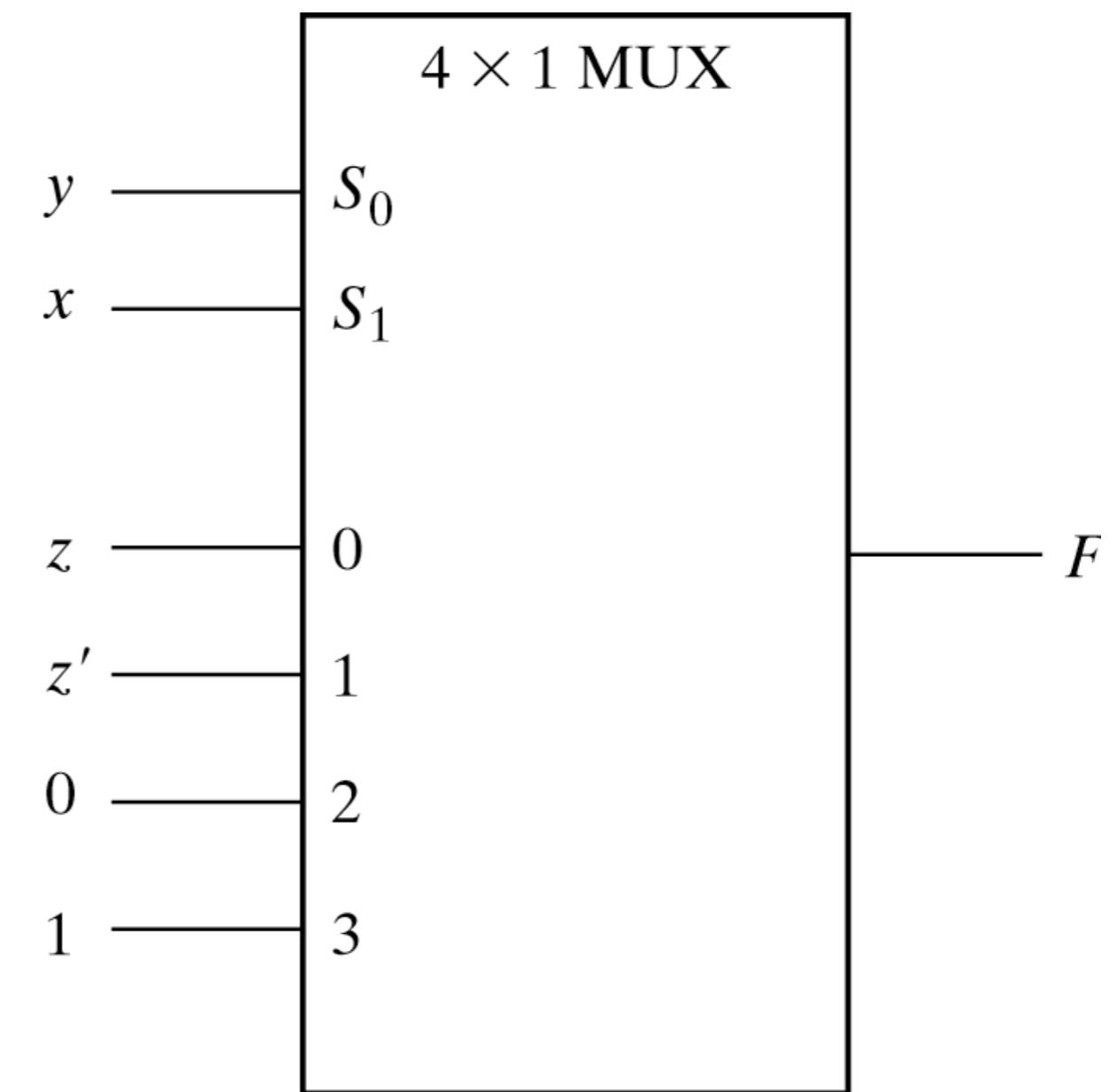

Boolean Function Implementation with a MUX (2/3)

- Assign an ordering sequence of the $n-1$ input variables (x,y) to the selection input of MUX
- The last variable (z) will be used for the input lines
- Construct the truth table
- Consider a pair of consecutive minterms starting from m_0
- Determine the input lines according to the last variable (z) and output signals (F) in the truth table

Boolean Function Implementation with a MUX (3/3)

$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

0 $F = D$
 1 $F = D'$
 2 $F = D'$
 3 $F = 0$
 4 $F = 0$
 5 $F = D$
 6 $F = 1$
 7 $F = 1$

C S_0
 B S_1
 A S_2

D 0
 1
 2
 3
 4
 5
 6
 7

0 0
 1
 2
 3
 4
 5
 6
 7

1 0
 1
 2
 3
 4
 5
 6
 7

0 0
 1
 2
 3
 4
 5
 6
 7

1 0
 1
 2
 3
 4
 5
 6
 7

0 0
 1
 2
 3
 4
 5
 6
 7

1 0
 1
 2
 3
 4
 5
 6
 7

0 0
 1
 2
 3
 4
 5
 6
 7

1 0
 1
 2
 3
 4
 5
 6
 7


0 0
 1
 2
 3
 4
 5
 6
 7

1





Bus

- Bus is a common communication channel which is routed around modules on a microchip or PCB.
- To construct a bus, we use a component, tristate driver (buffer), which has three possible output states: 0, 1, Z (high impedance).
- Functionally, a bus is equivalent to a selector. It has many inputs but allow only one data on the bus at a time.

	C	Y
0		Z
1		A

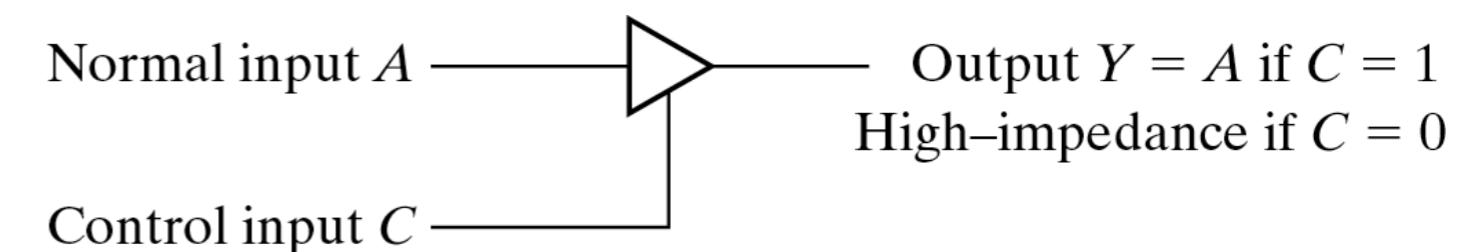


MUX with Three-State Gates

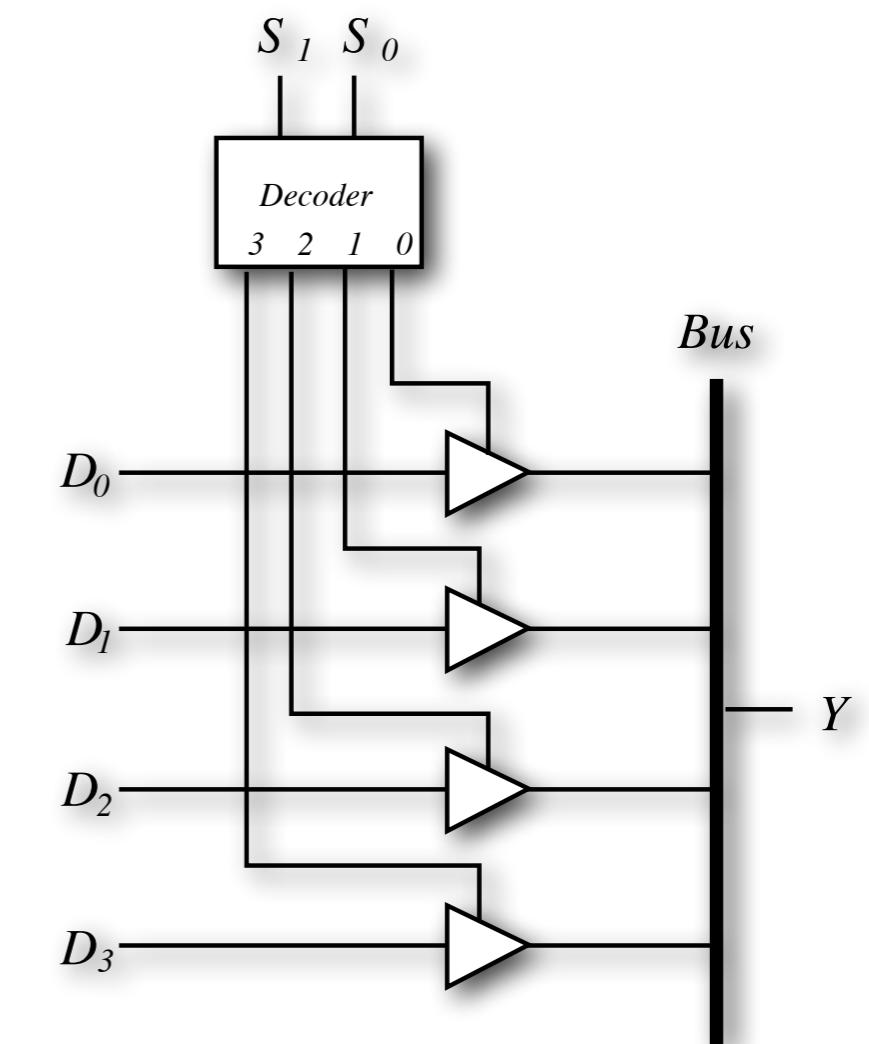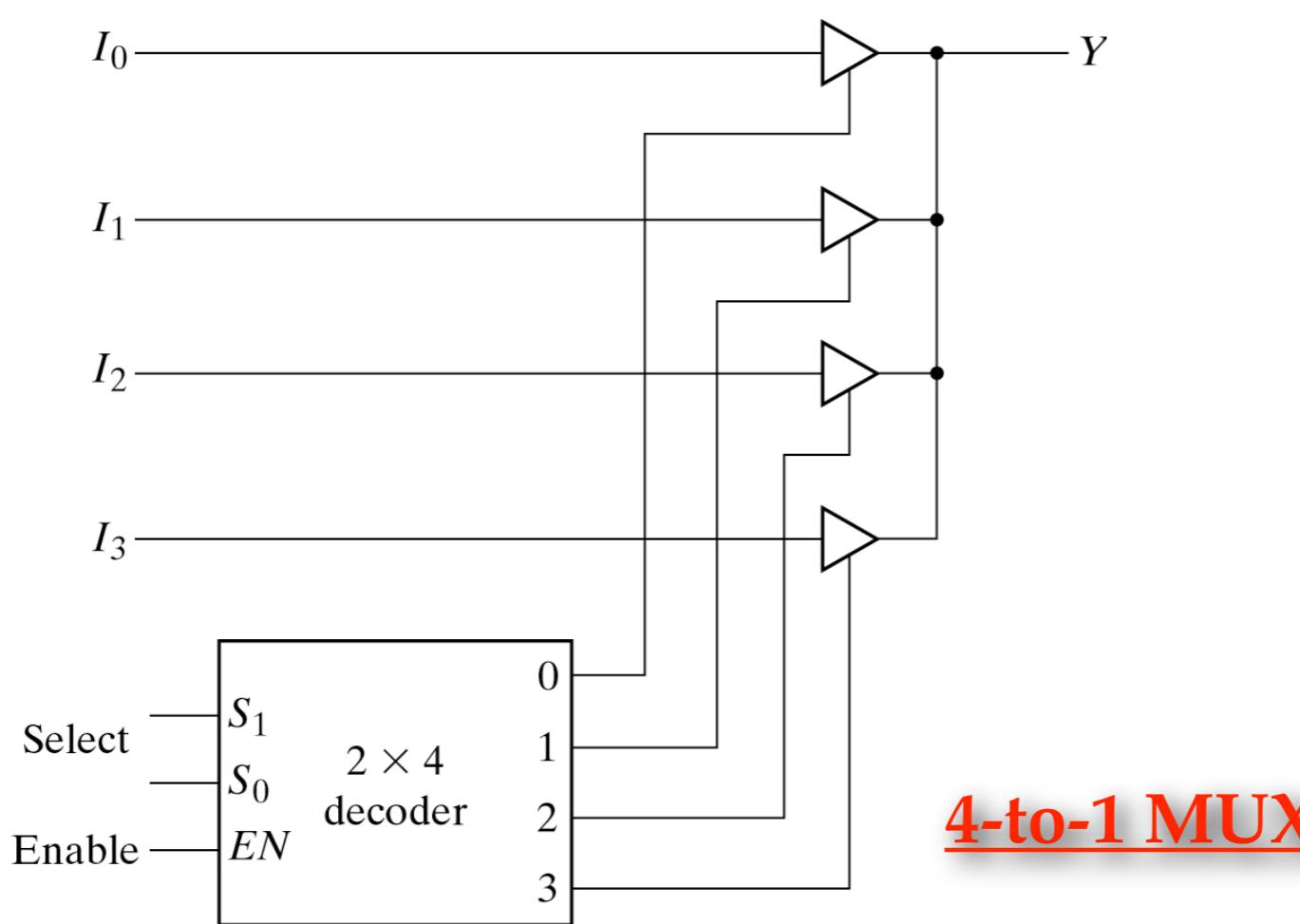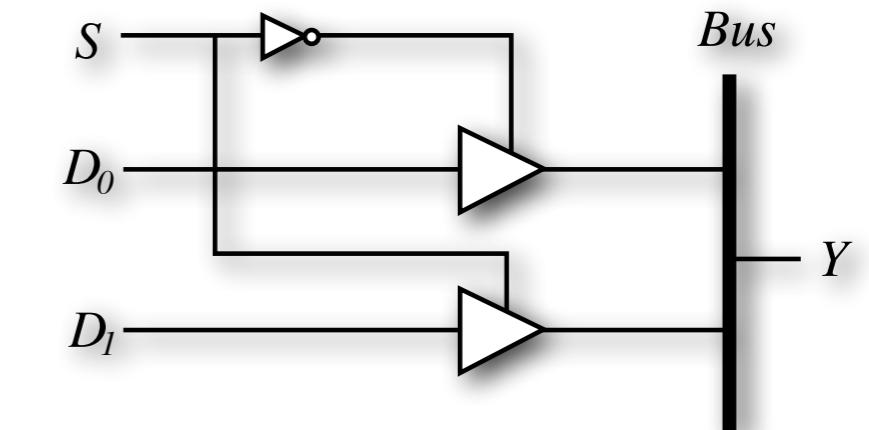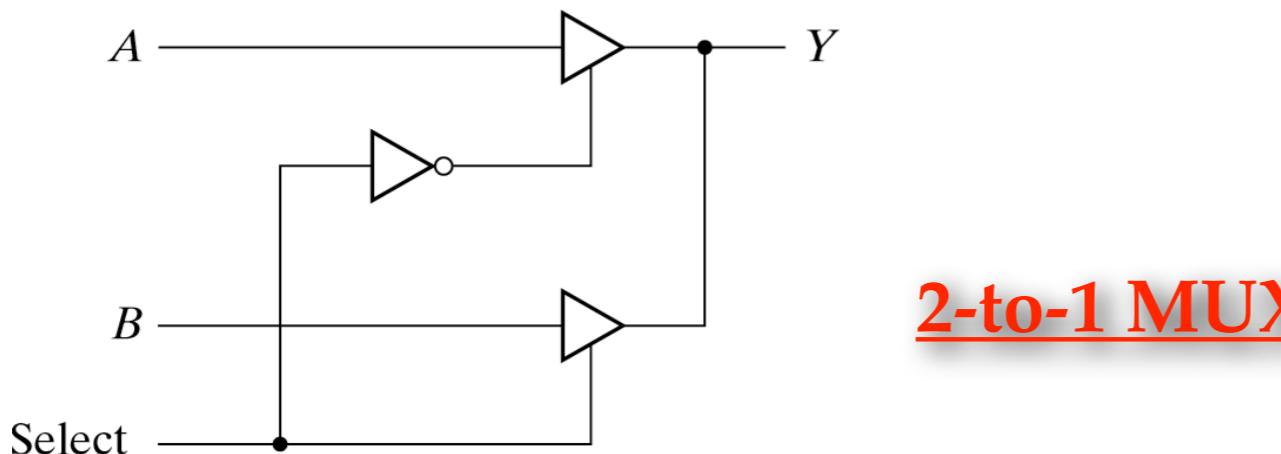

Shifter

Shifter

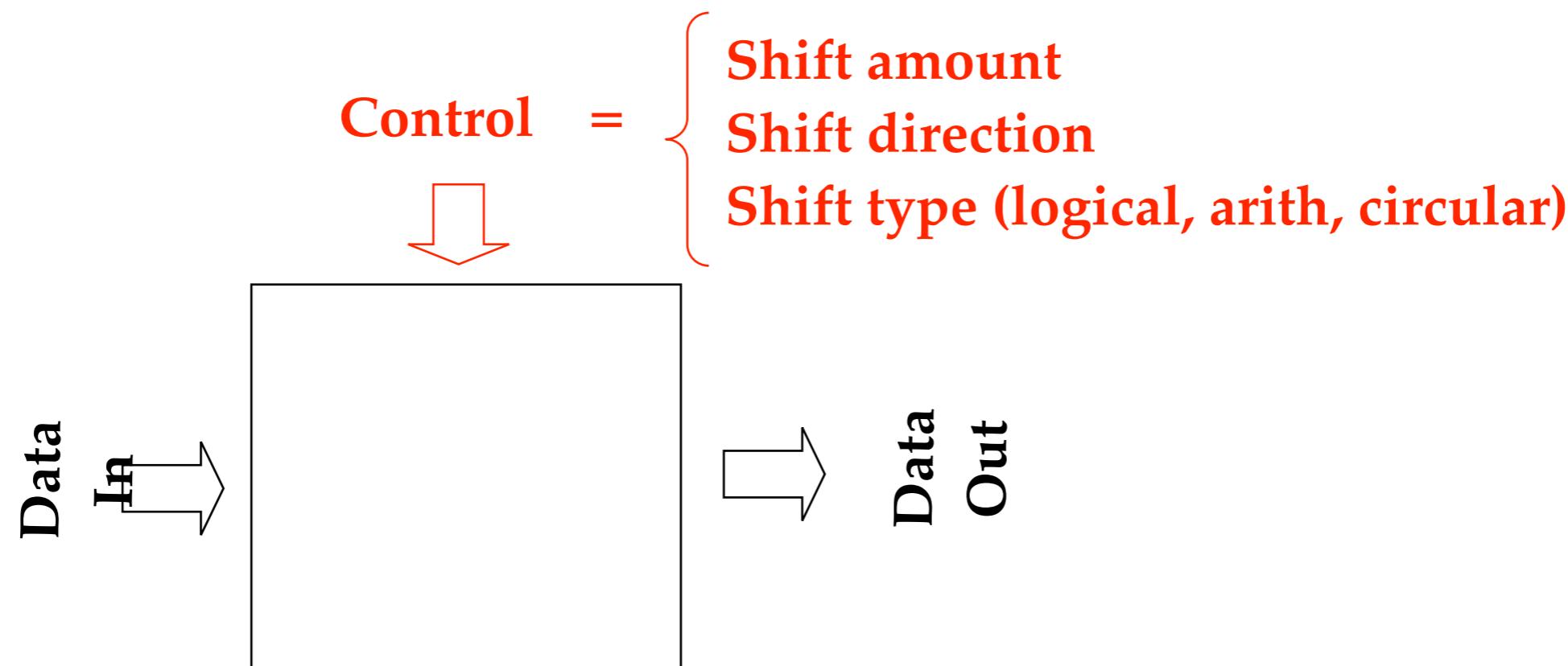- A shifter shifts one bit position of its content to the left or right at a time, taking the input bit from the right or left when it shifts.



Shifter Types

- Logical shifter

- Shift the number to the left or right and fills empty spots with 0's
- Ex: 1101, LSR 1=**0110**, LSL 1=**1010**

- Arithmetic shifter


- Same as logical shifter but on right shift fills empty the *MSBs* with the sign bit (sign extension)
- Ex: 1101, ASR 1=**1110**, ASL 1=**1010**

- Barrel shifter (rotator, cyclic shift)

- Rotate numbers in a circle such that empty spots are filled with *bits shifted off* the other end
- Ex: 1101, RSR 1=**1110**, RSL 1=**1011**


Funnel Shifter

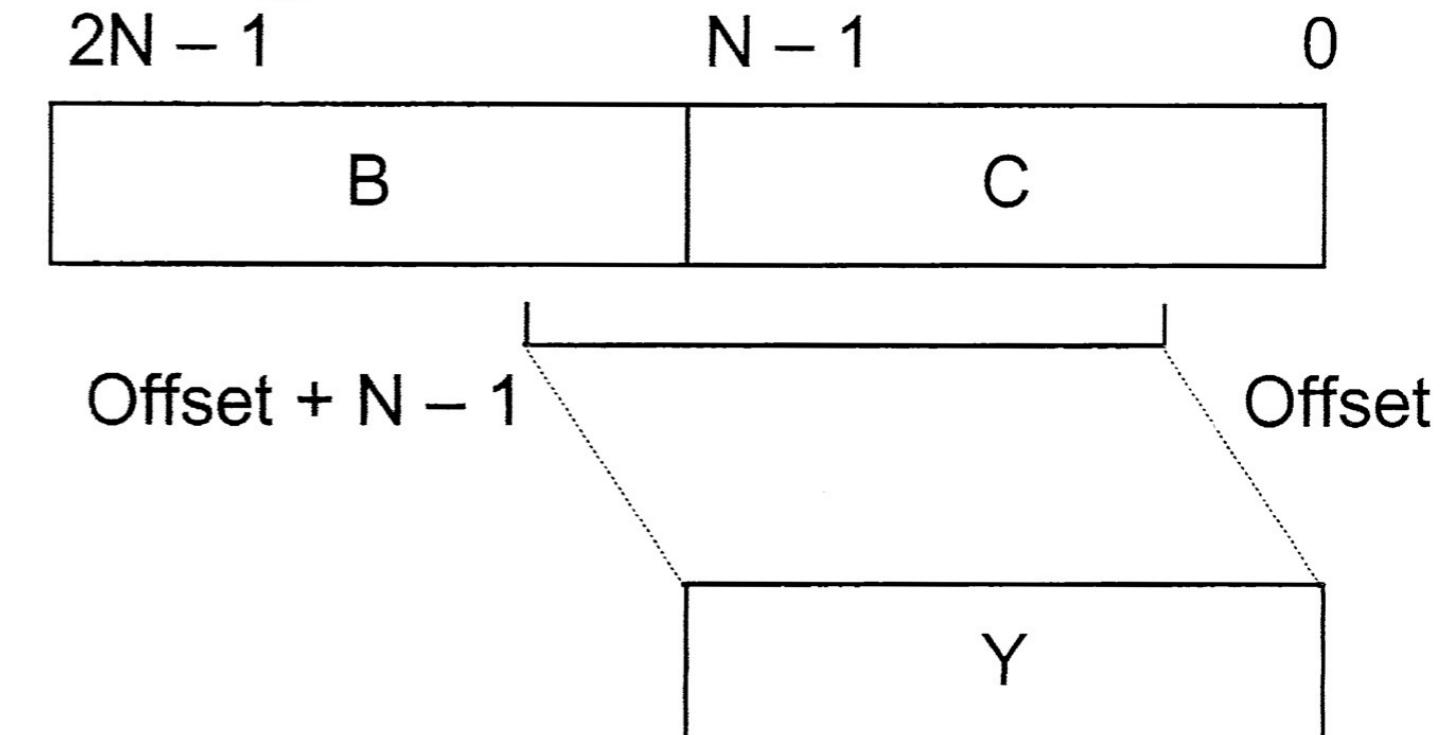- N-bit data shift k bits ($0 \leq k < N$)




Shift Type	B	C	Offset
Logical Right	0...0	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	0...0	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	$N-k$

Funnel Shifter

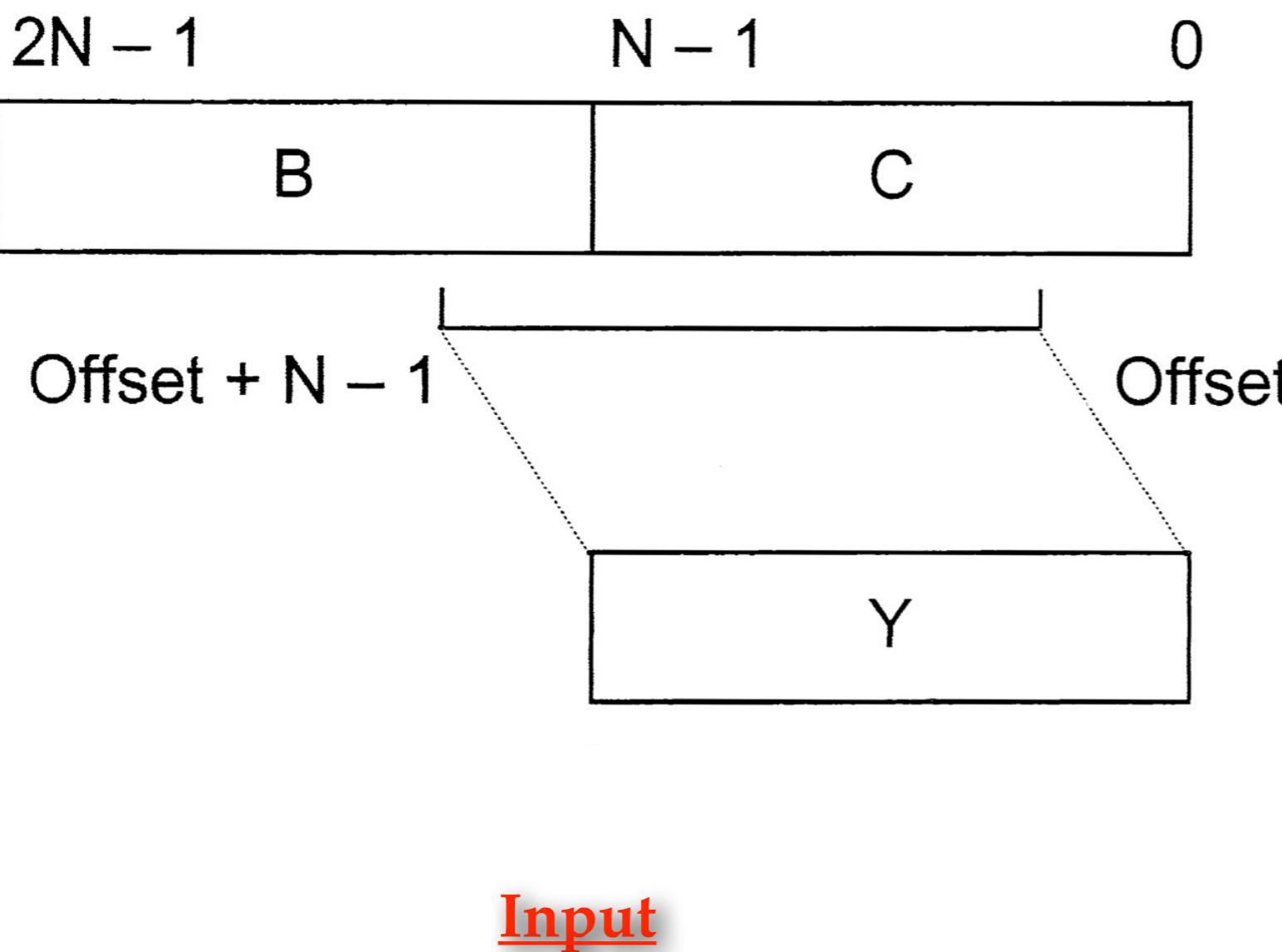

Input

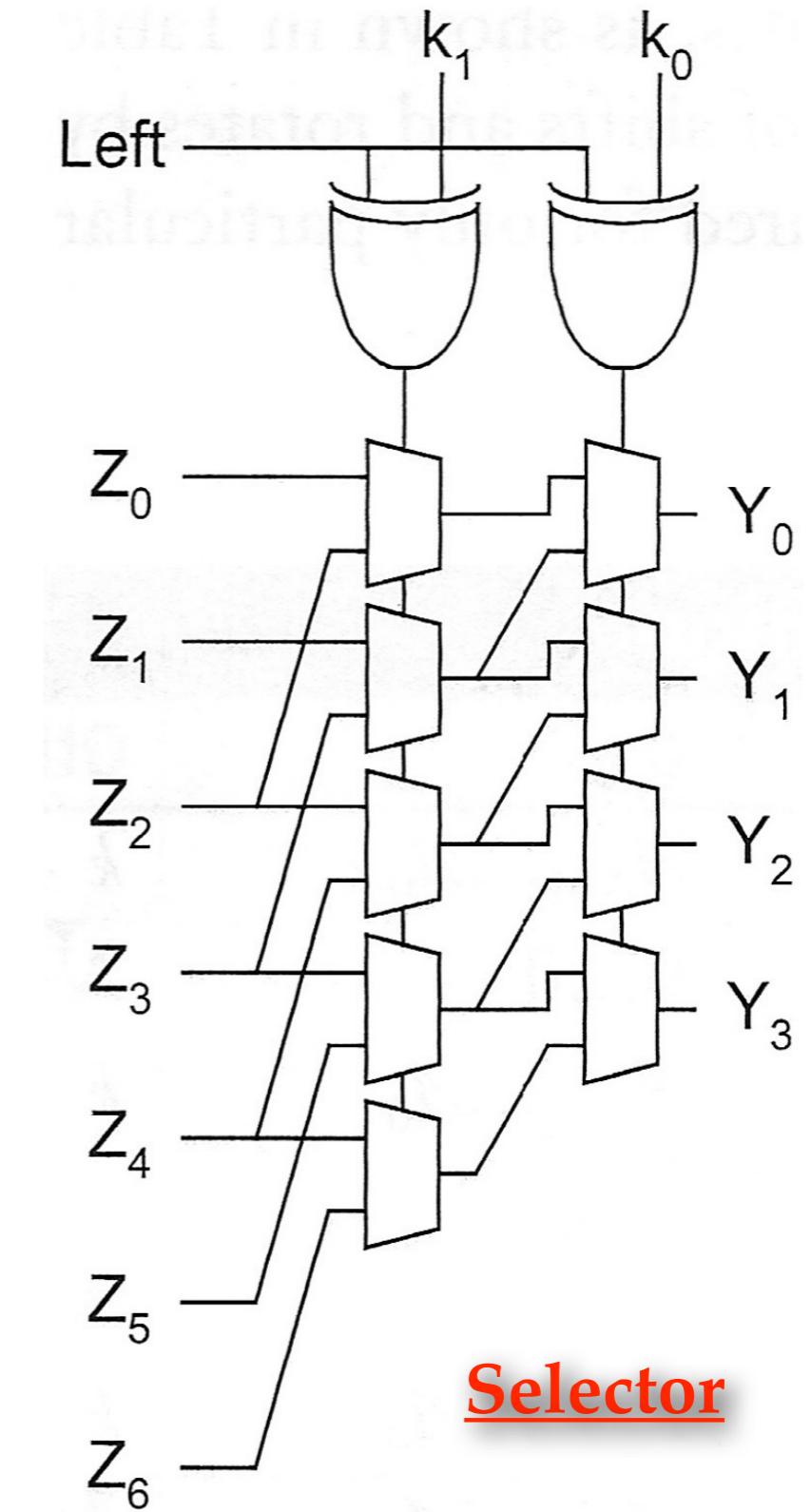

Selector

Verilog Description of a Left Shifter

```
module ShiftLeft(n, a, b);
parameter k=8;
parameter lk=3;
input [lk-1:0] n; // shift amount
input [k-1:0] a; // number to shift
output [2*k-2:0] b; // the output

assign b = a << n;

endmodule
```

Verilog Description of a Barrel Shifter

```
module BarrelShift(n, a, b);
parameter k=8;
parameter lk=3;
input [lk-1:0] n; // shift amount
input [k-1:0] a; // number to shift
output [k-1:0] b; // the output
wire [2*k-2:0] x; // output before wrapping

assign x = a << n;
assign b = x[k-1:0] | {1'b0, x[2*k-2:k]};

endmodule
```